

SULIT



**BAHAGIAN PEPERIKSAAN DAN PENILAIAN
JABATAN PENDIDIKAN POLITEKNIK
KEMENTERIAN PENDIDIKAN TINGGI**

JABATAN KEJURUTERAAN MEKANIKAL

PEPERIKSAAN AKHIR

SESI JUN 2017

DJM5103 : POWER ELECTRONICS

TARIKH : 02 NOVEMBER 2017

MASA : 11.15 PAGI - 1.15 PETANG (2 JAM)

Kertas ini mengandungi **SEMBILAN (9)** halaman bercetak.
Struktur (4 soalan)

Dokumen sokongan yang disertakan : Formula

JANGAN BUKA KERTAS SOALAN INI SEHINGGA DIARAHKAN

(CLO yang tertera hanya sebagai rujukan)

SULIT

INSTRUCTION:

This section consists of **FOUR (4)** structured questions. Answer **ALL** questions.

ARAHAN:

Bahagian ini mengandungi EMPAT (4) soalan struktur. Jawab semua soalan.

QUESTION 1**SOALAN 1**

- CLO1
C1
- (a) Draw and label the schematic symbol and block diagram for diode.
Lukis dan label simbol skematik dan gambarajah blok bagi diod.
- [5 marks]
[5 markah]
- CLO1
C2
- (b) Determine the condition of forward bias and reverse bias in a diode with the aid of a circuit diagram.
Dengan berbantuan gambarajah litar, terangkan keadaan pincang hadapan dan pincang balikan di dalam diod.
- [6 marks]
[6 markah]
- CLO1
C2
- (c) Explain the function of DC converter (rectifier) and give **THREE (3)** examples of its applications.
Terangkan fungsi penerus arus terus dan berikan TIGA (3) kegunaannya.
- [6 marks]
[6 markah]

CLO1
C3

- (d) A single phase half wave controlled rectifier connected to a 150V, 60 Hz source is supplying a resistive load, $10\ \Omega$. If the delay angle α is 30° , calculate;
Penerus separuh gelombang satu fasa disambungkan 150V, 60 Hz, beban perintang $10\ \Omega$. Jika sudut picuan ialah 30° , kirakan ;

- i. maximum load current, I_m
arus beban maksimum, I_m
- ii. RMS load current, I_{RMS}
arus beban purata punca ganda dua, I_{RMS}
- iii. power supplied to the load
kuasa dibekalkan ke beban

[8 marks]

[8 markah]

QUESTION 2

SOALAN 2

CLO1
C3

- (a) Sketch the circuit diagram and the waveform for the output voltage, V_o and output current, I_o of a step up chopper.

Lakarkan gambarajah litar dan gelombang bagi voltan keluaran, V_o dan arus keluaran, I_o bagi pemotong langkah-naik.

[8 marks]

[8 markah]

CLO1
C5

- (b) The DC converter (Chopper) has a resistive load of $R=10\ \Omega$ and the input voltage is 220V dc. The switching frequency, f is 1 kHz and the duty cycle is 50%. Value :

Sebuah penukar DC (Pemenggal) mempunyai beban rintangan $R=10\ \Omega$ dan voltan masukan ialah $V_s = 220V$ dc. Frekuensi penyuisan f ialah 1 kHz dan beroperasi pada kitar tugas 50%. Nilai :

- i. The average output voltage, V_o

Voltan purata keluaran, V_o

- ii. The average output current, I_o

Arus keluaran rms, I_o

[5 marks]

[5 markah]

CLO1
C3

- (c) A DC shunt motor 220V has an armature resistance, $R_a = 0.5\ \Omega$, a drop voltage of 5V and armature current, $I_a = 20A$.

Sebuah motor pirau arus terus 220V mempunyai $R_a = 0.5\ \Omega$ rintangan angker, 5V susut voltan dan arus angker, $I_a = 20A$.

- i. Sketch the circuit diagram for DC shunt motor.

Lakarkan gambarajah litar bagi motor pirau arus terus. [4 marks]

[4 markah]

SULIT

- ii. Calculate back e.m.f.

Kirakan balikan daya gerak elektromotif.

[2 marks]

[2 markah]

- iii. Calculate armature current if back e.m.f is 185V.

Kirakan arus angker jika balikan daya gerak elektromotif adalah 185V.

[2 marks]

[2 markah]

CLO1
C4

- (d) Explain the operation of controlling a DC motor in the second quadrant in Figure 2(d).

Terangkan prinsip operasi bagi kawalan motor arus terus pada sukuan kedua seperti Rajah 2(d).

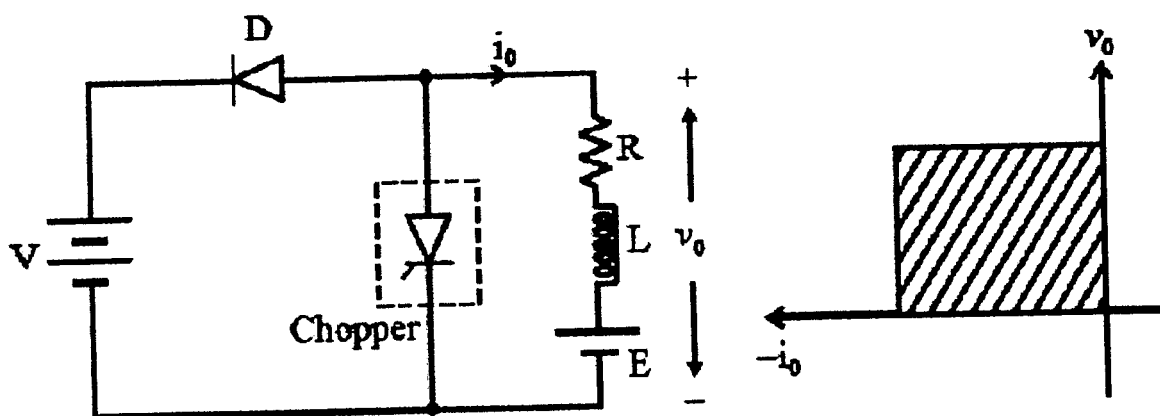


Figure 2 (d)

Rajah 2 (d)

[4 marks]

[4 markah]

QUESTION 3

SOALAN 3

CLO1
C2

- (a) Describe the function of AC converters and identify **FOUR (4)** examples of its application.

Terangkan fungsi penukar AC dan kenalpasti EMPAT (4) contoh aplikasinya.

[6 marks]

[6 markah]

CLO1
C3

- (b) i. Sketch and label the circuit diagram for single phase full bridge inverter circuit with resistive load.

Lukiskan dan labelkan gambarajah litar penyongsang jambatan penuh satu fasa dengan beban rintangan.

[6 marks]

[6 markah]

- ii. Explain the operational principle of the circuit and draw the output voltage, V_o and current output, I_o waveform load. in Question 3 (b)(i).

Terangkan prinsip operasi litar dan lukiskan gelombang voltan keluaran, V_o dan arus keluaran, I_o bagi litar pada seperti di Soalan 3 (b) (i).

[4 marks]

[4 markah]

CLO1
C4

- (c) Explain the operation of single-phase to single-phase cycloconverter and sketch the waveform for supply voltage and output voltage in Figure 3 (c).

Terangkan operasi penukar siklo satu fasa dan lakarkan gelombang voltan bekalan dan voltan keluaran di Rajah 3 (c).

[9 marks]

[9 markah]

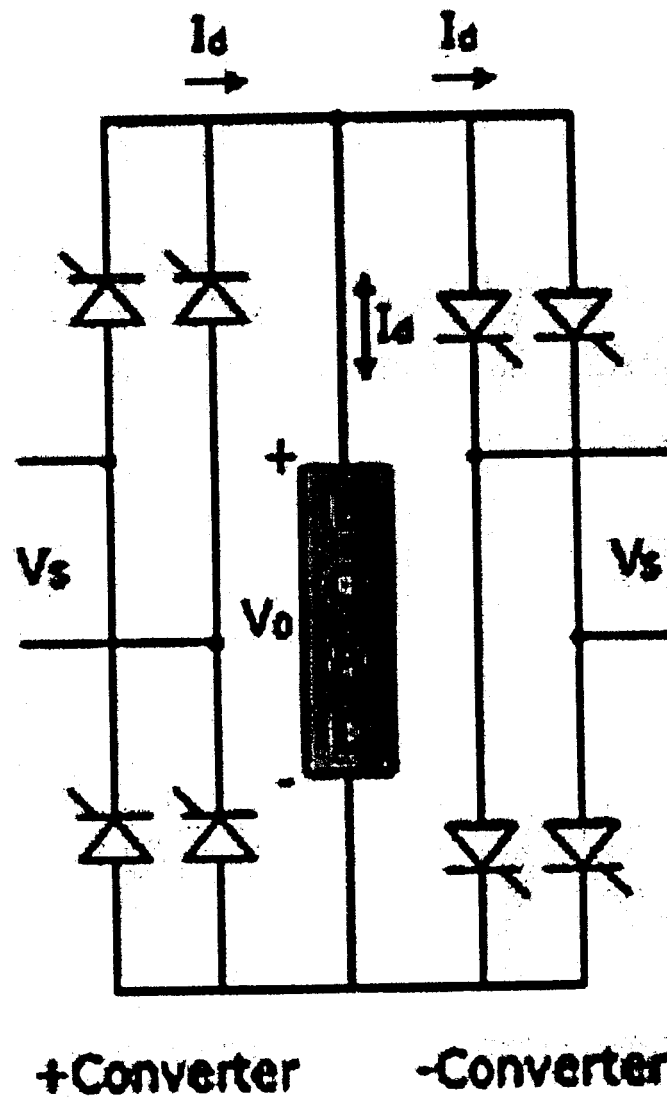


Figure 3 (c)

Rajah 3 (c)

SULIT

QUESTION 4

SOALAN 4

CLO1
C2

- (a) Identify **THREE (3)** main parts of DC motor and state **THREE (3)** examples of its application.

Kenalpasti TIGA (3) bahagian utama motor arus terus dan senaraikan TIGA (3) kegunaannya di dalam industri.

[5 marks]

[5 markah]

CLO1
C3

- (b) A three phase induction motor has 6 poles with a full load speed of 1100 rpm and a frequency of 60 Hz. Calculate :

Sebuah motor aruhan tiga fasa 6 kutub mempunyai kelajuan penuh 1100 putaran per minit dan frekuensi 60 Hz. Kirakan :

i. Synchronous speed, N_s
Kelajuan segerak, N_s

ii. Rotor Slip, s
Gelinciran rotor, s

iii. Rotor frequency, f_r
Frekuensi rotor, f_r

iv. Percentage of slip
Peratus gelinciran

[10 marks]

[10 markah]

CLO1
C4

- (c) Explain **TWO (2)** primary parts of the structure of AC motor and the basic operational of single-phase induction motor work.

Terangkan DUA (2) struktur utama motor arus ulangalik dan operasi motor aruhan satu fasa bekerja.

[10 marks]

[10 markah]

SOALAN TAMAT

DJM5103 : POWER ELECTRONICS

LIST OF FORMULA

Controlled half wave rectifier:

$$V_o = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin(\omega t) d\omega t$$

$$V_o = \frac{V_m}{2\pi} [1 + \cos \alpha]$$

$$V_{o,rms} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} [V_m \sin(\omega t)]^2 d\omega t}$$

$$V_{o,rms} = \frac{V_m}{2} \sqrt{1 - \frac{\alpha}{180} + \frac{\sin(2\alpha)}{2\pi}}$$

$$P_o = I_{rms}^2 \cdot R$$

$$P_o = \frac{V_{o,rms}^2}{R}$$

Controlled full wave rectifier:

$$V_o = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin(\omega t) d\omega t$$

$$V_o = \frac{V_m}{\pi} [1 + \cos \alpha]$$

$$V_{o,rms} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} [V_m \sin(\omega t)]^2 d\omega t}$$

$$V_{o,rms} = V_m \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin(2\alpha)}{4\pi}}$$

Motor drives:

$$V_f = R_f i_f + L_f \frac{di_f}{dt}$$

$$E_g = K_v \omega I_f$$

$$V_f = \frac{2V_m}{\pi} \cos \alpha_f$$

$$I_f = \frac{V_f}{R_f}$$

$$\eta = \frac{P_{output}}{P_{input}} \times 100\%$$

$$P_d = T_d \omega$$

$$T_d = K_v I_f I_a$$

$$V = E_b + I_a R_a$$

$$N_s = \frac{120 f}{P}$$

$$\% s = \frac{N_s - N_r}{N_s}$$

$$f_r = s \cdot f$$