

SULIT



**BAHAGIAN PEPERIKSAAN DAN PENILAIAN
JABATAN PENDIDIKAN POLITEKNIK DAN KOLEJ KOMUNITI
KEMENTERIAN PENDIDIKAN MALAYSIA**

JABATAN KEJURUTERAAN PETROKIMIA

PEPERIKSAAN AKHIR

SESI JUN 2019

DGP1013: ELECTRICAL TECHNOLOGY

TARIKH : 04 NOVEMBER 2019

MASA : 2.30 PETANG - 4.30 PETANG (2 JAM)

Kertas ini mengandungi **SEMBILAN (9)** halaman bercetak.

Struktur (4 soalan)

Dokumen sokongan yang disertakan : Tiada

JANGAN BUKA KERTAS SOALAN INI SEHINGGA DIARAHKAN

(CLO yang tertera hanya sebagai rujukan)

SULIT

INSTRUCTION:

This section consists of **FOUR (4)** questions. Answer **ALL** of them.

ARAHAN:

Bahagian ini mengandungi **EMPAT (4)** soalan. Jawab **SEMUA** soalan.

QUESTION 1**SOALAN 1**

CLO1
C1

- (a) List the colour of resistance with value of $13\text{M}\Omega \pm 10\%$.

Senaraikan warna bagi perintang dengan nilai $13\text{M}\Omega \pm 10\%$.

[6 marks]

[6 markah]

CLO1
C2

- (b) Short Circuit will occur if some errors exist in the circuit. By using a diagram, explain the short circuit.

Litar pintas akan berlaku apabila wujudnya beberapa ralat pada litar. Dengan bantuan rajah, jelaskan litar pintas tersebut.

[7 marks]

[7 markah]

CLO1
C3

- (c) Calculate the value of I_{r1} , I_{r2} and I_R by referring to **Figure 1 (c)** using Kirchoff Law.

*Kira nilai I_{r1} , I_{r2} and I_R dengan merujuk kepada **Rajah 1 (c)** menggunakan Hukum Kirchoff.*

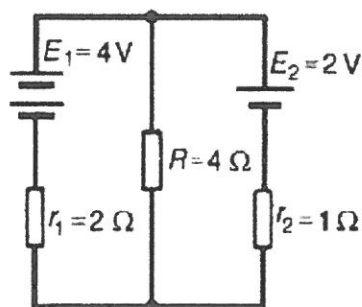


Figure 1 (c)

Rajah 1 (c)

[12 marks]

[12 markah]

QUESTION 2

SOALAN 2

CLO1
C1

- (a) Draw the symbol and state the unit for Inductor and Capacitor.

Lukiskan simbol dan nyatakan unit bagi Pearuh dan Pemuat.

[5 marks]

[5 markah]

CLO1
C2

- (b) Series circuit is a connection when there is only one path for current to flow. Calculate:

*Litar Siri adalah sambungan apabila hanya ada satu laluan bagi arus untuk mengalir.**Kira:*

- i. The Total Inductance in
- Figure 2 (b)(i)**
- .

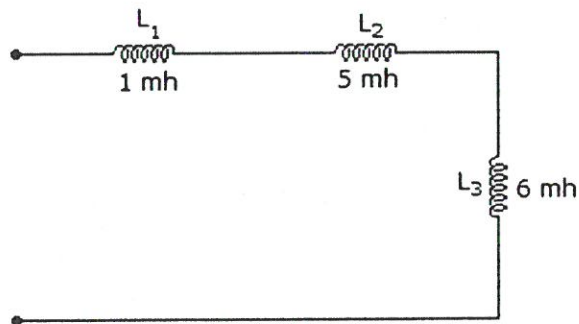
*Jumlah Aruhan bagi **Rajah 2 (b)(i)**.*

Figure 2 (b)(i)

Rajah 2 (b)(i)

[4 marks]

[4 markah]

- ii. The Total Capacitance in **Figure 2 (b)(ii)**.

*Jumlah Kemuatan bagi **Rajah 2 (b)(ii)**.*

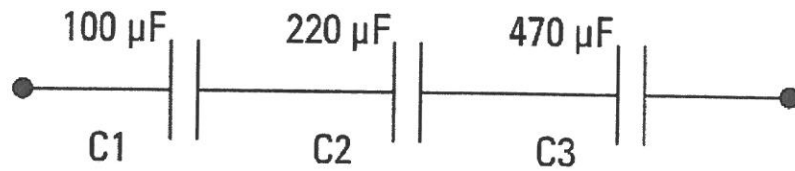


Figure 2 (b)(ii)

Rajah 2 (b)(ii)

[6 marks]

[6 markah]

CLO1
C3

- (c) Calculate the Total Impedance, Z in **Figure 2 (c)**.

*Kira Jumlah Galangan, Z bagi **Rajah 2 (c)**.*

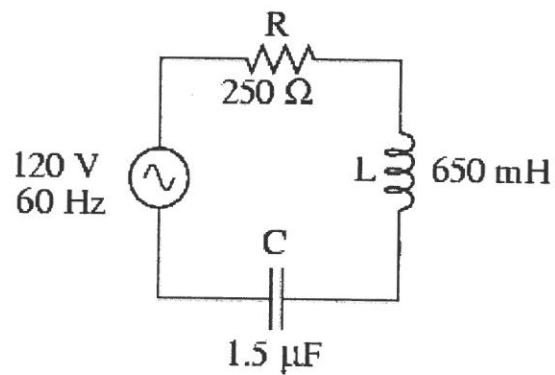


Figure 2 (c)

Rajah 2 (c)

[10 marks]

[10 markah]

QUESTION 3

SOALAN 3

CLO1
C1

(a) Define Magnet, Magnetism and Pure Magnet.

Definisikan Magnet, Kemagnetan dan Magnet Tulen.

[6 marks]

[6 markah]

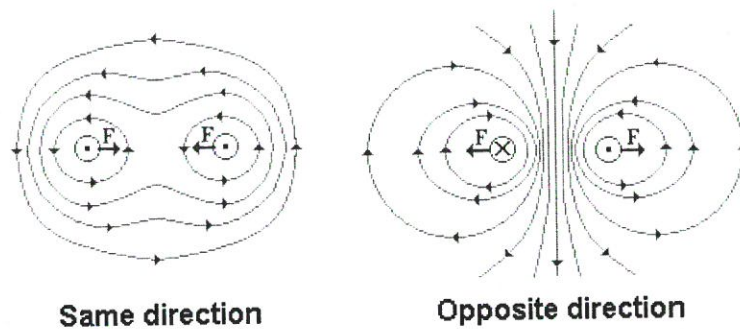
CLO1
C2(b) Describe what happened in **Figure 3 (b)**.*Terangkan apa yang berlaku dalam Rajah 3 (b).*

Figure 3 (b)

Rajah 3 (b)

[10 marks]

[10 markah]

CLO1
C3

(c) One soft iron solenoid with cross sectional area of 600mm^2 has an average length of 300mm and is wound with 300 turns of wire with 2A current running through it. Given the relative permeability, μ_r is 900. Calculate.

Satu solenoid besi lembut dengan luas keratan rentas 600mm^2 mempunyai purata panjang 300mm dan digelung dengan 300 gelung wayar dengan arus 2A melaluinya.

Diberi ketelapan relatif μ_r adalah 900. Kira:

i. Magnetomotive Force, F_m .

Dayakerak Magnet, F_m .

[3 marks]

[3 markah]

- ii. Magnetic Field Strength, H .

Kekuatan Medan Magnet, H .

[3 marks]

[3 markah]

- iii. Magnetic Flux Density, B .

Ketumpatan Fluks Magnet, H .

[3 marks]

[3 markah]

QUESTION 4

SOALAN 4

CLO1
C1

- (a) Draw a schematic diagram for Step Up Transformer and Step Down Transformer.

Lukiskan diagram skematik bagi Pengubah Langkah Naik dan Pengubah Langkah Turun.

[6 marks]

[6 markah]

CLO1
C2

- (b) Describe Isolator (Coupling) Transformer.

Terangkan Pengubah Pengasing.

[9 marks]

[9 markah]

CLO1
C3

- (c) **Figure 4 (c)** below shows a Transformer with 2400 Primary Turns.

Rajah 4 (c) di bawah menunjukkan sebuah Pengubah dengan 2400 putaran Primer.

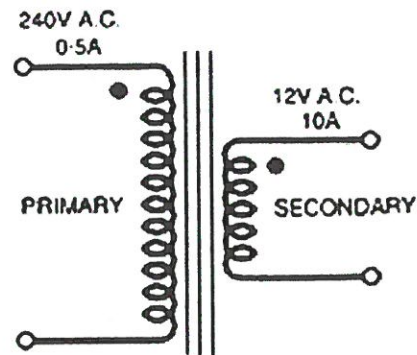


Figure 4 (c)

Rajah 4 (c)

- i. Calculate the secondary voltage, V_s .

Kira voltan sekunder, V_s .

[5 marks]

[5 markah]

- ii. Calculate the Expected Ratio, K .

Kira Nisbah Terjangka, K .

[3 marks]

[3 markah]

- iii. Relate the answer for (ii) above to the type of transformer.

Kaitkan jawapan pada (ii) di atas dengan jenis pengubah.

[2 marks]

[2 markah]

SOALAN TAMAT

Formula for Basic Electrical Principles**Ohms Law:**

$$V = IR \text{ or } I = \frac{V}{R} \text{ or } R = \frac{V}{I}$$

Charge: $Q = It$ **Resistivity :**

$$R = \frac{\rho l}{A} \text{ or } R = k \frac{l}{A} \text{ or } R = kl$$

Power :

$$P = I^2 R \text{ or } P = IV \text{ or } P = \frac{V^2}{R}$$

Electrical Energy: $E = Pt$ **Resistance:****Series :** $R_T = R_1 + R_2 + \dots + R_N$ **Parallel :** $R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}}$ **Parallel 2 branch:**

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

Voltage divider rule (VDR):

$$V_N = \left(\frac{R_N}{R_T} \right) V_T$$

Current divider rule (CDR):

$$I_N = \left(\frac{R_T}{R_N} \right) I_T$$

Current divider rule for 2 branch:

$$I_1 = \left(\frac{R_2}{R_1 + R_2} \right) I_T \text{ or } I_2 = \left(\frac{R_1}{R_1 + R_2} \right) I_T$$

Inductor in parallel:

$$L_T = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_N}}$$

Capacitive reactance, X_C :

$$X_C = \frac{1}{2\pi f C}$$

Inductive reactance, X_L :

$$X_L = 2\pi f L$$

R-C series :

$$Z = \sqrt{R^2 + X_C^2}$$

R-L series :

$$Z = \sqrt{R^2 + X_L^2}$$

R-L-C series:

$$Z = \sqrt{R^2 + (X_C - X_L)^2}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Electromagnetic induction:

$$E = Blv \sin \theta, \quad F_m = Hl, \quad F_m = IN, \quad F_m = S\phi$$

$$B = \frac{\phi}{A}, \quad \mu = \mu_0 \mu_r, \quad \mu = \frac{B}{H}$$

$$S = \frac{F_m}{\phi} = \frac{Hl}{BA} = \frac{l}{\left(\frac{B}{H} \right) A} = \frac{l}{\mu_0 \mu_r A}$$

Charge on capacitor :

$$Q = CV \text{ or } C = \frac{Q}{V} \text{ or } V = \frac{Q}{C} , E = \frac{1}{2} QV$$

Capacitor in series:

$$C_T = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N}}$$

Capacitor in parallel:

$$C_T = C_1 + C_2 + \dots + C_N$$

Inductor in series:

$$L_T = L_1 + L_2 + \dots + L_N$$

Transformer:

$$\frac{N_2}{N_1} = \frac{V_2}{V_1} \text{ or } \frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

$$S = V_1 I_1 = V_2 I_2$$

$$K = \frac{N_S}{N_P} = \frac{E_S}{E_P} = \frac{V_S}{V_P}$$