

INSTRUCTION:

This section consists of **FOUR (4)** structured questions. Answer **ALL** questions.

ARAHAN:

Bahagian ini mengandungi **EMPAT (4)** soalan berstruktur. Jawab **SEMUA** soalan.

QUESTION 1**SOALAN 1**

CLO1

- (a) Name the component and unit for Figure 1(a) below.

Namakan komponen dan unit untuk Rajah 1(a) di bawah.

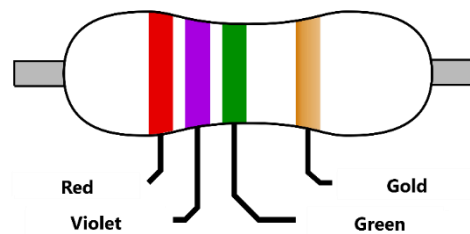


Figure 1(a) / Rajah 1(a)

[4 marks]

[4 markah]

CLO1

- (b) Circuit diagram in Figure 1(b) has Total Resistance of 11 k Ω . Approximate:

Litar pada Rajah 1(b) mempunyai Jumlah Rintangan 11 k Ω . Anggarkan:

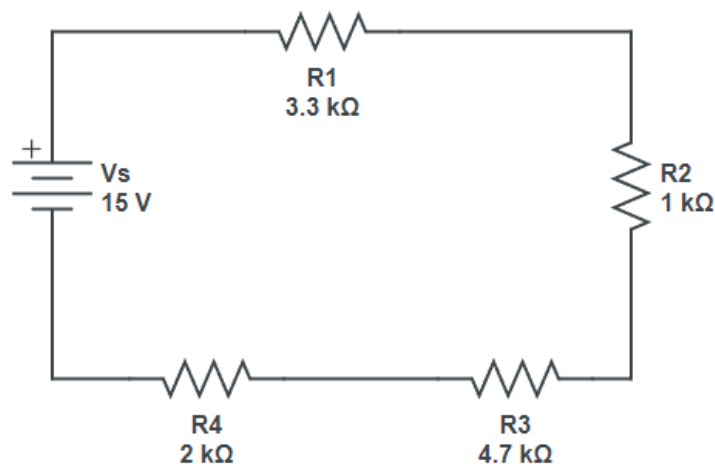


Figure 1(b) / Rajah 1(b)

- i. Total Current, I_T .

Jumlah Arus, I_T .

[2 marks]

[2 markah]

- ii. Voltage on R_2 , V_{R2} .

Voltan pada R_2 , V_{R2} .

[3 marks]

[3 markah]

- iii. Voltage on R_4 , V_{R4} .

Voltan pada R_4 , V_{R4} .

[3 marks]

[3 markah]

CLO1

- (c) Calculate I_1 , I_2 and I_3 for the circuit in Figure 1(c) below with the following parameter by using Kirchoff's Law:

Kira I_1 , I_2 dan I_3 bagi litar dalam Rajah 1(c) di bawah dengan parameter yang berikut dengan menggunakan Hukum Kirchoff:

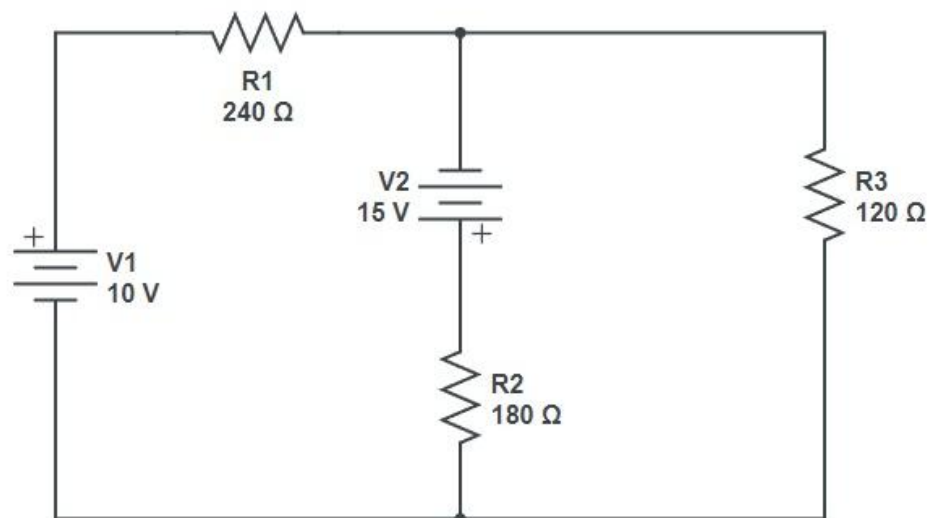


Figure 1(c) / Rajah 1(c)

[13 marks]

[13 markah]

QUESTION 2

SOALAN 2

CLO1

- (a) State the name of the component A and B in Figure 2(a) below.

Nyatakan nama komponen A dan B dalam Rajah 2(a) di bawah.

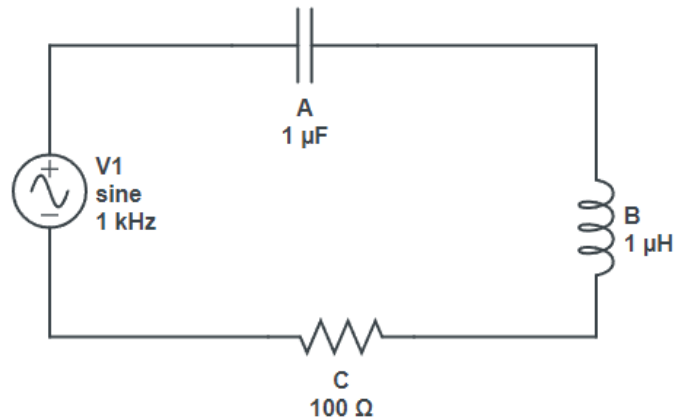


Figure 2(a) / Rajah 2(a)

[3 marks]

[3 markah]

CLO1

- (b) Capacitor and Inductor are the components that are widely used in electronic circuit.

Pemuat dan Peraruh adalah komponen yang digunakan secara meluas dalam litar elektronik.

- i. Approximate the Total Inductance (L_{Total}) in Figure 2(b)(i).

Anggarkan Jumlah Pearuh (L_{Total}) dalam Rajah 2(b)(i).

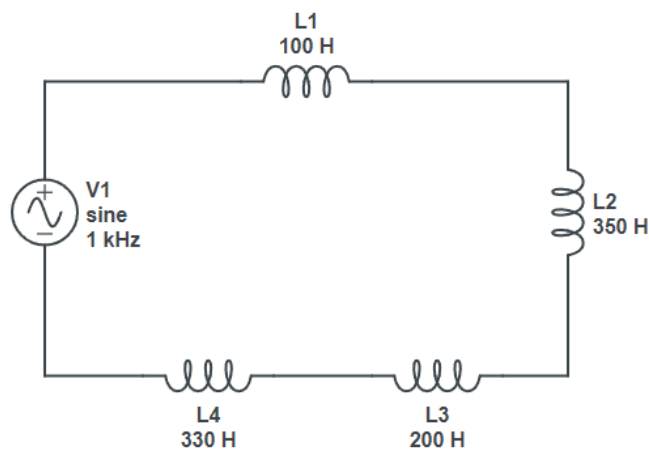


Figure 2(b)(i) / Rajah 2(b)(i)

[5 marks]

[5 markah]

- ii. Approximate the Total Capacitance (C_{Total}) in Figure 2(b)(ii).

Anggarkan Jumlah Kemuatan (C_{Total}) dalam Rajah 2(b)(ii).

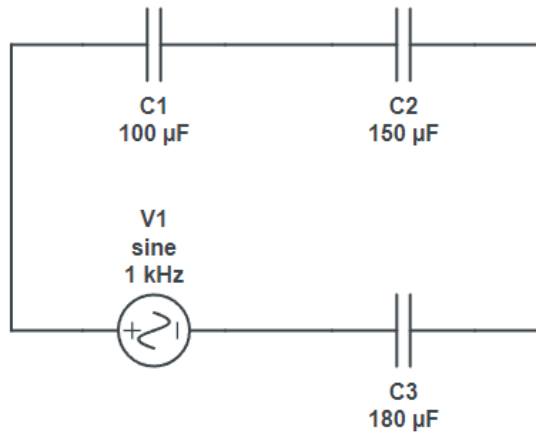


Figure 2(b)(ii) / Rajah 2(b)(ii)

[6 marks]

[6 markah]

CLO1

- (c) Impedance is the measure of the opposition to electrical flow.

Galangan adalah ukuran kepada halangan dalam aliran elektrik.

- i. Calculate Impedance (Z) by referring to Figure 2(c)(i).

Kira Galangan (Z) dengan merujuk kepada Rajah 2(c)(i).

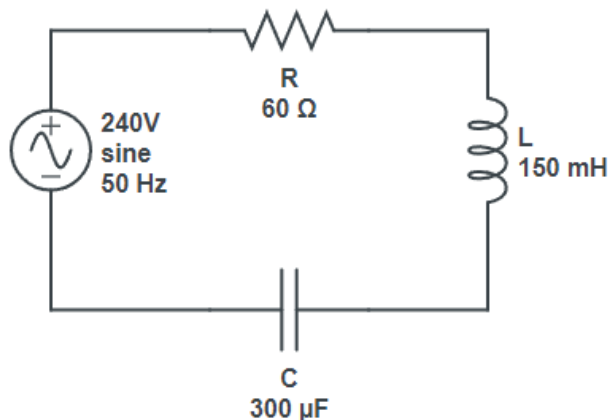


Figure 2(c)(i) / Rajah 2(c)(i)

[8 marks]

[8 markah]

- ii. Draw Impedance Triangle for Figure 2(c)(i) above.

Lukis Segitiga Galangan untuk Rajah 2(c)(i) di atas.

[3 marks]

[3 markah]

QUESTION 3

SOALAN 3

- | | |
|------|---|
| CLO1 | <p>(a) Define Magnet.
<i>Definisikan Magnet.</i></p> <p style="text-align: right;">[4 marks]
[4 markah]</p> |
| CLO1 | <p>(b) Compare Electric Circuit and Magnetic Circuit with an aid of a diagram.
<i>Bandingkan Litar Elektrik dan Litar Magnet dengan bantuan rajah.</i></p> <p style="text-align: right;">[9 marks]
[9 markah]</p> |
| CLO1 | <p>(c) A coil of 300 turns is wound uniformly on a ring of non-magnetic material. The ring has a mean circumference of 40 cm and a uniform cross-sectional area of 4 cm². If the current in the coil is 5 A, calculate:
<i>Satu gegelung 300 pusingan dililit secara seragam pada cincin bukan magnet. Cincin itu mempunyai purata lilitan 40 cm dan luas keratan rentas seragam 4 cm². Jika arus dalam gegelung ialah 5 A, kira:</i></p> <p>i. Magnetic Field Strength, H.
<i>Kekuatan Medan Magnet, H.</i> [4 marks]
[4 markah]</p> <p>ii. Permeability, μ.
<i>Kebolehtelapan, μ.</i> [4 marks]
[4 markah]</p> <p>iii. Flux Density, B.
<i>Ketumpatan Fluks, B.</i> [4 marks]
[4 markah]</p> |

QUESTION 4

SOALAN 4

- CLO1 (a) Name Label A, B, C and D by referring to Figure 4(a) below.

Labelkan label A, B, C dan D dengan merujuk kepada Rajah 4(a) di bawah.

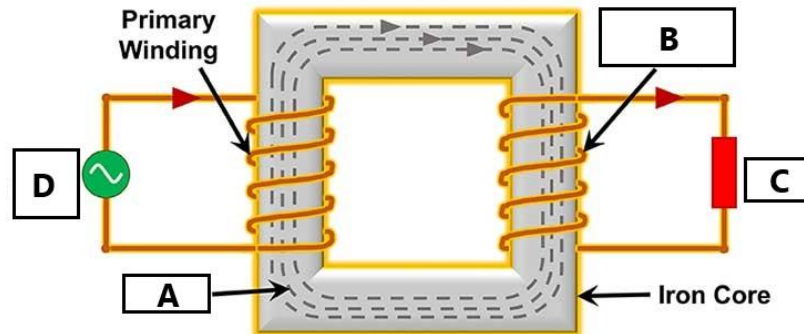


Figure 4(a) / Rajah 4(a)

[4 marks]

[4 markah]

- CLO1 (b) Explain Step Up Transformer and Step Down Transformer with the aid of a diagram.

Bincangkan Pengubah Langkah Naik dan Pengubah Langkah Turun dengan bantuan rajah.

[10 marks]

[10 markah]

- CLO1 (c) An ideal transformer is shown in Figure 4(c) below.

Sebuah pengubah ideal ditunjukkan seperti Rajah 4(c) dibawah.

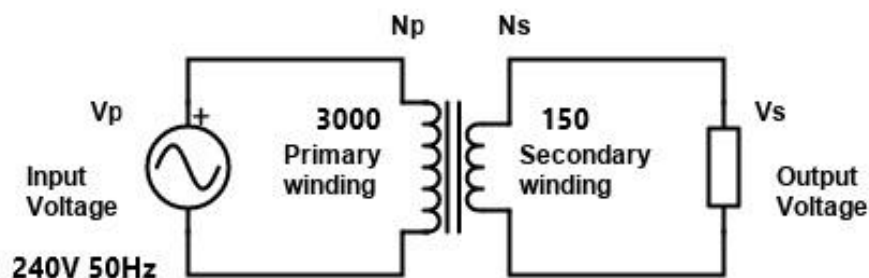


Figure 4(c) / Rajah 4(c)

- i. Calculate secondary voltage, V_s .

Kira voltan sekunder, V_s .

[5 marks]

[5 markah]

- ii. Calculate Expected Ratio, K .

Kira Nisbah Terjangka, K .

[4 marks]

[4 markah]

- iii. Show the type of this transformer.

Tunjukkan jenis pengubah ini.

[2 marks]

[2 markah]

SOALAN TAMAT