

ELECTRICAL CIRCUITS

2024

ALTERNATING CURRENT
SINUSOIDAL STEADY STATE CIRCUIT ANALYSIS
RESONANCE



Ts. AZIHA BINTI MOHD NOR
RAZIMAH BINTI ABDUL RAHIM
SUHAIDA BINTI ABDUL HALIM

ELECTRICAL CIRCUITS

2024

**ALTERNATING CURRENT
SINUSOIDAL STEADY STATE CIRCUIT ANALYSIS
RESONANCE**



Cataloguing-in-Publication Data

Perpustakaan Negara Malaysia

A catalogue record for this book is available
from the National Library of Malaysia

eISBN 978-629-7643-45-8

All rights reserved.

No part of this publication may be reproduced, stored in a retrieval system, or transmitted in any form or by any means, electronic, mechanical, photocopying, recording, or otherwise without the prior permission of Jabatan Pengajian Politeknik dan Kolej Komuniti, Kementerian Pengajian Tinggi.

Published by;
POLITEKNIK PORT DICKSON
KM14, JALAN PANTAI, 71050
SI RUSA, PORT DICKSON
NEGERI SEMBILAN

September 2024

ACKNOWLEDGEMENT

PATRON

Hasan bin Mohd Sharif B.C.M, P.J.K
Director of Politeknik Port Dickson

ADVISORS

Ts. Dr. Engku Shahrulerizal bin Engku Ab Rahman
Deputy Director (Academic, Politeknik Port Dickson)

Izwan Kamal bin Abdul Wahab
Head of Electrical Engineering Department
Politeknik Port Dickson

Jumaliah binti Jahuri
Head of Diploma in Electrical Engineering Programme
Politeknik Port Dickson

EDITOR

Alizawati binti Mat Zim
Department of Electrical Engineering

FACILITATORS

Che Azlina binti Che Norohoseni
Department of Mechanical Engineering

Ahmad Qusyairi bin Ahmad Khairiri
Department of Civil Engineering

WRITERS

Ts. Aziha binti Mohd Nor
Razimah binti Abdul Rahim
Suhaida binti Abdul Halim

we would like to convey our utmost gratitude to the Department of Polytechnic and Community College Education particularly the E- learning and Instructional Division (BIPD) for funding our e-book project.

We hereby declare that this book is our original work. To the best of our knowledge. It contains no materials previously written or published by another person. However if there is any, due acknowledgment and credit are mentioned accordingly in the e-book.

PREFACE

Electrical circuits is a fundamental to understand the principles of electrical engineering and forms the backbone of many technological advancements in our modern world. This book is designed to provide students with the knowledge related to alternating current of electrical circuits.

The chapters in this book are structured to gradually build the reader's understanding, starting from the basic concepts of alternating current, sinusoidal steady state circuit analysis and resonance. Each chapter includes detailed explanations, illustrative examples, and practical exercises designed to reinforce learning and encourage critical thinking.

In writing this book, we have drawn upon our experiences in teaching electrical engineering. Our goal is to make the subject accessible to all readers, regardless of their prior knowledge, while also challenging them to deepen their understanding and apply what they have learned to real-world problems.

We want to express our gratitude to our colleagues and students who have contributed valuable feedback during the development of this book. Their insights have been instrumental in shaping the content and ensuring that it meets the needs of a diverse readers.

Hopefully this book will serve as a reliable resource for anyone who is interested in the study of electrical circuits and inspire further exploration and innovation in this exciting field.

Ts. AZIHA BINTI MOHD NOR
RAZIMAH BINTI ABDUL
SUHAIDA BINTI ABDUL HALIM

Table of Contents

01 Alternating Voltage And Current

- 1.1 Remember an alternating current
- 1.2 Understand the generation of alternating current
- 1.3 Apply the sinusoidal voltage and current values of a sine wave
- 1.4 Apply a sinusoidal wave for an angular measurement
- 1.5 Apply the understanding of phasor to represent a sine wave
- 1.6 Apply the basic circuit laws of resistive AC circuits

02 Sinusoidal Steady State Circuit Analysis

- 2.1 Understand the AC baic
- 2.2 Apply the circuit with inductive and capacitive loads.
- 2.3 Apply the series and parallel R-L-C circuits.
- 2.4 Apply the combination of the series-parallel R-L-C circuits.
- 2.5 Understand the power in AC circuits.
- 2.6 Apply the understanding of the power consumption in AC circuits.

03 Resonance

- 3.1 Understand resonance in series and parallel circuits.
- 3.2 Apply resonance in series and parallel circuits.

TOPIC 1


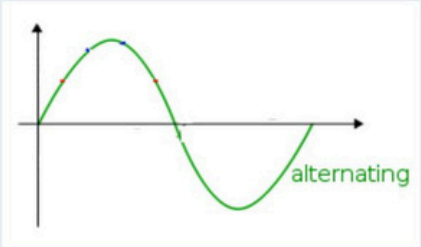
ALTERNATING VOLTAGE AND CURRENT





1.1 REMEMBER AN ALTERNATING CURRENT




1.1.1 DISTINGUISH BETWEEN DIRECT CURRENT AND ALTERNATING CURRENT

DC	AC
The flow of electrical charge is only in one direction	The movement of electrical charge periodically reverses directions.
	
The output voltage will remain essentially constant over time	AC source of electrical power charges constantly in amplitude & regularly changes polarity

	ALTERNATING CURRENT	DIRECT CURRENT
Amount of energy that can be carried	Safer to transfer over longer city distances and can provide more power	Voltage of DC cannot travel very far until it begins to lose energy
Flow of Electrons:	Electrons keep switching directions-forward and backward 	Electrons move steadily in one direction or 'forward' 

	ALTERNATING CURRENT	DIRECT CURRENT
Cause of the direction of flow of electrons	Rotating magnet along the wire	Steady magnetism along the wire
Frequency	The frequency of alternating current is 50Hz or 60Hz depending upon the country.	The frequency of direct current is zero.
Direction	It reverses its direction while flowing in a circuit	It flows in one direction in the circuit
Current	It is the current of magnitude varying with time	It is the current of constant magnitude

1.1.2 Why AC is used in preference to DC

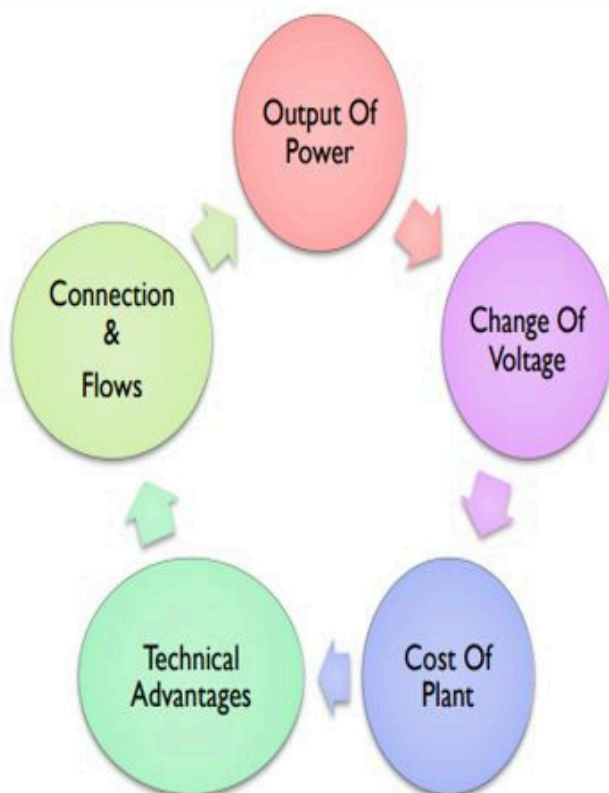

The **Output Of Power** Stations comes from a rotary turbine, which by its nature is AC and therefore requires no power electronics to convert to DC



It is much **Easier To Change The Voltage** of AC electricity for transmission and distribution

The **Cost Of Plant** associated with AC transmission (Circuit Breakers, Transformers etc) is much lower than the equivalent of DC transmission

AC transmission provides a number of **Technical Advantages**. When a fault on the network occurs, a large fault current occurs.

It is also **easier to meter AC connections and monitor power flows** across a network

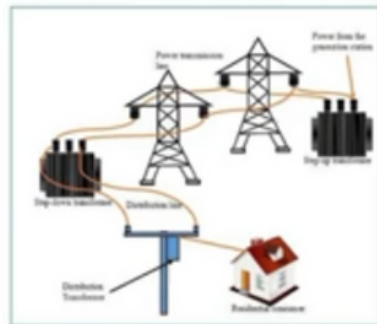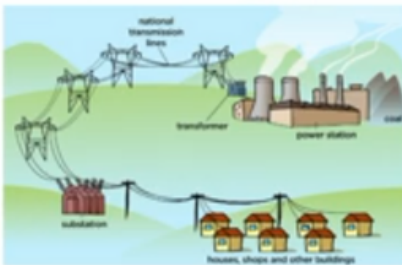WHY WE USE **AC** FOR HOUSEHOLD ? WHY NOT **DC** ?



IMPORTANT CONCEPTS

https://youtu.be/_CytmsGy3xc?feature=shared

1.1.2 The sources of alternating current



Alternating current generator



Generating plant



Wind power station




Any other AC sources?




Generation of an alternating current

ALTERNATOR

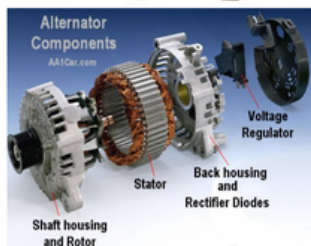- An alternator is a machine which produces the Alternating Current, by converting mechanical energy into electrical energy.
- It is termed as an AC generator or the synchronous generator.
- Electricity is produced when a magnetic field spins inside the windings of wire.



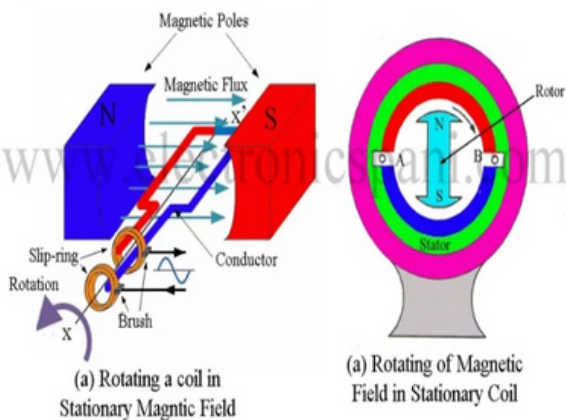2 METHODS TO GENERATE ALTERNATING CURRENT



Alternating voltage may be generated by

- * rotating a coil in the magnetic field or
- * rotating a magnetic field within a stationary coil.

The value of the voltage generated depends on :

- o The number of turns in the coil.
- o Strength of the field.
- o The speed at which the coil or magnetic field rotates.

1.2.1 Faraday's Law and Lenz's law in generating AC current

Faraday's Law:


Any change in the magnetic environment of a coil of wire will cause a voltage (emf) to be induced in the coil.

Faraday's law of electromagnetic induction is a basic principle of physics that explains how a changing magnetic field can generate an electric current.

The law was first discovered by English scientist Michael Faraday in 1831.

Faraday's law states that the magnitude of the induced electric current is proportional to the rate of change of the magnetic flux through the area.

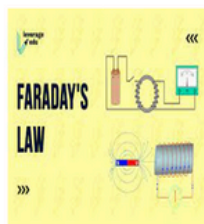The greater the change in magnetic flux, the greater the induced current. The direction of the current is determined by the direction of the change in flux.



LENZ'S LAW

An induced Current always flows in a direction such that it opposes the change which produced it.

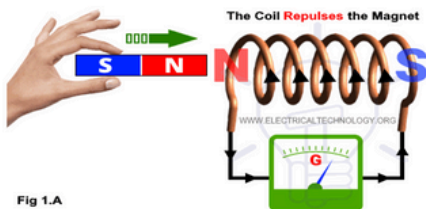


Fig 1.A

When the "N" Pole of the magnet is moved towards the coil, end of the coil becomes "N" Pole.

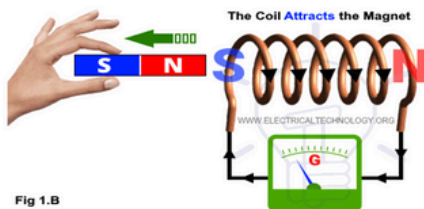


Fig 1.B

When the "N" Poles of the magnet is moved away from the coil, end of the coil becomes "S" Pole.

The Lenz's law states that when an E.M.F is induced in a circuit, the current setup always opposes the motion, or change in current, which produces it. OR

An induced EMF will cause a current to flow in a close circuit in such a direction that its magnetic effect will oppose the change that produced it.



When both the bar magnet and coil is in static position, no current flowing or induced EMF (even the small amount of flux (N pole's of static magnet bar) linked to the coil movement), hence, no deflection in the galvanometer.

When the magnet bar moves quickly towards the coil, there is rapid deflection in the galvanometer for an instance. The deflection will remain constant until the continuous movement of the magnet bar with respect to the coil (i.e. relative moment between magnet bar and coil). If both the magnet bar and coil achieve the static position, the deflection of the galvanometer will be at Zero position (as shown in fig 1 A).


When the magnet bar is moved away from the coil, there will be again a deflection in the galvanometer until the relative movement between magnet bar and coil becomes at rest or static position. Keep in mind the direction of the galvanometer is in the opposite direction with the respect of fig 1A (as shown in fig 1 B).

The same happens (Step 2 & 3) if the magnet bar is in a static position while the coil moves towards or moves away from the static magnet bar


BASIC SINGLE COIL AC GENERATOR

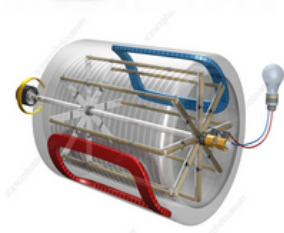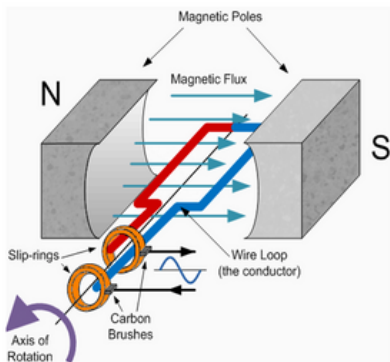

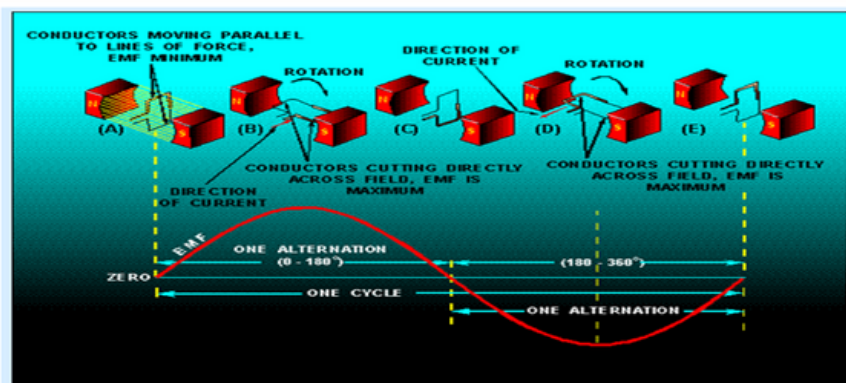1.2.2 Explain the AC waveforms produced by a simple alternating current generator (one loop in 2-pole magnet)



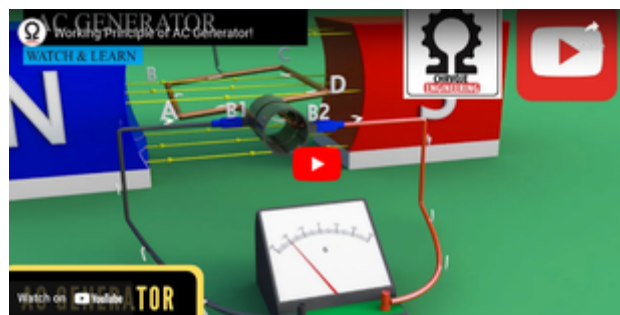When the coil rotating across the magnetic field in a constant angular velocity, an sinusoidal e.m.f will be produced



1.2.3 Express equation of a sinusoidal waveform

$$e = E_m \sin(\omega t + \theta)$$

$$e = E_m \sin(\omega t \pm \theta)$$



E_m = is the peak voltage @ current. (unit: **volt @ A**).

ω = is the **angular frequency** (unit: **radians per second; rads**)


The angular frequency is related to the physical frequency, (unit = **hertz**), which represents the number of cycles per second by the equation .

t = is the time (unit: **second**).

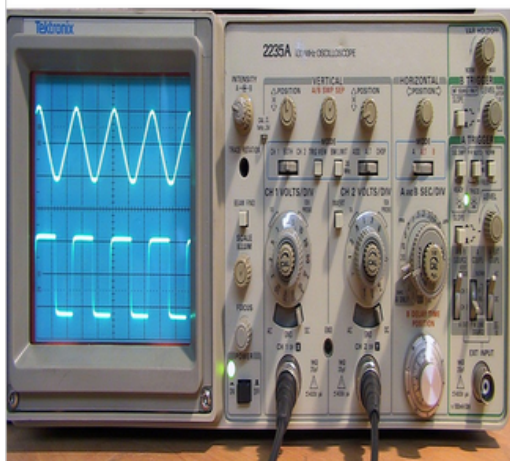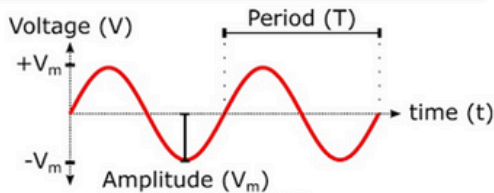θ = the phase, specifies where in its cycle the oscillation begin at $t = 0$.




Types of Periodic Waveform

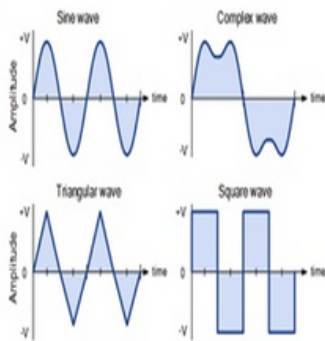




Peak Value / Amplitude

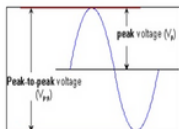- Peak voltage is the voltage measured from the baseline of an AC waveform to its maximum or peak level.
- Symbol V_p
- The peak value of a waveform is also called **amplitude**.



Amplitude or Peak Value = V_p

Peak To Peak Value

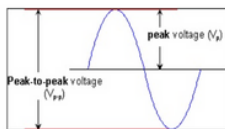

Peak to peak value = $2V_p @ 2E_m$



Period

- The time required for completing one full cycle.
- The symbol for period is **T**.
- Period is measured in units of seconds, **s**

$$T = \frac{1}{f} = \frac{1}{\omega/2\pi} = \frac{2\pi}{\omega}$$

Frequency

- The number of cycles that is completed one second
- The symbol for frequency is **f**
- Frequency is measured in units of cycles per second, or **Hertz, Hz**

$$f = \frac{1}{T}$$

or


$$f = \frac{\omega}{2\pi}$$



rms Value

- RMS voltage is the amount of dc voltage that is required for producing the same amount of power as the ac waveform. For a sine wave:
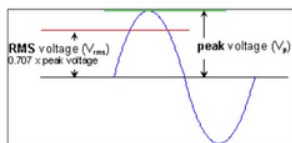
$$\begin{aligned} \text{rms value} &= \frac{1}{\sqrt{2}} \times \text{peak value} \\ &= 0.707 \text{ peak value} \end{aligned}$$



Average value

- The average or mean value of a symmetrical alternating quantity, (such as a sine wave), is the **average value** measured over a half cycle, (since over a complete cycle the average value is zero).
- For a sine wave:

$$\text{average value} = \frac{2}{\pi} \times \text{peak value}$$





Form factor

$$\text{form factor} = \frac{\text{rms value}}{\text{average value}}$$

- For a sine wave,

$$\text{form factor} = \frac{\text{rms value}}{\text{average value}} = \frac{0.707}{0.637} = 1.11$$

Peak factor

$$\text{peak factor} = \frac{\text{peak value}}{\text{rms value}} = \frac{\text{peak value}}{0.707 \text{ peak value}}$$


- For a sine wave,

$$\begin{aligned} \text{peak factor} &= \frac{\text{peak value}}{\text{rms value}} \\ &= \frac{\text{peak value}}{0.707 \text{ peak value}} = \frac{1}{0.707} = 1.414 \end{aligned}$$



Instantaneous value

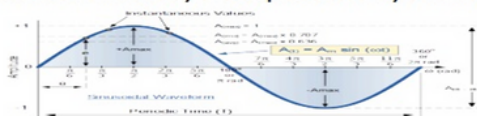- Instantaneous values are the values of the alternating quantities at any instant of time. They are represented by small letters, i , v , e , etc.



$$a = A_m \sin(\omega t \pm \theta)$$

Where

- a = amplitude (v, i, e, e.m.f)
- A_m = maximum amplitude @ peak amplitude
- ω = angular velocity
- θ = phase angle

SUMMARY

	FORMULA	UNIT
Frequency	$f = \frac{1}{T}$	Hz
Period	$T = \frac{1}{f}$	Sec
Amplitude	Vp @ Ip	Volt @ A
Peak to Peak value	2 x Vp @ 2 x Ip	Volt @ A
RMS value	0.707 x Vp @ 0.707 x Ip	Volt @ A
Average value	0.637 x Vp @ 0.637 x Ip	Volt @ A
Form Factor	$\frac{\text{RMS value}}{\text{Average value}} = 1.11$	-
Peak Factor	$\frac{\text{Peak value}}{\text{RMS value}} = 1.414$	-



EXAMPLE 1

» An alternating voltage is given by $v = 282.8 \sin 314t$ v. Find;

- The r.m.s voltage
- The frequency
- The instantaneous value of voltage when $t = 4\text{ms}$

Solution:

a) $V_{\text{rms}} = 0.707 \times V_p = 0.707 \times 282.8\text{V} = 200\text{V}$

b) $\omega = 314 \text{ rad/s} = 2\pi f$
 $f = 314 / 2\pi = 50\text{Hz}$

a) $v = 282.8 \sin (314 \times 4\text{ms}) = 282.8 \sin 1.256$
 $= 282.8 \sin 71.96^\circ = 268.9\text{V}$

EXAMPLE 2

» An alternating voltage is given by $v = 310 \sin 100\pi t + 30^\circ$. Determine;

- The amplitude
- The root mean square voltage
- The average voltage
- The instantaneous value of voltage when $t = 5\text{ms}$
- The time when the voltage first reach maximum value

Solution:

a) Amplitude = $V_p = 310\text{V}$



b) $V_{\text{rms}} = 0.707 \times V_p = 0.707 \times 310\text{V} = 219.17 \text{ v}$

c) $V_{\text{avg}} = 0.637 \times V_p = 0.637 \times 310\text{V} = 197.47 \text{ V}$

d) $V = 310 \sin [100 \pi \times 5\text{ms}] + 30^\circ$
 $= 310 \sin [1.571 + 30^\circ]$
 $= 310 \sin [90^\circ + 30^\circ]$
 $= 268.47 \text{ V}$

e) $310 = 310 \sin [100\pi t + 30^\circ]$
 $310 / 310 = \sin [100\pi t + 30^\circ]$
 $1 = \sin [100\pi t + 30^\circ]$
 $\sin^{-1} 1 = 100\pi t + 30^\circ$
 $90^\circ - 30^\circ = 100\pi t$
 $60^\circ = 100\pi t$
 $1.047 \text{ rad} = 100\pi t$
 so, $t = 1.047 \text{ rad} / 100\pi = 3.33\text{ms}$

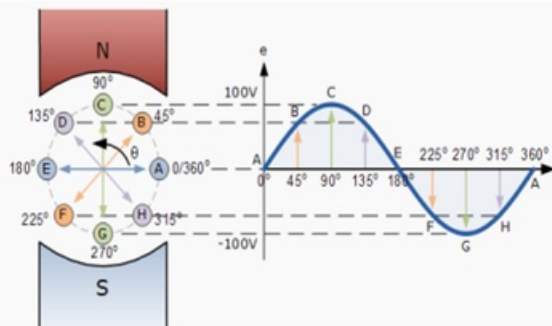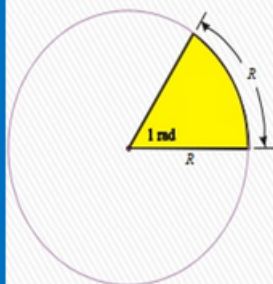
1.4.1 Show how to measure a sine wave in term of angle



- As angle A increases, the values of the trigonometric functions of A undergo a periodic cycle from 0, to a maximum of 1, down to a minimum of -1, and back to 0.

- If we now plot the sine of the angle measured in radians along the Cartesian coordinate system, we see that we again get the characteristic rise and fall.

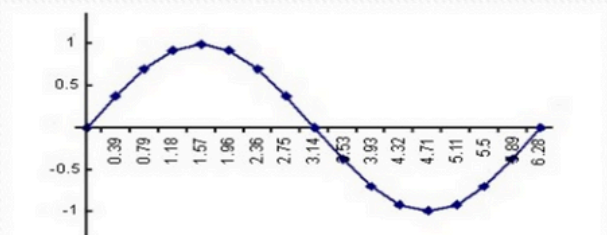- If you look closely at this graph you will see that the wave crosses the x-axis at multiples of 3.1416... – the value of pi. One full wave is completed at the value 6.2832..., or 2π , exactly the circumference of the unit circle.



1.4.2 Calculate the phase angle of a sine wave in

a. degree

b. radians

- There are 2π radians in one complete revolution and 360° in a revolution, the conversion between radians and degrees is given by:

$$\text{Radians} = \left(\frac{\pi}{180^\circ} \right) \times \text{degrees}$$

$$\text{Degrees} = \left(\frac{180^\circ}{\pi} \right) \times \text{radians}$$

EXERCISE



- (a) Convert the angle of 5.32 radians to degree unit
- (b) Convert the angle of 314° to radian unit



Give solution
to the above exercises




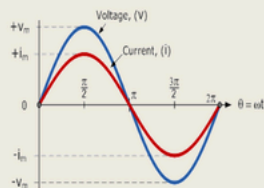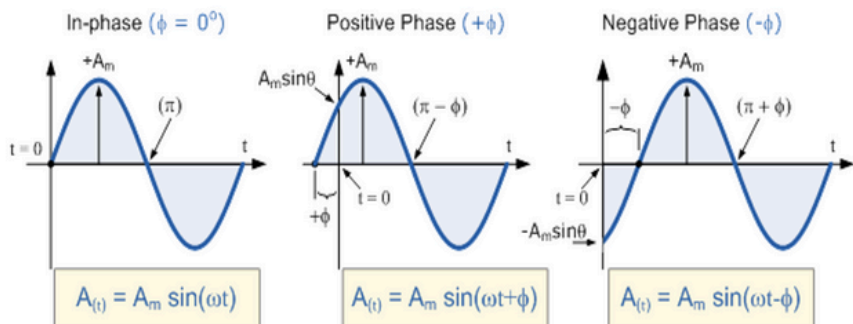1.5.1 Show how phasors are related to the sine wave formula



Two waveforms are said to be in phase when they have the same frequency

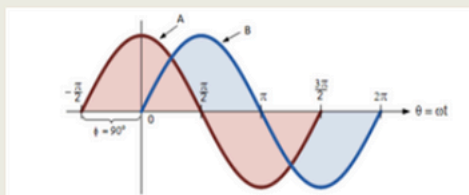
There is no phase difference between them.



A leading waveform is **one that is ahead of a reference waveform of the same frequency.**

A is ahead B
 \therefore A "LEADS" B

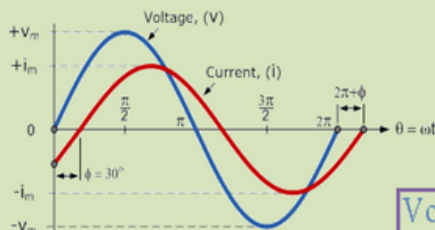A lagging waveform is **one that is behind a reference waveform of the same frequency.**
 B is behind A
 \therefore B "LAGS" A



The current, i is lagging the voltage, v by angle θ and in our example is 30°

$$\text{Voltage, } (v_t) = V_m \sin \omega t$$

$$\text{Current, } (i_t) = I_m \sin(\omega t - \theta)$$



EXERCISE

Q1 : What is the phase relationship between the sinusoidal waveforms of each of the following sets?

- $V = 10\sin(\omega t + 30^\circ)$
 $I = 5\sin(\omega t + 70^\circ)$
- $I = 15\sin(\omega t + 60^\circ)$
 $v = 10\sin(\omega t - 20^\circ)$







1.5.2 Draw a phasor diagram

Phasor is a scaled line whose length represents an AC quantity that has both magnitude ("peak amplitude") and direction ("phase") which is "frozen" at some point in time

A phasor is a vector that has an arrow head at one end which signifies partly the maximum value of the vector quantity (V or I) and partly the end of the vector that rotates

In the phasor diagram, everything is plotted on a coordinate system.

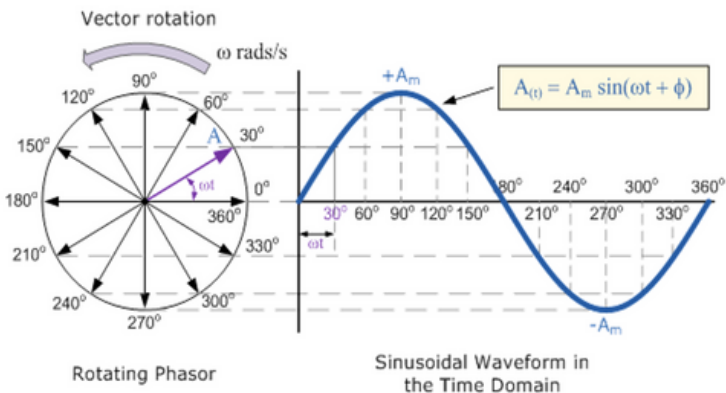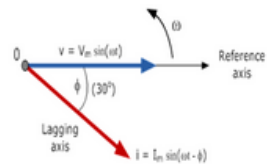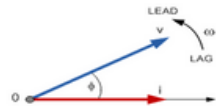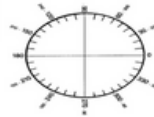Phasors are defined relative to the 'reference phasor' which is always chosen to point to the right.






- **The phasor diagram is drawn corresponding to time zero ($t = 0$) on the horizontal axis
- **The lengths of the phasors are proportional to the values of the voltage, (V) and the current, (I) at the instant in time that the phasor diagram is drawn.
- **The current phasor lags the voltage phasor by the angle, Φ , as the two phasors rotate in an *anticlockwise* direction as stated earlier, therefore the angle, Φ is also measured in the same anticlockwise direction.

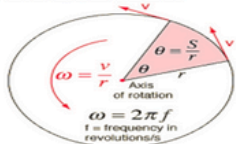1.5.3 Calculate Angular Velocity

Angular velocity

- Angular velocity can be considered to be a **vector quantity**, with direction along the axis of rotation in the right-hand rule sense.
- For an object rotating about an axis, every point on the object has the same angular velocity.
- The tangential velocity of any point is proportional to its distance from the axis of rotation. Angular velocity has the units rad/s.



$$v = \omega r \text{ or } \omega = \frac{v}{r}$$

EXAMPLE 1

A sinusoidal waveform is defined as $v = 169.8 \sin(377t)$ volts. Calculate the RMS voltage of the waveform, its frequency and the instantaneous value of the voltage after a time of 6ms.

SOLUTION EXAMPLE 1

Generally

$$a = A_m \sin(\omega t \pm \theta)$$

Then comparing this to our given expression for a sinusoidal waveform above of $v = 169.8 \sin(377t)$ volts;

$$A_m = V_p = 169.8V$$

$$\omega = 377$$

RMS voltage;

$$V_{rms} = 0.707 \times V_p = 0.707 \times 169.8 = 120 V$$

Frequency;

$$\text{Frequency, } f = \frac{\omega}{2\pi} = \frac{377}{2\pi} = 60\text{Hz}$$

SOLUTION EXAMPLE 1(CONT)

The instantaneous value of the voltage after a time of 6ms

Method 1: Using angle in radian for calculation.

Convert calculator mode to rad (radians)

$$\begin{aligned}v &= 169.8 \sin(377t) \\v &= 169.8 \sin(377 \times 6m) \\v &= 169.8 \sin(2.262) \\v &= 130.83 V\end{aligned}$$

The instantaneous value of the voltage after a time of 6ms

Method 2: Using angle in degree for calculation.


Convert $\omega = 377$ to degree

$$\omega = \frac{180^\circ}{\pi} \times 377 = 21600^\circ$$

$$\begin{aligned}v &= 169.8 \sin(21600t) \\v &= 169.8 \sin(21600 \times 6m) \\v &= 169.8 \sin(129.61) \\v &= 130.83 V\end{aligned}$$

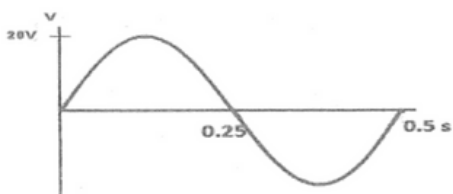EXAMPLE 2

Based on figure, write the sinusoidal waveform equation.



SOLUTION EXAMPLE 2

The sinusoidal waveform equation

Generally

$$a = A_m \sin(\omega t \pm \theta)$$

$$A_m = \text{peak value} = V_p = 20$$

$$\omega = \frac{2\pi}{T} = \frac{2\pi}{0.5} = 12.57$$

$$\theta = 0^\circ$$


$$\therefore v = 20 \sin(12.57t)$$

EXAMPLE 3


Given $V_1 = 15 \sin(\omega t + 70^\circ)$ and $V_2 = 20 \sin(\omega t - 10^\circ)$. By using phasor diagram, state which sinusoid is leading and the phase difference.

SOLUTION EXAMPLE 3

- V_1 leads V_2 by 80°

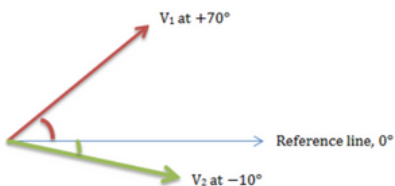

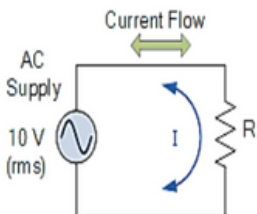1.6.1 Apply Ohm's Law to resistive circuits with AC sources




Resistors are "passive" device and do not produce or consume any electrical energy, but convert electrical energy into heat.

In DC circuits the linear ratio of voltage to current in a resistor is called its resistance.

However, in AC circuits this ratio of voltage to current depends upon the frequency and phase difference or phase angle (Φ) of the supply.

So when using resistors in AC circuits the term Impedance, symbol Z is the generally used and we can say that DC resistance = AC impedance, $R = Z$.

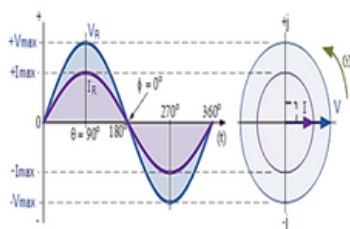V-I Phase Relationship and Vector Diagram



For resistors in AC circuits the direction of the current flowing through them **has no effect on the behavior of the resistor** so will rise and fall as the voltage rises and falls.

The current and voltage reach maximum, fall through zero and reach minimum at exactly the same time. - "in-phase"

At any point along the horizontal axis that the instantaneous voltage and current are in-phase because the current and the voltage reach their maximum values at the same time, that is their phase angle θ is 0° .

- The instantaneous voltage across the resistor, V_R is equal to the supply voltage, V_c and is given as:


$$V_R = V_{max} \sin(\omega t)$$

- The instantaneous current flowing in the resistor will therefore be:

$$I_R = \frac{V_R}{R} = \left(\frac{V_{max}}{R}\right) \sin(\omega t) = I_{max} \sin(\omega t)$$

- As the voltage across a resistor is given as $V_R = I_R R$, the instantaneous voltage across the resistor above can also be given as:

$$V_R = I_{max} R \sin(\omega t)$$

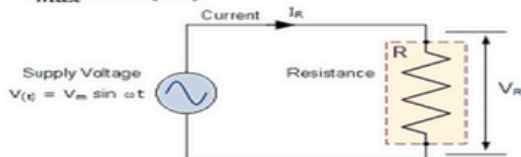


1.6.2 Apply Kirchhoff's Voltage Law and Current Law to resistive circuits with AC sources


- » Kirchhoff's Voltage and Current Laws apply to all AC circuits as well as DC circuits.

Kirchhoff's Current Law:

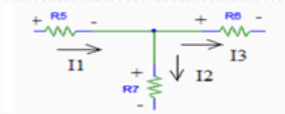- The sum of current into a junction equals the sum of current out of the junction.
- $i_2 + i_3 = i_1 + i_4$
- The sum of all currents at a node must equal to zero.




$$I_1 - I_2 - I_3 = 0.$$

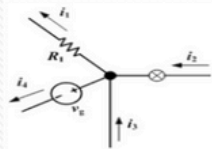

A diagram of Kirchhoff's Current Law.

Kirchhoff's Voltage Law:

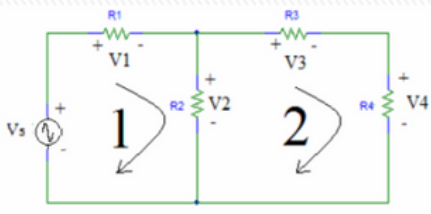- The algebraic sum of the voltage (potential) differences in any loop must equal zero.
- Example:



$$V_1 + V_2 - V_s = 0$$


1.6.3 Apply Kirchhoff's Voltage Law and Current Law to resistive circuits with AC sources

- In a direct current circuit the power is equal to the voltage times the current, or $P = E \times I$.
- The **TRUE POWER** depends upon the phase angle between the current and voltage.
- True power of a circuit is the power actually used in the circuit.
- Measured in watts.

$$P = \text{true power} \quad P = I^2 R \quad P = \frac{E^2}{R}$$

*Measured in units of **Watts***

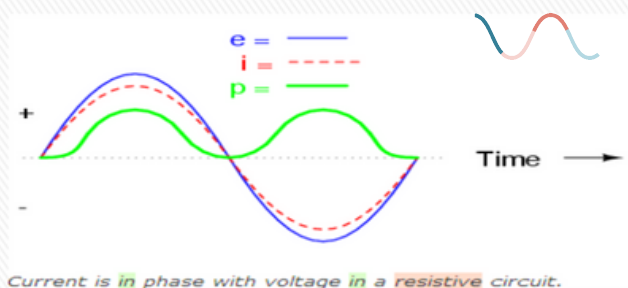- Note that the waveform for power is always positive, never negative for this resistive circuit.
- This means that power is always being dissipated by the resistive load, and never returned to the source as it is with reactive loads.





END OF CHAPTER

01

List TWO(2) methods of generating alternating current

ANSWER

- Permanent Magnet Moving Coil (PMMC)
- Permanent Coil Moving Magnet(PCMM)

02

Explain THREE (3) reasons why AC is preferred over DC.

ANSWER

- i. Power plants use rotary turbines as their source of output, which are by nature AC and don't need power electronics to convert to DC.
- ii. Changing the voltage of AC electricity for distribution and transmission is far simpler.
- iii. Compared to DC transmission, the cost of plant related to AC transmission (transformers, circuit breakers, etc.) is substantially lower.
- iv. There are a few technical benefits to AC transmission. Large fault currents happen when there is a network fault.
- v. Metering AC connections and keeping an eye on power flows over a network is also simpler.

***Choose any 3 answers*

03

Explain TWO (2) laws related to generating alternating current.
[4 marks]

ANSWER

- ✓ Faraday's Law states that, a coil of wire will produce a voltage (emf) in response to any changes in its magnetic surroundings.
- ✓ Lenz's Law states that the current configuration in a circuit always opposes the motion, or change in current, that induces an E.M.F.

04


Convert from AC voltage equation to AC voltage waveform for:

i. $V = 20 \sin(\omega t + \pi/2)$ volt


ii. $V = 12 \sin(\omega t - \pi/2)$ volt

ANSWER

i. $V = 20 \sin(\omega t + \pi/2)$ volt

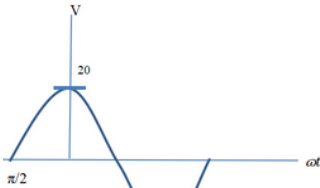

ii. $V = 12 \sin(\omega t - \pi/2)$ volt

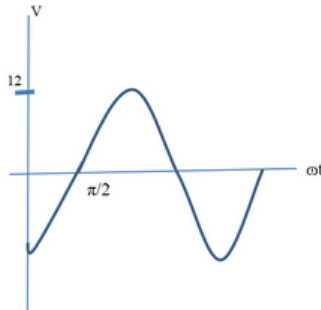

(a) An Alternating Voltage equation is given by V . Calculate the value of amplitude, frequency, phase angle in degree and the the voltage when $t=5.5\text{ms}$

ANSWER

The amplitude, $V_p = 215\text{V}$

The frequency $\omega = 100\pi \text{ rad/s}$

$$2\pi f = 100\pi$$

$$f = \frac{100\pi}{2\pi} = 50\text{Hz}$$

phase angle in degree

$$0.25 \times \frac{360}{2\pi} = 14.32^\circ$$

The value of voltage when $t=5.5\text{ms}$

$$V = 215 \sin(100\pi t + 0.25)A$$

$$V = 215 \sin(100\pi(5.5\text{m}) + 0.25)A$$

$$= 215 \sin(99^\circ + 14.32^\circ)$$

$$= 215 \sin(113.32^\circ)$$

$$= 197.43\text{v}$$

EXERCISE



1

Determine the rms voltage of the 14V peak to peak voltage.

Answer : 4.95V



2

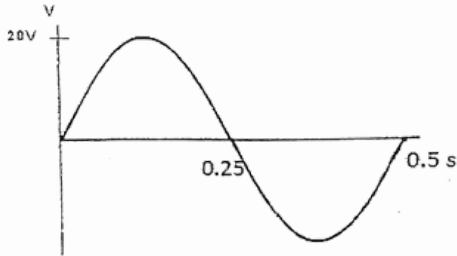


Figure 2a

Referring to figure 2a,

- Give the definition of time period, T of a sinusoidal waveform
- Find the value of time period
- State the peak voltage
- Write the sinusoidal equation

Answer : $T = 0.5s$, $V_p = 20V$, $V = 20 \sin 12.57t$


3

An alternating voltage is given by $V(t) = 282.8 \sin 314t$ Volt. Find:

- Average Voltage
- Frequency
- The instantaneous voltage value when $t = 4ms$

Answer : $V_{avg} = 180.14V$, $f = 49.97 \text{ Hz}$, $V(t = 4ms) = 268.9V$

4

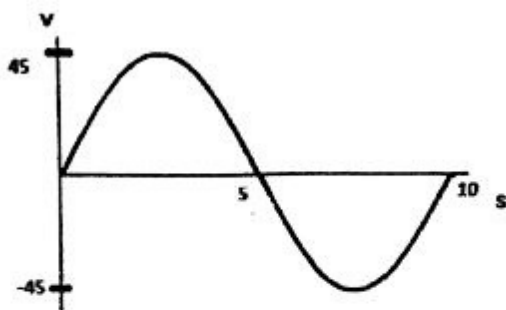

Based on the above figure calculate peak to peak voltage, root mean square voltage, average voltage and write the sinusoidal equation

Answer : $V_{pp} = 90V$, $V_{rms} = 31.815V$, $V_{avg} = 28.66V$,
 $V = 45 \sin 0.628t$

5

The current in AC circuit at any time t seconds is given by $i = 20 \sin(60\pi t + 0.38) A$. Calculate

- The period time and frequency
- The value of current when $t = 0$

Answer: $T = 0.033s$, $f = 30Hz$, $i = 7.42A$

6

- An alternating voltage is given by $V = 15 \sin (314t - 0.52) \text{mA}$. Determine
- The amplitude
 - The peak to peak value
 - The periodic time
 - The phase angle in degree

Answer : $V_p = 15 \text{mV}$, $V_{pp} = 30 \text{mV}$, $T = 20 \text{ms}$, 29.8

7



Based on the figure 7a, find:

- The total current in the circuit
- Voltage drop across R
- True power of the circuit

Answer : $I = 2 \text{A}$, $V = 120$, $P = 240 \text{W}$

8

Calculate the current and power consumed in a single phase 240V AC circuit by a heating element which has an impedance of 60 ohm. Also draw the corresponding phasor diagram

Answer: $I = 4 \text{A}$, $P = 960 \text{W}$






TOPIC 2
SINUSOIDAL STEADY-STATE
CIRCUIT ANALYSIS





Purely Resistive Circuit with AC Source

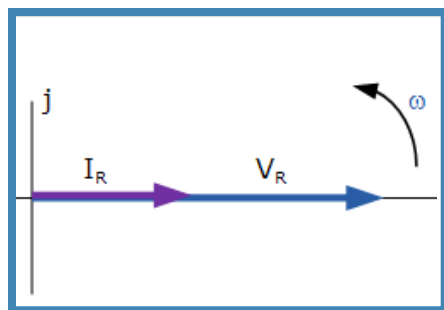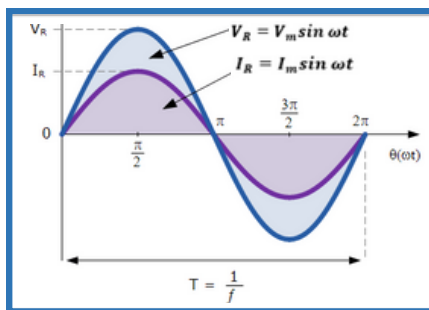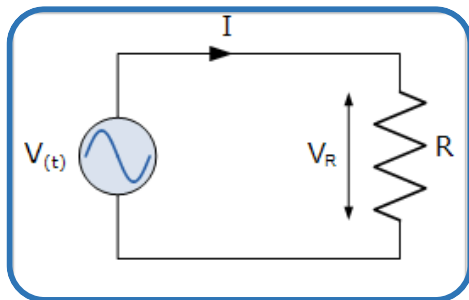In a purely resistive AC circuit, the voltage and current are in phase, meaning the phase angle difference between them is zero. This can be understood by examining the relationship between voltage and current in a resistor and the behaviour of sinusoidal waveforms, as shown in Figure below.



Sinusoidal waveform showing V_R is in phase with I_R :

$$V_R = V_m \sin \omega t$$

$$I_R = I_m \sin \omega t$$

Phasor diagram: V_R is in phase with I_R . (Phase angle = 0°)

$$V_R = V_m \angle 0^\circ$$

$$I_R = I_m \angle 0^\circ$$

- In the resistive circuit, current, voltage, and voltage source are the sine waves.
- The phase angle is 0 degrees.
- The frequency does not affect the Resistance, R.
- Whether the frequency rises or falls, R never changes.
- Ohm's law is used to solve resistors in AC circuits:

$$V_R = I \times R$$

Example 1

A circuit with 50 Ohms resistance is connected across an AC supply with a 230 Vrms voltage. Calculate the total current and the voltage drop across the resistance. Draw the corresponding phasor diagram, showing the voltage and current phase relationship.

Solution

i. Total current:

$$I = \frac{V}{R} = \frac{230}{50} = 4.6 \text{ A}$$

ii. Voltage drop across the resistance:

$$V_R = I \times R = 4.6 \times 50 = 230 \text{ V}$$

iii. Since a resistive component ($\theta = 0$) has no phase difference, the appropriate phasor diagram is as follows:



Example 2

$V(t) = 100\sin(\omega t + 30^\circ)$ is the equation for a sinusoidal voltage source that is connected to a 50 Ohms resistance. Calculate the peak current and draw the phasor diagram.


Solution

$$V_{R(t)} = 100\sin(\omega t + 30^\circ) \longrightarrow V_R = 100\angle 30^\circ \text{ V}$$

By using Ohm's Law




$$I_R = \frac{V_R}{R} = \frac{100\angle 30^\circ}{50} = 2\angle 30^\circ \text{ A}$$

The phasor diagram:

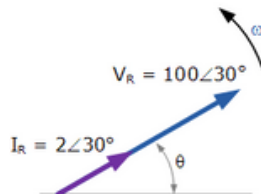

Pure Inductive Circuit with AC Source

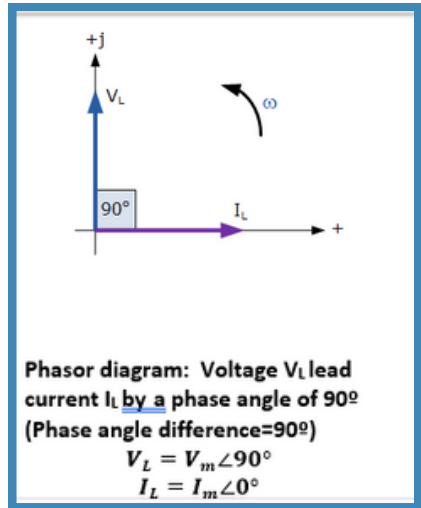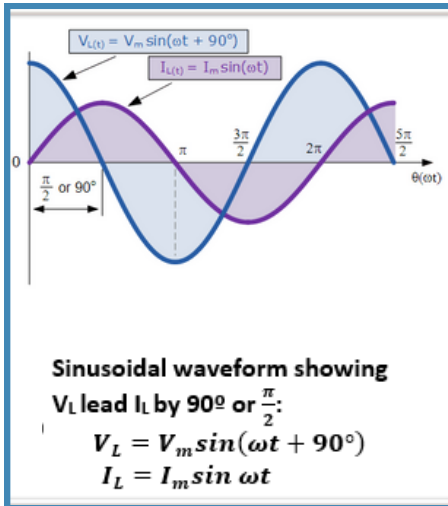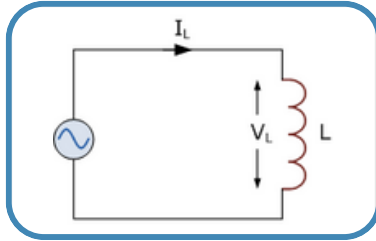The current fluctuates against an inductor. An AC voltage placed across an inductor causes it to produce a reverse electromotive force, or EMF, which opposes the change in current.




Inductive Reactance

- Inductive reactance, represented by the symbol X_L , is the resistance of an inductive circuit with unit ohm.
- The inductive reactance X_L rises in proportion to the frequency across it.
- As a result, inductive reactance and frequency are directly proportional, and the formula yields X_L .
- Since $\omega = 2\pi f$, then inductive reactance will be $X_L = \omega L$.
- The relationship between an inductor's voltage and current is expressed using a formula similar to Ohm's law:

$$V_L = I_L \times X_L$$

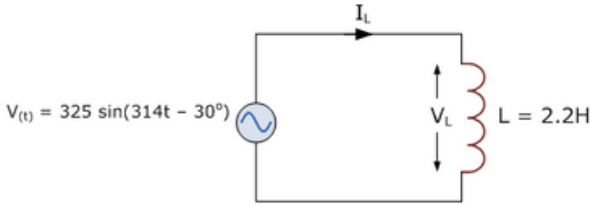Example 1

By referring to circuit below, $V(t) = 325\sin(314t - 30^\circ)$ and $L = 2.2\text{H}$. Draw the phasor diagram and calculate the rms current at the coil.



Solution

The supply voltage will give the coil's rms voltage. If the peak voltage is 325V, and the equivalent rms value is 230V. We get $V_L = 230 \angle -30^\circ$.


Inductive reactance:

$$X_L = \omega L = 314 \times 2.2 = 690\Omega.$$

The current I_L :

$$I_L = \frac{V_L}{jX_L} = \frac{230 \angle -30^\circ}{690 \angle 90^\circ} = 0.33 \text{ A} \angle -120^\circ$$



Phasor diagram

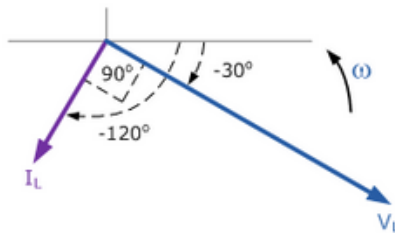

Pure Capacitive Circuit with AC Source


In a purely capacitive AC circuit, the current leads the voltage by 90 degrees ($\pi/2$ radians). This phase relationship and the concept of capacitive reactance can be understood by examining the behavior of a capacitor in an AC circuit and the mathematical relationships that describe this behavior.

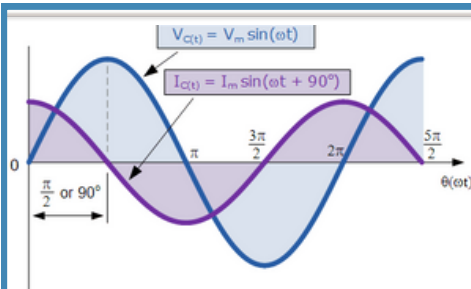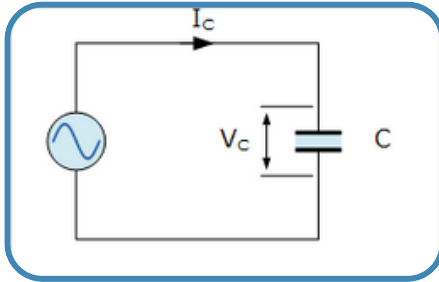A capacitor stores energy in an electric field created by a voltage across its plates. When an AC voltage is applied, the voltage across the capacitor changes over time, causing a time-varying current to flow as the capacitor charges and discharges.



Sinusoidal waveform showing I_C lead V_C by 90° or $\frac{\pi}{2}$:
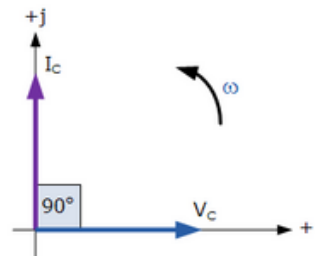
$$I_C = I_m \sin(\omega t + 90^\circ)$$
$$V_C = V_m \sin \omega t$$



**Phasor diagram: I_C leads V_C by 90° or $\frac{\pi}{2}$:
(Phase angle = 90°)**

$$I_C = I_m \angle 90^\circ$$
$$V_C = V_m \angle 0^\circ$$

Capacitive Reactance

- In circuits that are exclusively capacitive, capacitive reactance inhibits the passage of current.
- Capacitive reactance is denoted by the letter X_C . We use the ohm as its unit.
- As the frequency across it rises, the capacitor's X_C decreases.
- Thus, the frequency and capacitive reactance have an inverse relationship.
- The formula yields X_C as follows:

$$X_C = 1/2\pi fC \Omega$$


Given that ω (the angular frequency) equals $2\pi f$,

- The equation that relates a capacitor's voltage and current is comparable to Ohm's law:

$$V_C = I_C \times X_C$$

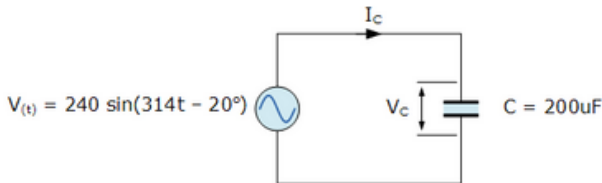Example 1

An ac supply voltage $V(t) = 240 \sin(314t - 20^\circ)$ is connected in series with a $200\mu\text{F}$ capacitance. Calculate the current following the capacitor and draw a phasor diagram.



Solution


$$V_C = 240 \angle -20^\circ \text{ V.}$$

Reactance capacitance:




$$X_C = \frac{1}{\omega C} = \frac{1}{314(200\mu)} = 16 \angle -90^\circ \Omega$$

$$I_C = \frac{V_C}{jX_C} = \frac{240 \angle -20^\circ}{16 \angle -90^\circ} = 15 \angle 70^\circ \text{ A}$$

Phasor diagram:

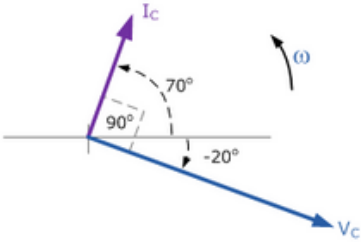

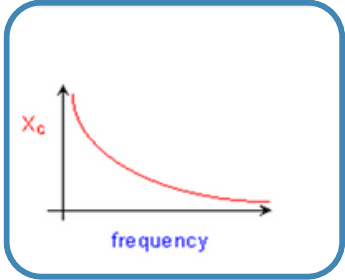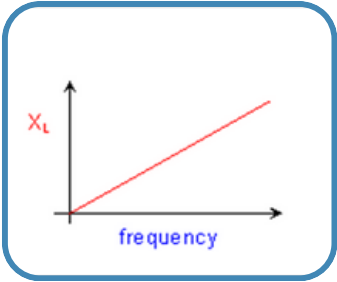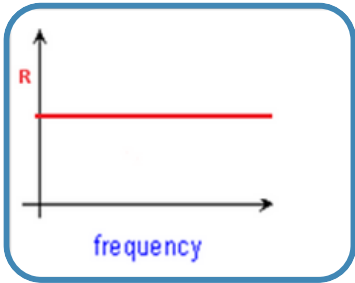A graph illustrating the frequency-related relationship between R, X_L , and X_C



List of differences between resistance and impedance


Aspect	Resistance	Impedance
Nature of Opposition	Opposition to direct current (DC).	Opposition to alternating current (AC).
Components	Only resistance (R).	Combination of resistance (R) and reactance (X).
Frequency Dependence	Independent of frequency.	Dependent on frequency.
Reactance	No reactance.	Includes reactance (capacitive X_C and inductive X_L).
Phase Relationship	Voltage and current are in phase.	Voltage and current can be out of phase.
Mathematical Representation	Represented as R.	Represented as a complex number $Z=R+jX$.
Power Dissipation	$P= I^2R$	$P= I^2Z\cos\theta$ or $P=IV\cos\theta$
Calculation	$R=V/I$ for DC circuits.	$Z=V/I$ for AC circuits (complex quantities).

Impedance Triangle

Z is the impedance in AC circuits.

$$\text{Impedance} = \frac{\text{Voltage}}{\text{current}}$$

$$Z = \frac{V}{I}$$

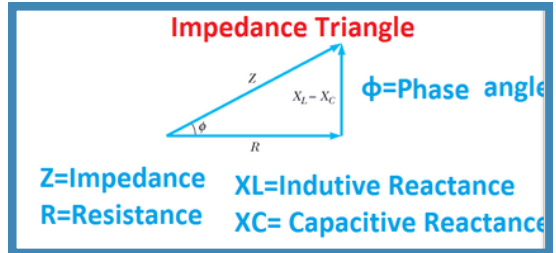

In general, the impedance triangle can be used to calculate the impedance, Z.

If $X_L > X_C$, the impedance become:

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

If $X_C > X_L$, the impedance become:


$$Z = \sqrt{R^2 + (X_C - X_L)^2}$$



Inductive and capacitive load in a series circuit

In series circuit, current is used as a reference.

R-L series

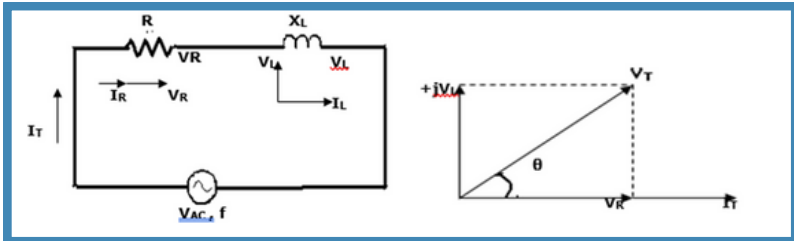


- The current and all of the voltage drops in an RL circuit are sinusoidal waves.
- The source voltage (V_T) in an RL circuit always leads to the total current (I_T).
- V_R and I_T are in phase or zero phase angle.
- V_L leads I_T by 90° .
- The impedance of an RL circuit is the total resistance to the flow of AC current.
- An RL circuit's total impedance (Z_T) can be calculated using this equation:

$$Z = \sqrt{X_L^2 + R^2}$$

or in complex form:

$$Z = R + jX_L$$

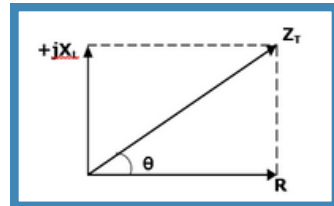

The total voltage:

$$V_T = \sqrt{V_R^2 + V_L^2}$$

or in complex form:

$$V_T = V_R + jV_L$$

Where:

V_T = total voltage

V_R = voltage across resistor R

V_L = voltage across inductor L

The total phase angle:

$$\theta = \tan^{-1}\left(\frac{X_L}{R}\right)$$

or

$$\theta = \tan^{-1}\left(\frac{V_L}{V_R}\right)$$

RL Series Circuit Analysis:

1) Inductive reactance: $X_L = 2\pi fL$

2) Total impedance: $Z = \sqrt{R^2 + X_L^2}$
or in complex form, $Z = R + jX_L$

3) The total current:

$$I_T = \frac{V_T}{Z_T}$$

4) $I_T = I_L = I_R$ (current is the same in a series circuit)

5) The voltages across R and L:

$$V_R = I_T \times R \quad \text{and} \quad V_L = I_T \times X_L$$

6) The phase angles for R and L.


$$\theta_R = 0^\circ \quad \theta_L = 90^\circ$$

7) The total phase angle for the circuit:

$$\theta_T = \tan^{-1}\left(\frac{X_L}{R}\right)$$

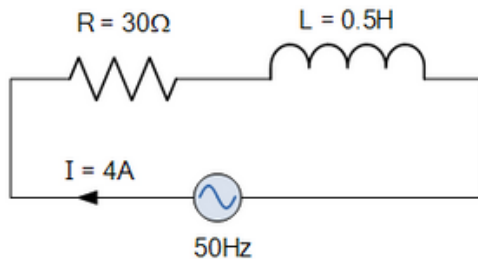Example

A coil has a resistance of 30Ω and an inductance of 0.5H . What will be the supply's rms value if the coil is receiving 4 amps of current and the supply voltage has a frequency of 50 Hz?



Solution

The circuit's impedance will be:

$$X_L = 2\pi fL = 2\pi(50)(0.5) = 157$$

$$Z = R + jX_L$$

$$Z = 30 + j157$$

$$Z = 159.84\angle 79.18^\circ \Omega$$

Next, each component's voltage drop across is computed as follows:

$$V_R = I(R) = 4(30) = 120 \text{ V}$$


$$V_L = I(X_L) = 4(j157) = j628 \text{ V}$$

$$V_T = V_R + jV_L = 120 + j628 = 639.36\angle 79.18^\circ \text{ V}$$


or

$$V_S = I(Z) = 4(159.84\angle 79.18^\circ) = 639.36\angle 79.18^\circ \text{ V}$$

There will be a phasor diagram. .

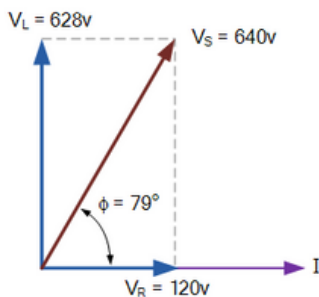

R-C Series Circuit

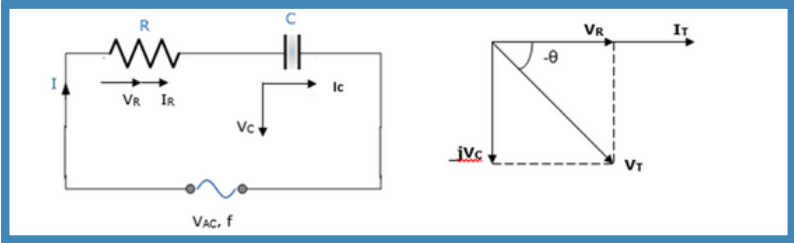


- In an RC circuit, I_T leads V_T by 90° or V_C lags the I_T by 90° .
- The V_R is in phase with the I_T .
- The impedance (Z) of an RC circuit is the total opposition to AC current flow.
- The equation for the total impedance (Z_T) of an RC circuit is:

complex form:

$$Z = \sqrt{R^2 + X_C^2}$$

or

$$Z = R - jX_C$$

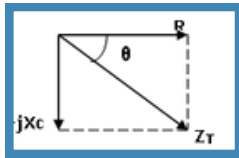

- The total voltage:

complex form:

$$V_T = \sqrt{V_R^2 + V_C^2}$$

or

$$V_T = V_R - jV_C$$

Where:

V_T = total voltage

V_R = voltage across resistor R

V_C = voltage across capacitor C

The total phase angle:

$$\theta = -\tan^{-1}\left(\frac{X_C}{R}\right)$$

or

$$\theta = -\tan^{-1}\frac{V_C}{V_R}$$

RC Series Circuit Analysis:

1) Capacitive Reactance, X_C : $X_C = \frac{1}{2\pi fC} \Omega$

2) Impedance:

$$Z = \sqrt{R^2 + X_C^2} \text{ or in complex form } Z = R - jX_C$$

3) The circuit's current:

$$I_T = \frac{V_T}{Z_T}$$

4) The currents at R and C:

$$I_T = I_C = I_R$$

5) The voltages across R and C:

$$V_R = I_T \times R \quad \text{and} \quad V_C = I_T \times X_C$$

6) The phase angles for R and C.


$$\theta_R = 0^\circ \quad \text{and} \quad \theta_C = -90^\circ$$

7) The total phase angle for the RC circuit:

$$\theta_T = -\tan^{-1}\left(\frac{X_C}{R}\right) \quad \text{or} \quad \theta = -\tan^{-1}\frac{V_C}{V_R}$$

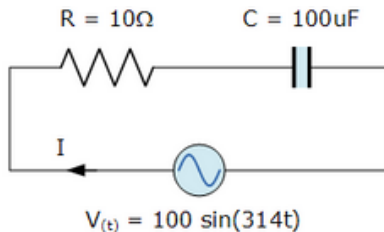Example

$V(t) = 100 \sin(314t)$ is the source voltage connected to a 100 μ F capacitor with 10 Ω an internal resistance. Calculate the maximum current flowing into the capacitor at any instantaneous time. Draw a voltage triangle as well, showing each individual voltage drop.



Solution

The circuit impedance and reactance capacitance are computed as follows:

$$I = \frac{V_C}{Z} = \frac{100\angle 0^\circ}{33.38\angle -72.57^\circ} = 3\angle 72.57^\circ A$$

$$X_C = \frac{1}{\omega C} = \frac{1}{314(100\mu)} = 31.85\angle -90^\circ \Omega$$

$$Z = R - jX_C = 10 - j31.85 = 33.38\angle -72.57^\circ \Omega$$

$$Z = \sqrt{R^2 + X_C^2} = \sqrt{10^2 + 31.85^2} = 33.4\Omega$$

Next, the maximum current following the circuit:

$$I = \frac{V_C}{Z} = \frac{100\angle 0^\circ}{33.38\angle -72.57^\circ} = 3\angle 72.57^\circ A$$

$$I = \frac{V_C}{Z} = \frac{100\angle 0^\circ}{33.38\angle -72.57^\circ} = 3\angle 72.57^\circ A$$


Next, the circuit's individual voltage drops are computed as follows:

$$V_R = I(R) = 3(10) = 30 V$$

$$V_C = I(X_C) = 3(31.85\angle -90^\circ) = 95.55\angle -90^\circ V$$

$$V_T = V_R - jV_C = 30 - j95.55 = 100\angle -72.57^\circ V$$

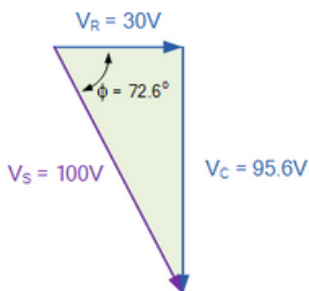The voltage triangle that results for the computed peak values is then as follows:



RLC Series Circuit


The phase relationships for RLC will change significantly if an AC supply with a sinusoidal waveform is connected to them. The voltage and current are "in-phase" when using a resistor. In an inductance, the voltage "leads" the current by 90° (ELI), while in a capacitance, the voltage "lags" the current by 90° (ICE).

The phase difference depends on how reactive the components are. It is well known that reactance (X) is negative in capacitive elements, positive in inductive components, and zero in resistive elements. The following impedance values can be obtained from these values:

$$Z_R = R = R\angle 0^\circ$$

$$Z_L = j\omega L = \omega L\angle 90^\circ$$
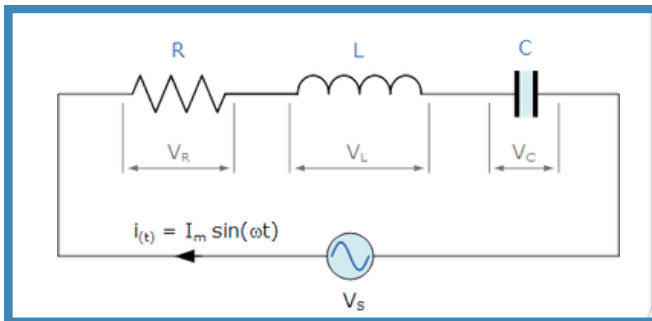
$$Z_C = \frac{1}{j\omega C} = \frac{1}{\omega C}\angle -90^\circ$$



RLC Series Circuit Analysis:

1) Find X_C and X_L :

$$X_C = 1 / (2\pi fC) \text{ and } X_L = 2\pi fL$$

2) Impedance:

$$Z_T = R + jX_L - jX_C$$

3) Total current:

$$I_T = V_T / Z_T$$

4) The currents through R, L and C. Since this is a series circuit:

$$I_T = I_C = I_L = I_R$$

5) The voltages across R, L and C:

$$V_R = I_T \times R, \quad V_C = I_T \times X_C \text{ and } V_L = I_T \times X_L$$

6) Show that the total voltage in a series circuit is equal to the sum of the vectors of voltages across R, L, and C's components.


$$V_T = V_R + jV_L - jV_C$$

7) The total phase angle for the R-L-C series circuit:

$$\theta_T = -\tan^{-1}(X_C - X_L / R) \text{ if } X_C > X_L$$


$$\theta_T = \tan^{-1}(X_L - X_C / R) \text{ if } X_L > X_C$$

The R-L-C series phasor

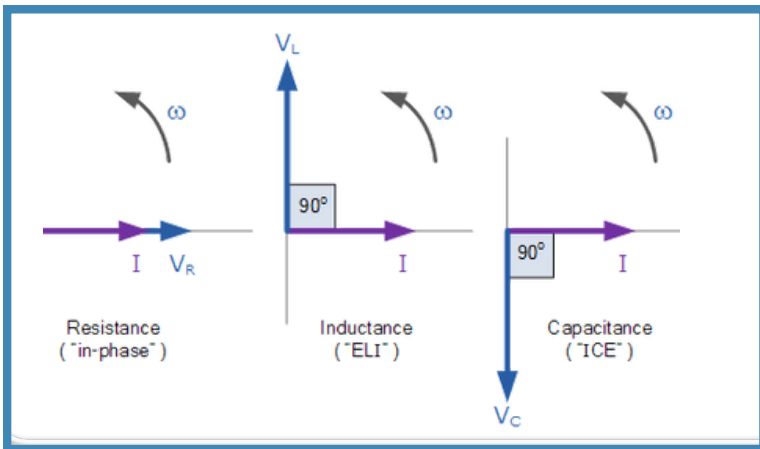

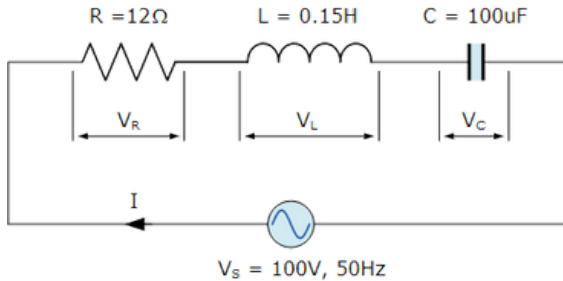Example

An RLC series circuit with a $12\ \Omega$ resistance, 0.15H inductance, and a $100\mu\text{F}$ capacitor is connected in series across a 100V , 50Hz supply. Calculate the voltage phasor diagram, total impedance, and current in the circuit.



Solution

Calculate X_L .

$$X_L = 2\pi fL = 2\pi \times 50 \times 0.15 = 47.13\ \Omega$$

Calculate X_C .

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}} = 31.83\ \Omega$$

Calculate, Z .

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{12^2 + (47.13 - 31.83)^2}$$

$$Z = \sqrt{144 + 234} = 19.4\ \Omega$$

Total current, I.

$$I = \frac{V_S}{Z} = \frac{100}{19.4} = 5.14 \text{ Amps}$$


The voltages of V_R , V_L , V_C .

$$V_R = I \times R = 5.14 \times 12 = 61.7 \text{ volts}$$

$$V_L = I \times X_L = 5.14 \times 47.13 = 242.2 \text{ volts}$$

$$V_C = I \times X_C = 5.14 \times 31.8 = 163.5 \text{ volts}$$


The Phasor Diagram.

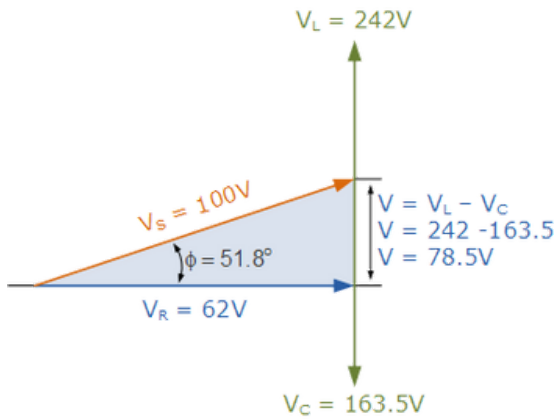

RL Parallel Circuit

In parallel circuit, voltage is used as a reference.

R-L parallel Circuit

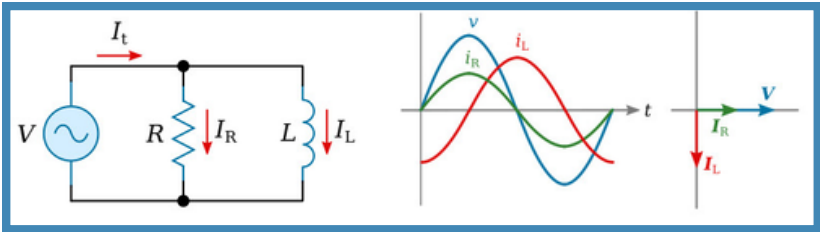

Parallel RL Circuit Analysis:

1) Inductive Reactance, X_L :

$$X_L = 2\pi fL \text{ or } j\omega L$$

2) The voltages for R and L

$$V_T = V_L = V_R$$

3) The current for R and L:

$$I_R = V_T / R \quad \text{and} \quad I_L = V_T / X_L$$

4) The total current:

$$I_T = \sqrt{I_R^2 + I_L^2} \text{ or in complex form: } I_T = I_R - jI_L$$

5) Impedance:

$$Z_T = V_T / I_T$$

6) Phase angles for R and L.

$$\theta_R = 0^\circ \text{ and } \theta_L = -90^\circ$$

7) Total phase angle:

$$\theta_T = -\tan^{-1}(I_L / I_R)$$

8) Impedance:

$$Z_T = \frac{R \times X_L}{R + X_L} \quad \text{or} \quad \frac{1}{Z_T} = \frac{1}{R} + \frac{1}{X_L}$$

Example

Calculate the phase angle, Z_t , I_t , I_R , and I_L in a parallel RL circuit with a 10 V source operating at 4 kHz, a 1.4 mH coil, and a 25 Ω resistor.

Solution


$$X_L = 2\pi fL = 2\pi(4k)(1.4m) = 35.17\Omega$$

$$I_R = \frac{V}{R} = \frac{10}{25} = 0.4A$$

$$I_L = \frac{V}{X_L} = \frac{10}{j35.17} = -j0.284A$$

$$I_T = I_R + I_L = 0.4 - j0.284 = 0.491\angle -35.4^\circ A$$

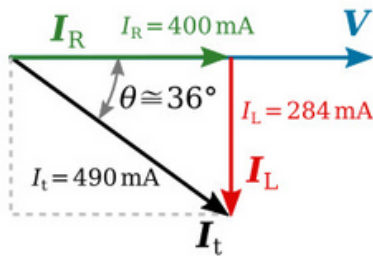
$$Z_T = \frac{V}{I_T} = \frac{10\angle 0^\circ}{0.491\angle -35.4^\circ} = 20.37\angle 35.4^\circ\Omega$$




RC Parallel Circuit

Parallel RC circuits are similar to parallel RL circuits in that they can be solved similarly. Below is an example of a parallel resistor circuit.

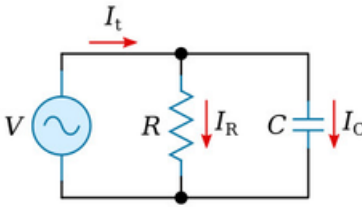Here is an illustration of the circuit conditions showing a diagram. The total current needs to be determined using phasor addition because the phasors I_R and I_C are currently out of phase. When addressing an RC circuit, the same steps are taken as when addressing an LR circuit.



Parallel RC Circuit.

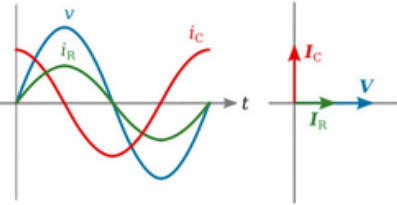

Waveforms and phasors.

RC Parallel Circuit Analysis:

1) Capacitive Reactance, X_C :

$$X_C = 1/(2\pi fC)$$

2) The voltages for R and L:

$$V_T = V_C = V_R$$

3) The currents for R and L:

$$I_R = V_T / R \text{ and } I_C = V_T / X_C$$

4) Total current:

$$I_T = \sqrt{I_R^2 + I_C^2} \text{ or in complex form: } I_T = I_R + jI_C$$

5) Impedance:

$$Z_T = V_T / I_T$$

6) Phase angles for R and L:

$$\theta_R = 0^\circ \text{ and } \theta_C = 90^\circ$$

7) Total phase angle:


$$\theta_T = \tan^{-1}(I_C/I_R)$$

8) Impedance:

$$Z_T = \frac{R \times X_C}{R + X_C} \Omega \quad \text{or} \quad \frac{1}{Z_T} = \frac{1}{R} + \frac{1}{X_C}$$

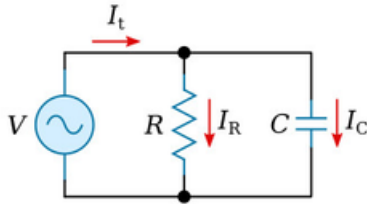Example

A 36-ohm resistor and a 6 microfarad capacitor are connected in parallel as shown in the circuit below. They are both connected across a 1.46 kHz, 25-volt source. Calculate the following: X_C , I_R , I_C , I_t , and Z_t .



Solution


$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(1.46k)(6\mu)} = 18.2\Omega$$

$$I_R = \frac{V}{R} = \frac{25}{36} = 694mA$$


$$I_C = \frac{V}{-jX_C} = \frac{25}{-j18.2} = j1.37A$$

$$I_T = I_R + I_C = 694m + j1.37 = 1.54\angle 63.1^\circ A$$

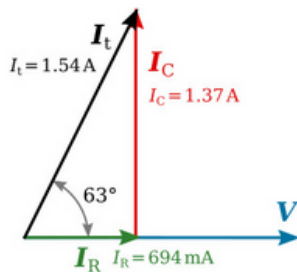
$$Z_T = \frac{V}{I_T} = \frac{25\angle 0^\circ}{1.54\angle 63.1^\circ} = 16.2\angle -63.1^\circ \Omega$$



R-L-C parallel Circuit

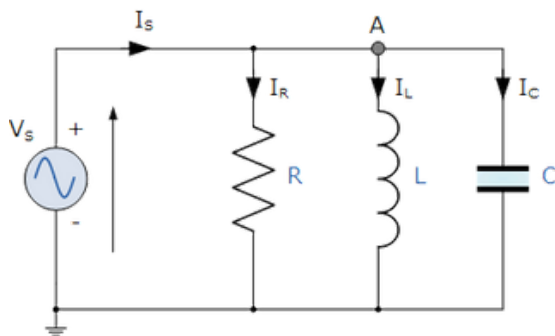

The Phasor diagram:

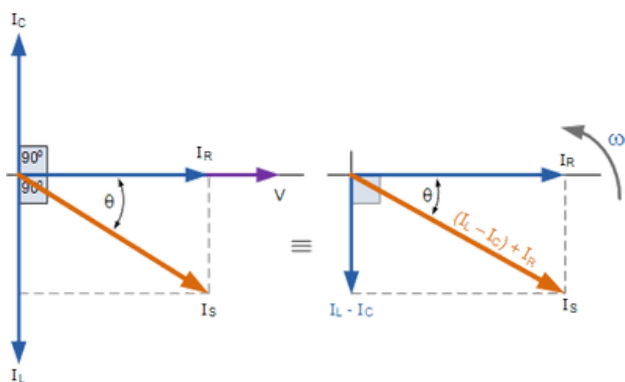

RLC Parallel Circuit Analysis

1) Calculate X_L and X_C

- $X_L = 2\pi fL$
- $X_C = 1/2\pi fL$

2) Calculate the voltages for R, L and C. Since this is a parallel circuit:

- $V_T = V_L = V_C = V_R$

3) By using Ohm's Law, calculate the currents for R and L:

- $I_R = V_T/R$
- $I_L = V_T/X_L$
- $I_C = V_T/X_C$

4) Calculate the total current:

- $I_T = \sqrt{I^2 R + (I_L - I_C)^2}$ or in complex form
- $I_T = I_R + jI_C + (-jI_L)$

5) By using Ohm's Law, calculate the total impedance:

- $Z_T = V_T / I_T$

6) Calculate the phase angles for R and L. Phase angles for these components in a parallel circuit are always:

- $\theta_R = 0^\circ$
- $\theta_C = 90^\circ$
- $\theta_L = -90^\circ$

7) Calculate the total phase angle for the circuit:

- $\theta_T = \tan^{-1} (I_C - I_L) / I_R$

A Parallel RLC Circuit's Impedance

$$R = \frac{V}{I_R} \quad X_L = \frac{V}{I_L} \quad X_C = \frac{V}{I_C}$$

$$Z = \frac{1}{\sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_L} - \frac{1}{X_C}\right)^2}}$$

$$\therefore \frac{1}{Z} = \sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_L} - \frac{1}{X_C}\right)^2}$$

Impedance Triangle

In AC circuit analysis, the relationship between the three elements of impedance—capacitive reactance (X_C), inductive reactance (X_L), and resistance (R)—is visually depicted using an impedance triangle. This triangle helps explain how various components work together to produce the overall impedance (Z) of a circuit.




Impedance Triangle

When examining AC circuits, this triangle is a helpful tool, especially when it comes to power calculations and comprehending how the circuit behaves when alternating current is applied.

Example 1

A 240V, 60Hz supply is used to connect a 160 μ F capacitor, a 142mH coil, and a 1k Ω resistor in parallel. Calculate the supply current as well as the parallel RLC circuit's impedance.

Solution:

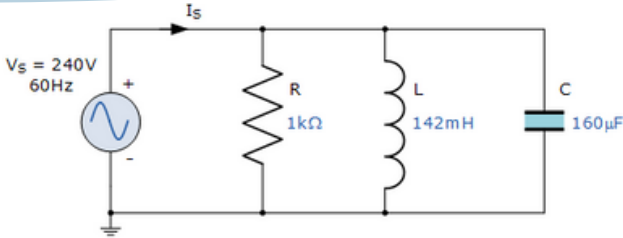

Find X_L :

$$X_L = \omega L = 2\pi fL = 2\pi \cdot 60 \cdot 142 \times 10^{-3} = 53.54 \Omega$$

Find X_C :

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC} = \frac{1}{2\pi \cdot 60 \cdot 160 \times 10^{-6}} = 16.58 \Omega$$

Calculate an Impedance, (Z):

$$Z = \frac{1}{\sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_L} - \frac{1}{X_C}\right)^2}} = \frac{1}{\sqrt{\left(\frac{1}{1000}\right)^2 + \left(\frac{1}{53.54} - \frac{1}{16.58}\right)^2}}$$

$$Z = \frac{1}{\sqrt{1.0 \times 10^{-6} + 1.734 \times 10^{-3}}} = \frac{1}{0.0417} = 24.0 \Omega$$


Calculate the Supply Current, (I_S):

$$I_S = \frac{V_S}{Z} = \frac{240}{24} = 10 \text{ Amperes}$$

Example 2

Three components are connected in parallel over a 50V, 100Hz supply: a 5 μ F capacitor, a 20mH coil, and a 50 Ω resistor. Calculate the total current drawn from the source, the current flowing through each branch, the circuit's total impedance, and the phase angle. Draw the triangles that currently represent the circuit as well.

Solution:

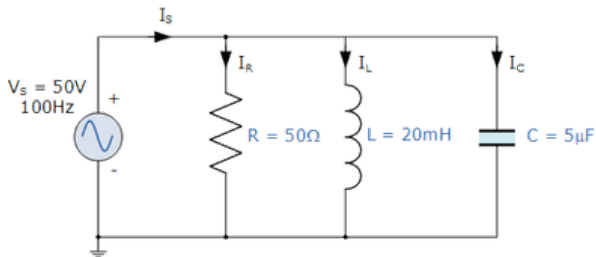

1) Find X_L :

$$X_L = \omega L = 2\pi fL = 2\pi \cdot 100 \cdot 0.02 = 12.6\Omega$$

2) Find X_C

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC} = \frac{1}{2\pi \cdot 100 \cdot 5 \times 10^{-6}} = 318.3\Omega$$

3) Calculate an Impedance, (Z):

$$Z = \frac{1}{\sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_C} - \frac{1}{X_L}\right)^2}} = \frac{1}{\sqrt{\left(\frac{1}{50}\right)^2 + \left(\frac{1}{318.3} - \frac{1}{12.6}\right)^2}}$$

$$Z = \frac{1}{\sqrt{0.0004 + 0.0058}} = \frac{1}{0.0788} = 12.7\Omega$$

4) Calculate the current through resistance, (I_R):

$$I_R = \frac{V}{R} = \frac{50}{50} = 1.0 \text{ (A)}$$

5) Calculate the current through inductor, (I_L)

$$I_L = \frac{V}{X_L} = \frac{50}{12.6} = 3.9 \text{ (A)}$$


6) Calculate the current through capacitor, (I_C)

$$I_C = \frac{V}{X_C} = \frac{50}{318.3} = 0.16 \text{ (A)}$$

7) Calculate the total supply current, (I_S)


$$I_S = \sqrt{I_R^2 + (I_L - I_C)^2} = \sqrt{1^2 + (3.9 - 0.16)^2} = 3.87 \text{ (A)}$$

Draw the current Triangle

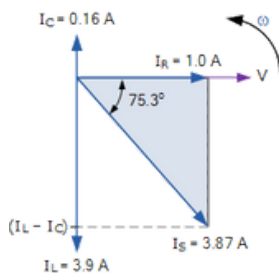

Current Triangle

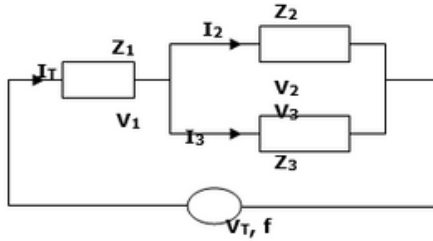R-L-C circuit combination using series and parallel



- Every component in a series connection needs to have the same current.
- The voltage of components connected in parallel must be the same.
- These two guidelines cover both individual parts and sections of circuits.

i) A series-parallel circuit's total impedance .

$$Z_T = Z_1 + Z_2 \parallel Z_3$$
$$Z_T = Z_1 + \frac{Z_2 \times Z_3}{Z_2 + Z_3}$$

ii) Total current:

The supply current, I_T , is equal to the vector sum of the branch currents, I_2 and I_3 .

$$I_T = \frac{V_T}{Z_T} \quad I_2 = \frac{V_2}{Z_2} \quad I_3 = \frac{V_3}{Z_3}$$

iii) The voltage drops across each impedance in a series-parallel circuit.

iv) Since Z_2 and Z_3 are parallel, the voltage loss is equivalent, $V_2 = V_3$. The supply voltage, often known as V_T , is equal to the vector sum of V_1 and V_2 or V_1 and V_3 .

$$V_1 = I_T \times Z_1$$
$$V_2 = V_3 = I_T \times \frac{Z_2 \times Z_3}{Z_2 + Z_3}$$

Energy and Power

- Physics defines work as the application of energy to overcome an obstacle or change the physical state of a body.
- The work capacity is called energy.
- Energy can take many different forms. Some of these include:
 - heat energy
 - light energy
 - sound energy
 - mechanical energy
 - chemical energy
 - electrical energy.
- Numerous commonplace devices transform energy into different forms. For instance:
 - The conversion of electrical energy to sound energy occurs in a loudspeaker.
 - Thermal energy is produced by a toaster from electrical energy.
 - An LED or light bulb produces light by converting electrical energy.
- The unit of measurement for energy (E) is called a joule, and its symbol is J

Power

- The rate of energy consumption is called power, or simply P.
- Said another way, power is the quantity of energy utilized each time, or energy per time, in a particular amount of time. That's an equation.

$$P = \frac{E}{t} \text{ , joules per second or WATT (W)}$$

Power Equations

- When current flows through resistance, electric energy is converted to heat energy.
- The rate of this energy conversion is the power.

$$P = I \times V \quad P = I^2 \times R \quad P = \frac{V^2}{R}$$


- In each of these equations, R is the size (in ohms) of the resistance, V is the voltage (in volts) across the resistance, and I is the current (in amps) through the resistance.

AC circuit power consumption

Pure Resistive Power

- An electrical component or circuit's true or actual power determines how quickly energy is lost from it. Generally, this energy loss is caused by heat dissipation in resistors or by converting one kind of energy into another, as in the case of motors that convert electrical energy into motion.
- In a resistive circuit, current and voltage are in phase, Average power:

$$P = I_{rms} \times E_{rms}$$

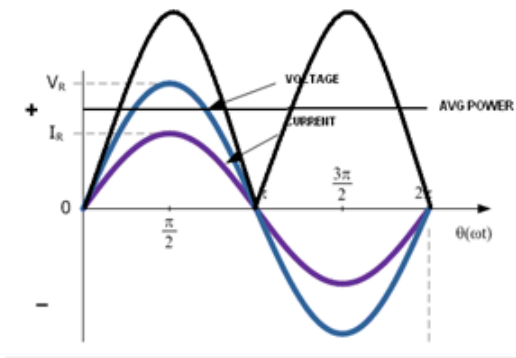

- The voltage and current of the resistor in AC circuits must be in rms values or effective values:

$$P_{true} = V_{rms} \times I_{rms}$$

$$P_{true} = I_{rms}^2 \times R$$


$$P_{true} = \frac{V_{rms}^2}{R}$$

- When a resistor dissipates power, it indicates that a portion of the electrical energy in the circuit is being converted to thermal energy. Due to the heating of the air surrounding the resistor, this energy is lost from the circuit. This is called True Power.

Inductance and capacitance

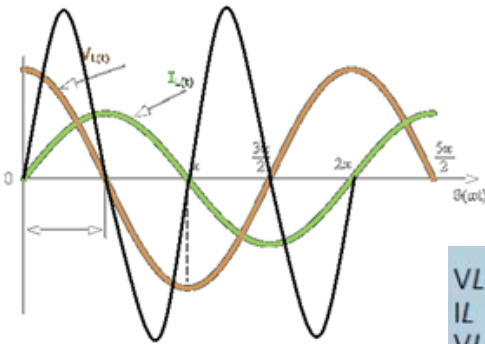a) Electrical Power in an Inductor

- The power in an inductor is associated with the energy stored in its magnetic field.
- The voltage across an inductor is related to the rate of change of current through it.
- When an AC voltage is applied to an ideal inductor, energy is periodically stored and then returned to the source over each cycle.
- During one part of the cycle, energy is stored in the inductor's magnetic field, and during another part, this energy is returned to the source.
- In an ideal inductor:
 - True Power (P_{true}): The net power over a full cycle is zero because all the energy stored during the positive part of the cycle is returned during the negative part. As a result, the true power, measured in watts (W), is zero.
 - Reactive Power (Q): The power associated with the energy that is alternately stored and returned by the inductor is called reactive power. It is measured in volt-amperes reactive (VAR).
- True reactive power represents the rate at which energy is stored and returned by the inductor, with no net loss of energy as heat in an ideal scenario.



$$Q = V_{rms} \times I_{rms}$$

$$Q = I_{2rms} \times X_L$$

$$Q = \frac{V_{2rms}}{X_L}$$

$$V_L = V_{max} \sin(\omega t + 90^\circ)$$

$$I_L = I_{max} \sin \omega t$$


$$V_L \text{ lead } I_L \text{ by } 90^\circ$$

$P = I V = 0$ watt (because +cycle = -cycle so average power = 0)

0 - 90°	90° - 180°	180° - 270°	270° - 360°
V _L = +	V _L = -	V _L = -	V _L = +
I _L = +	I _L = +	I _L = -	I _L = -

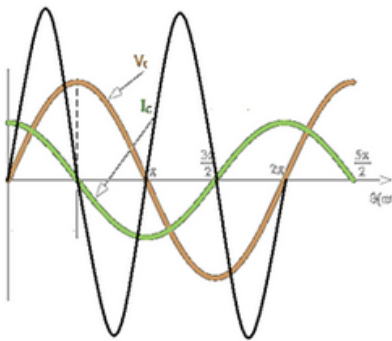b) Power in A Capacitor

- The power in a capacitor, like in an inductor, relates to the energy stored in its electric field.
- The current through a capacitor is related to the rate of change of the voltage across it
- The power represents the rate at which energy is stored in or released from the capacitor's electric field.
- Like in an inductor, in an ideal capacitor, there is no net energy loss over time because the energy stored during one part of the cycle is returned during another part.
- As demonstrated in the example below, for sinusoidal waves, the current flowing through a capacitor leads the voltage across it by 90 degrees.



$$Q = V_{rms} \times I_{rms}$$

$$Q = I_{2rms} \times X_C$$

$$Q = \frac{V_{2rms}}{X_C}$$

$$V_c = V_{max} \sin \omega t$$

$$I_c = I_{max} \sin (\omega t + 90^\circ)$$

I_c lead V_c by 90°

$P = I V = 0$ watt (because +cycle =-cycle so, average power (True Power) =0)

$0 - 90^\circ$	$90^\circ - 180^\circ$	$180^\circ - 270^\circ$	$270^\circ - 360^\circ$
$V_c = +$	$V_c = +$	$V_c = -$	$I_c = +$
$I_c = +$	$I_c = -$	$I_c = -$	$V_c = -$

Reactive Power

- Reactive power (Q) is the power consumed in an AC circuit because of the expansion and collapse of magnetic (inductive) and electrostatic (capacitive) fields.
- Reactive power is expressed in volt-amperes-reactive (VAR).
- Unlike true power, reactive power is not useful power because it is stored in the circuit itself.

Apparent Power

- Apparent Power is the total power in an AC (alternating current) circuit, combining both the real power (which performs actual work) and the reactive power (which oscillates between the source and the reactive components).
- Apparent power represents the product of the circuit's voltage and current without considering the phase angle between them.
- Apparent power is the total power in an AC circuit, representing both the real power that does useful work and the reactive power that cycles back and forth between the source and reactive components.
- It is measured in volt-amperes (VA) and can be visualized using the power triangle, where it is the vector sum of real and reactive power.

Power Triangle

- Power factor (pf), is calculated by dividing true power by its Apparent Power.
- Reactive power is the power that an AC circuit stores
- Real power is the power that the circuit uses.
- $\cos \Phi$ is referred to as the power factor (pf) for an AC circuit. where the phase angle between the applied voltage and the current sine waves is represented by the symbol Φ on a power triangle (see power triangle reference).
- How much of the apparent power is true power is indicated by the power factor ($\text{pf} = \cos \Phi$).
- The circuit is entirely reactive if the power factor is zero, and solely resistive if it is one.

$$\text{Power Factor (pf)} = \cos \Phi = P/S = \text{Watt/VA.}$$

where,

$$\cos \Phi = \text{power factor (pf)}$$

$$P = \text{true power (watts)}$$

$$S = \text{apparent power (VA)}$$

- When the current in a circuit with an inductive load falls behind the voltage, it is referred to as having a lagging power factor.
- A circuit that uses capacitors and has a higher current than voltage is said to have a leading power factor.

Power Factor Correction

- Power Factor Correction is the process of improving the power factor of an electrical system, typically by reducing the amount of reactive power in the system.
- This helps to make the system more efficient by ensuring that more of the power is being used for actual work (real power) and less is being wasted in the form of reactive power.
- Power factor correction is a technique used to improve the power factor of an electrical system, making it more efficient.
- By reducing reactive power, power factor correction lowers energy costs, increases system capacity, reduces losses, and improves voltage stability.
- This is typically achieved through the use of capacitors, synchronous condensers, or other specialized equipment.

Example 2

A 240V, 1kHz voltage source is connected to a parallel 20Ω resistor with a 20mH inductance. Calculate the overall current, the current in each branch, the apparent power, the true power, and the reactive power.



Solution:

$$X_L = 2\pi fL = 2\pi(1k)(20m) = 125.66\Omega$$

$$I_R = \frac{V}{R} = \frac{240}{20} = 12A$$

$$I_L = \frac{V}{X_L} = \frac{240}{125.66} = 1.91A$$

$$I_T = I_R - jI_L = 12 - j1.91 = 12.15\angle -9.04^\circ A$$

$$\text{True Power, } P = IV \cos \theta = (12.15)(240) \cos 9.04^\circ = 2.88kW$$

$$\text{Reactive Power, } Q = IV \sin \theta = (12.15)(240) \sin 9.04^\circ = 458.17VAR$$

$$\text{Apparent Power, } S = IV = (240)(12.15) = 2.92kVA$$




END OF CHAPTER

QUESTION 1:


For the below circuit, express the phasor diagram that demonstrates the relationship between V_R , V_C , V_T , I_T , I_R , and I_C .

ANSWER:

i. Series circuit

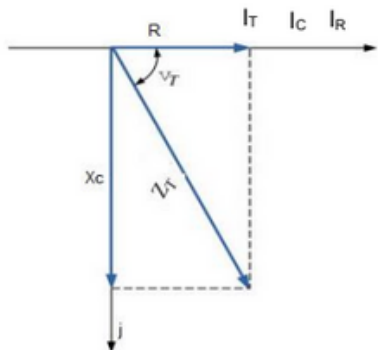

ii. Parallel RC circuit

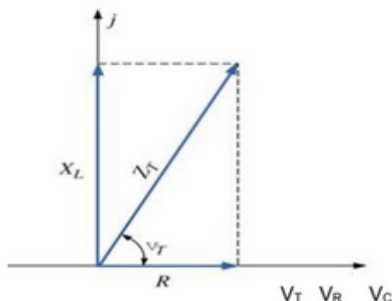

QUESTION 2:

The values of a series RLC circuit are as follows: $L = 25 \text{ mH}$, $C = 220 \mu\text{F}$, and $R = 8 \Omega$. Suppose the instantaneous voltage in the circuit is $V_s = 17 \sin(377t) \text{ V}$. Calculate the instantaneous current at $t = 5 \text{ ms}$ and create a phasor diagram for it.

ANSWER:

$$f = \frac{\omega}{2\pi} = \frac{377}{2\pi} = 60 \text{ Hz}$$

$$X_L = 2\pi fL = 2\pi(60)(25 \text{ m}) = 9.34 \Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(60)(220 \mu)} = 12.06 \Omega$$

$$Z_T = R + jX_L - jX_C$$


$$Z_T = 8 + j9.34 - j12.06$$

$$Z_T = 8 - j2.63 \quad \text{or} \quad 8.42 \angle -18.19^\circ \Omega$$

$$I_T = \frac{V_S}{Z_T} = \frac{17 \angle 0^\circ}{8.42 \angle -18.19^\circ} = 2.02 \text{ A} \angle 18.19^\circ$$

Current leads the voltage by 18.19°

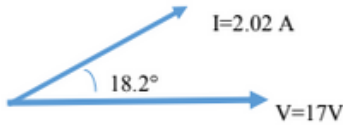Voltage is given $V_S = 17 \sin(377t)$ V, which makes voltage the reference at 0° and $I = 2.02 \sin(377t + 18.2^\circ)$



Value of current at 5.0ms,
 $I = 2.02 \sin(377t + 18.2^\circ)$ A
 $I = 2.02 \sin(377(5m) + 18.2^\circ)$
 $I = 1.63$ A

QUESTION 3:

A capacitive circuit is fed by a 240V, 50Hz supply. There is a 2A current flow in the circuit and 150 watts of power loss. Calculate the resistance and capacitance values.

ANSWER:

$$\text{Power Dissipated, } P = IV \cos \theta$$

$$\cos \theta = \frac{150}{(240)(2)} = 0.3125$$

$$Z_T = \frac{V_S}{I_T} = \frac{240}{2} = 120 \Omega$$

$$\text{Power Factor, } \cos \theta = \frac{R}{Z_T}$$

$$R = \cos \theta (Z_T) = (0.3125)(120) = 37.5 \Omega$$

$$Z_T = \sqrt{R^2 + X_C^2}$$

$$X_C = \sqrt{Z_T^2 - R^2} = \sqrt{120^2 - 37.5^2} = 114 \Omega$$

$$X_C = \frac{1}{2\pi fC}$$

$$C = \frac{1}{2\pi(50)(114)} = 27.92 \mu F$$

QUESTION 4:

A 240V, 1KHz voltage source is connected in parallel to a 75Ω resistor with a 40mH inductance. Calculate the total current, the true power, apparent power, reactive power, power factor, and the current in each branch.

ANSWER:

$$X_L = 2\pi fL = 2\pi(1k)(40m) = 251.33\Omega$$

$$I_R = \frac{V_R}{R} = \frac{240}{75} = 3.2A$$

$$I_L = \frac{V_L}{X_L} = \frac{240}{251.33} = 0.95A$$

$$I_T = I_R - jI_L = 3.2 - j0.95 = 3.34A \angle -16.53^\circ$$

True power, $P = IV \cos \theta$

$$\text{True power, } P = (3.34)(240) \cos 16.53^\circ = 768.47 \text{ W}$$

Reactive power, $Q = IV \sin \theta$

$$\text{Reactive power, } Q = (3.34)(240) \sin 16.53^\circ = 228.07 \text{ VAR}$$

Apparent power, $S = IV$

$$\text{Apparent power, } S = (3.34)(240) = 801.6 \text{ VA}$$

QUESTION 5:

A 120V, 50 Hz voltage supply is used in an RLC series circuit, which also has $R = 22\Omega$, $C = 220\mu\text{F}$, and $L = 110\text{mH}$.

a. Calculate:-

i. Total Impedance

ii. Total Current

iii. Power factor

iv. True power

v. Reactive power

vi. Apparent

b. Draw the vector diagram.

ANSWER:

$$X_L = 2\pi fL = 2\pi(50)(110m) = 34.56\Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(50)(220\mu)} = 14.47\Omega$$

$$Z_T = 22 + j34.56 - j14.47 = 22 + j20.1 = 29.8 \angle 42.4^\circ \Omega$$


$$I_T = \frac{V_S}{Z_T} = \frac{120 \angle 0^\circ}{29.8 \angle 42.4^\circ} = 4A \angle -42.4^\circ$$

$$\text{Power Factor, } pf = \cos 42.4^\circ = 0.74 \text{ lagging}$$

$$\text{True Power, } P = IV \cos 42.4^\circ = (4)(120)(0.74) = 355.2W$$

$$\text{Reactive Power, } Q = IV \sin 42.4^\circ = (4)(120) \sin 42.4^\circ = 322.86 \text{ VAR}$$
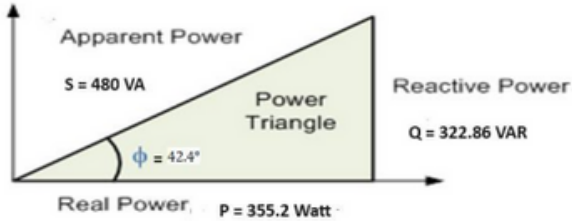
$$\text{Apparent Power, } S = IV = (4)(120) = 480 \text{ VA}$$



EXERCISE



1

For purely resistive, purely inductive, and purely capacitive AC circuits, draw a phasor diagram to show the relationship between current and voltage.




Answer

Refer to topic 2

2

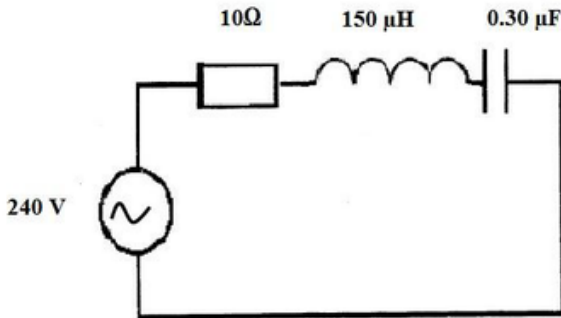Calculate the Z_T , or total impedance, for the series circuit at a frequency of 30 kHz by referring to the figure below.




Answer

$$Z_T = 10 + j10.59 = 14.56 \angle 46.64^\circ \Omega$$

3

Calculate the total current (I_T) following through the circuit by referring to the figure below.

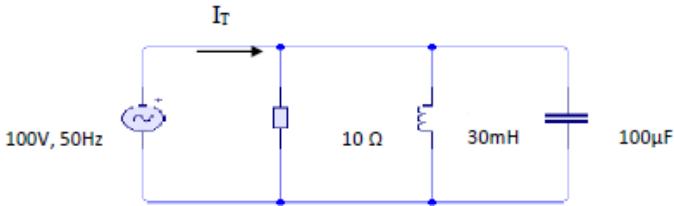**Answer**

$$I_T = 10 - j7.84 = 12.49 \angle -36.8^\circ A$$

4

Calculate the total impedance and circuit current of an RLC series circuit that is connected in series across a 100V, 50Hz supply with a 12Ω resistance, a 0.15H inductance, and a 100uF capacitor.

**Answer**


$$Z = 19.4 \Omega$$

$$I = 5.15 A$$

5

As shown in the figure below, a 50Hz power source is connected in series with a 100 μ F capacitor and a coil of inductance 100mH and resistance 10 Ω . Calculate :

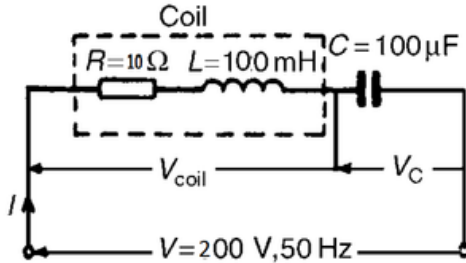- i) Circuit impedance, Z
- ii) Circuit current, I
- iii) Phase angle
- iv) Voltage across inductor
- v) Voltage across capacitor



Answer

- (i) $Z = 10 \Omega$ (iii) $\phi = 2.35^\circ$ (v) $V_C = 636.6 \text{ V}$
 (ii) $I = 20 \text{ A}$ (iv) $V_L = 628.4 \text{ V}$

6

An 80 μ F capacitor, a 0.1H inductor, and a 15 Ω resistor are connected in series to power supply 100V at 50Hz. Calculate:

- i) Total impedance
- ii) Total circuit current
- iii) Voltage across each components



Answer

$$Z = 15 - j8.37 = 17.18 \angle -29.16^\circ \Omega$$

$$I = 5.82 \angle 29.16^\circ \text{ A}$$

$$V_R = 87.3 \text{ V}$$

$$V_L = 182.86 \text{ V}$$

$$V_C = 234.36 \text{ V}$$

7

A 100V, 50Hz supply is connected in series with a 90Ω resistor, 0.3H inductor, $10\mu\text{F}$ capacitor, and 1H inductor. Calculate the actual power dissipation of the circuit as well as the voltage across each component.



Answer

$$V_R = 71.1 \text{ V}$$


$$V_L = 322.64 \text{ V}$$

$$V_C = 251.5 \text{ V}$$

$$P = 55.83 \text{ Watt}$$

8

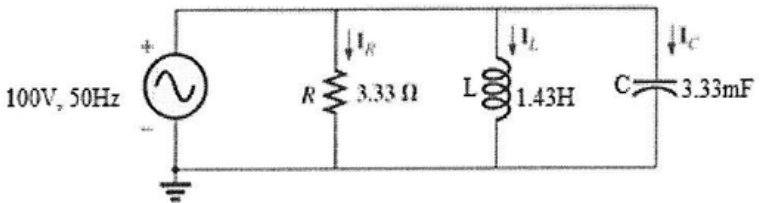Calculate the total current I_T and total impedance Z_T by referring to the figure below.



Answer

$$Z_T = 0.254 + j0.885 = 0.921 \angle -73.95^\circ \Omega$$

$$I_T = 30.02 + j104.35 = 108.58 \angle 73.95^\circ \text{ A}$$

9

A coil has a 40 mH inductance and negligible resistance. Calculate the current that results from its inductive reactance if it is connected to:

- A 240V, 50 Hz supply
- A 100V, 1KHz supply




Answer

- $X_L = 12.57\Omega, I = 19.09A$
- $X_L = 251.3\Omega, I = 0.398A$

10

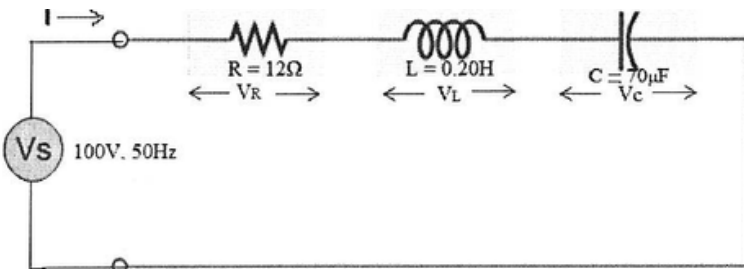Calculate the circuit's total current flow (I) and draw the voltage phase diagram by referring to the figure below.




Answer

$$I = 4.739 A$$



Answer

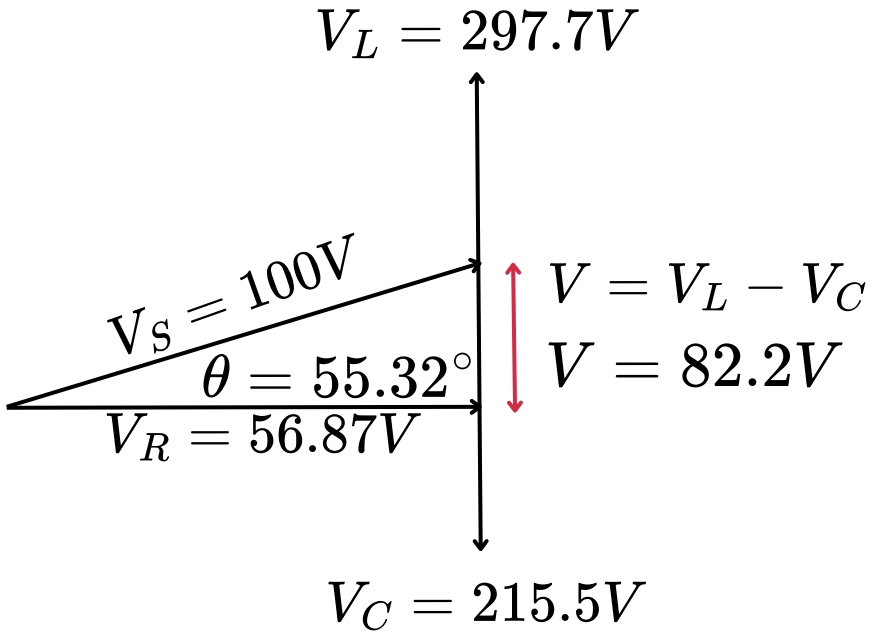

TOPIC 3

RESONANCE



INTRODUCTION

Resonance

At this chapter we will: (CLO 1)

- Understand resonance in series and parallel circuits
- Apply resonance in series and parallel circuits



Resonance is a system's tendency to oscillate with greater amplitude at certain frequencies than at others



Resonance occurs when a system can easily store and transfer energy between two or more different storage modes




Resonance is used, among other things, to establish a stable frequency state in circuits intended to generate AC signals

FUNCTIONS OF RESONANCE:



1

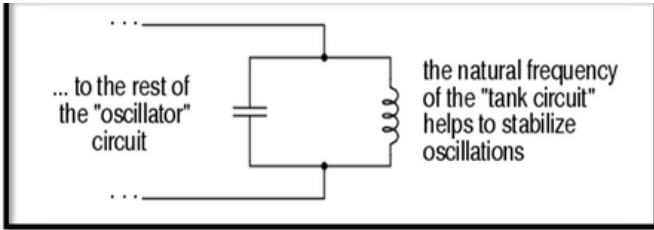
The resonance circuit acts as stable frequency source



The frequency set by the tank circuit is safety depending on the value of L & C

2

Resonance circuit serves as filter

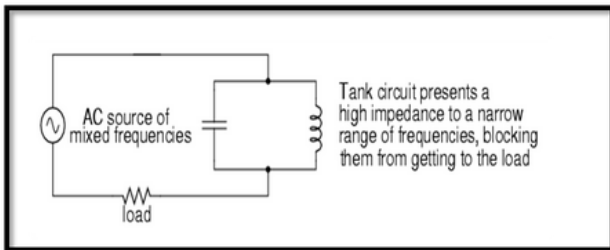


Acting as a short of frequency "filter" to prevent some frequencies from mixing with others.

RESONANCE PHENOMENON



In an RLC circuit, resonance occurs when the capacitive and inductive reactance are the same magnitude, resulting in a completely resistive impedance
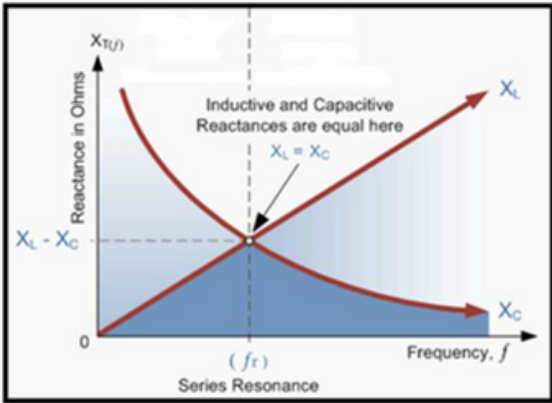
$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right) \quad ; \text{ note : } \omega L - \frac{1}{\omega C} = 0$$



$$X_L = X_C$$

$$X_L = 2\pi fL \qquad X_C = \frac{1}{2\pi fC}$$

.. setting the two equal to each other, representing a condition of equal reactance (resonance) ..


$$2\pi fL = \frac{1}{2\pi fC}$$

RLC Series & Parallel Circuit

RLC Series Circuit


Explain the effect of changing the frequency

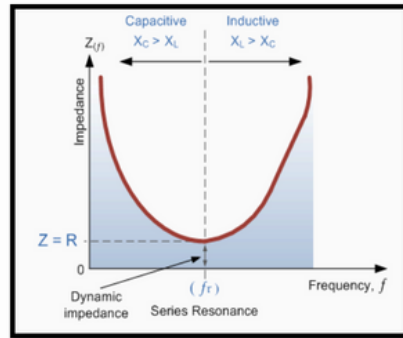- ✓ A series RLC circuit contains both inductive reactance (X_L) and capacitive reactance (X_C)
- ✓ A series RLC circuit's reactance changes as you change the voltage source's frequency.
- ✓ Its total impedance also changes.
- ✓ At low frequencies, $X_C > X_L$ and the circuit is primarily capacitive.
- ✓ At high frequencies, $X_L > X_C$ and the circuit is primarily inductive.



RLC Parallel Circuit

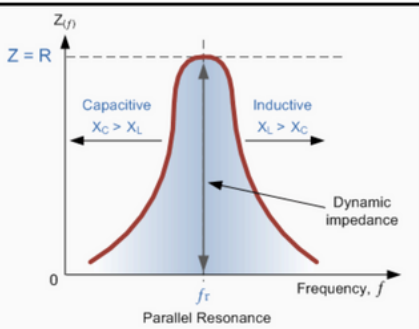Explain the effect of changing the frequency



- ✓ Reactance change as you change the voltage source's frequency.
- ✓ At low frequencies, $X_L < X_C$ and the circuit is primarily inductive.
- ✓ At high frequencies, $X_C < X_L$ and the circuit is primarily capacitive.

Series Resonance

Current will be maximum & offering minimum impedance


- ✓ Consider a RLC circuit in which resistor, inductor and capacitor are connected in series across a voltage supply.
- ✓ This series RLC circuit has distinguishing property of resonating at a specific frequency called resonant frequency
- ✓ In this circuit containing inductor and capacitor the energy is stored in two different ways
- ✓ When a current flows in an inductor, energy is stored in magnetic field
- ✓ When a capacitor is charged, energy is stored in electric field.

series resonance




min Z at series resonance

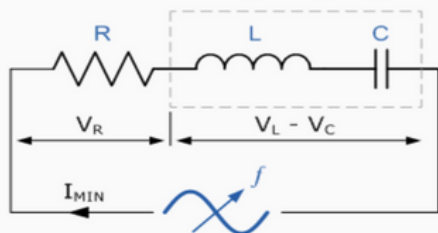Either side of resonance the voltage drop = $V_L - V_C$



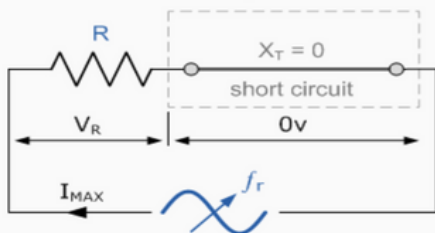At resonance the voltage drop equals zero



(i) $V_L = V_C$

(ii) $Z = R$ (i.e. the minimum circuit impedance possible in an RLC circuit)

(iii) $I = \frac{V}{R}$ (i.e. the maximum current possible in an RLC circuit).

(iv) Since $X_L = X_C$, then $2\pi fL = \frac{1}{2\pi fC}$



$$f^2 = \frac{1}{2\pi L \times 2\pi C} = \frac{1}{4\pi^2 LC} = \sqrt{\frac{1}{4\pi^2 LC}}$$

$$f = \frac{1}{2\pi\sqrt{LC}} \text{ (Hz)}$$

Parallel Resonance

Current will be minimum & offering maximum impedance

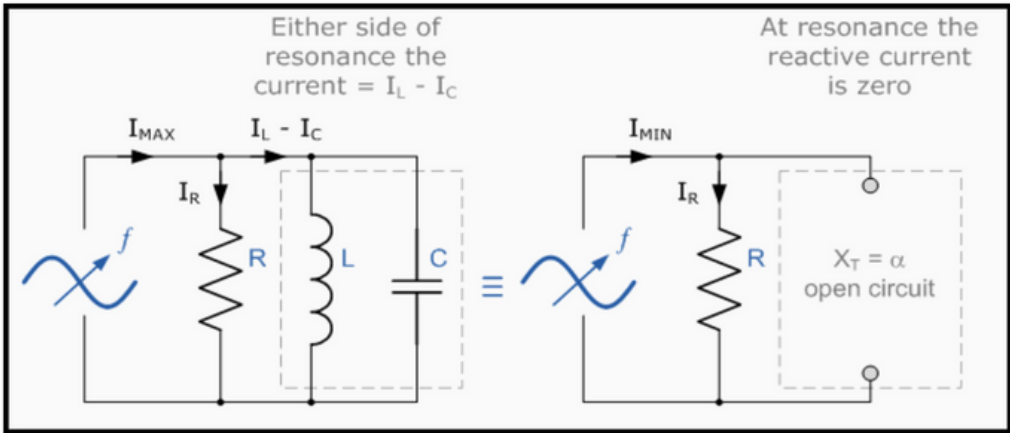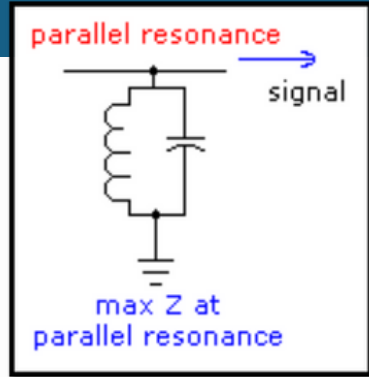- Resonance occurs in the two branch network containing capacitance (C) in parallel with inductance (L) and resistance (R) in series when the quadrature (i.e. vertical) component of current ILR is equal Ic
- At this condition the supply current I is in-phase with the supply voltage V.




Resonance occurs when $X_L = X_C$ and the imaginary parts of Y become zero.

$$X_L = X_C \Rightarrow 2\pi fL = \frac{1}{2\pi fC}$$

Then:

$$f^2 = \frac{1}{2\pi L \times 2\pi C} = \frac{1}{4\pi^2 LC} = \sqrt{\frac{1}{4\pi^2 LC}}$$
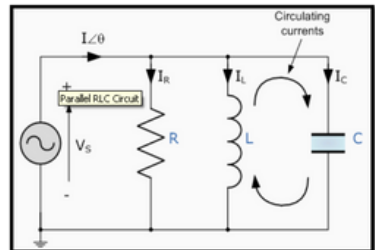
$$\therefore f_r = \frac{1}{2\pi\sqrt{LC}} \text{ (Hz)} \text{ or } \omega_r = \frac{1}{\sqrt{LC}} \text{ (rads)}$$



Think About It!



EXAMPLE 3.1a:

A coil with a resistance of 14Ω and inductance of 120mH is connected in series with a $60\mu\text{F}$ capacitor across a 140V supply. What frequency produces resonance? Determine the current flowing at the resonance frequency.

$$\begin{aligned}\text{Resonant frequency, } f_r &= \frac{1}{2\pi\sqrt{LC}} \\ &= \frac{1}{2\pi\sqrt{(120\text{m})(60\mu)}} \\ &= 59.31\text{Hz}\end{aligned}$$

ANSWER 3.1a:

At resonance, $X_L = X_C$ and impedance $Z = R$

$$\text{Hence current, } I = \frac{V}{R} = \frac{140}{14} = 10\text{A}$$

EXAMPLE 3.1b:

The current at resonance in a series RLC circuit is $100\mu\text{A}$. Determine the circuit resistance and capacitance when the applied voltage is 2mV at a frequency of 200kHz and the circuit inductance is $50\mu\text{H}$.

ANSWER 3.1b:

At resonance, impedance $Z = R$

$$\text{Hence, } R = \frac{V}{I} = \frac{2\text{m}}{200\mu} = 10\Omega$$

At resonance, $X_L = X_C$


$$\text{Hence, } 2\pi fL = \frac{1}{2\pi fC}$$

$$30\mu\text{H} = \frac{1}{2\pi fC}$$

$$C = \frac{1}{2\pi(150\text{kHz}) \times (30\mu\text{H})}$$

$$C = 35.37\text{mF}$$

FREQUENCY BANDWIDTH

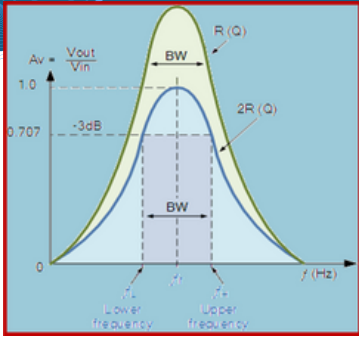

- Figure show how current I varies with frequency in an RLC series circuit.
- At the resonant frequency , current is a maximum value, shown as I_r .
- Also shown are the points A and B where the current is 0.707 of the maximum value at frequencies and
- The power delivered to the circuit is

- At $I = 0.707 I_r$, the power is $(0.707 I_r)^2 R = 0.5 I_r^2 R$, i.e. half the power that occurs at frequency f_r .
- The distance between these points, i.e. $(f_2 - f_1)$, is called the bandwidth, BW.

$$Q = \frac{f_r}{B} = \frac{f_r}{(f_2 - f_1)}$$

or Bandwidth, B,

$$f_2 - f_1 = \frac{f_r}{Q}$$

The points corresponding to f_L and f_U are called the half-power points.

$$\text{Lower frequency, } f_L = f_r - \frac{BW}{2}$$

$$\text{Upper frequency, } f_U = f_r + \frac{BW}{2}$$

QUALITY FACTOR, Q



A) SERIES CIRCUIT

- Q is the ratio of power stored to power dissipated in the circuit reactance and resistance
- Q is the ratio of its resonant frequency to its bandwidth

$$Q = \frac{X_L}{R} = \frac{2\pi fL}{R}$$

$$\text{if; } f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$Q = \frac{2\pi \left(\frac{1}{2\pi\sqrt{LC}} \right) L}{R}$$

$$Q = \frac{L}{R\sqrt{LC}} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$



B) PARALLEL CIRCUIT

- Quality factor: the ratio of the circulating branch currents to the supply current.

$$\begin{aligned} Q &= \frac{R}{2\pi fL} \\ &= 2\pi fCR \\ &= R \sqrt{\frac{C}{L}} \end{aligned}$$

Think About It!

EXAMPLE 3.2:

A 100mH coil of inductance is connected in series with a 2μF capacitor and 10Ω resistance across a 240V variable frequency supply. Calculate the resonant frequency, the current at resonance, the voltage across inductor and capacitor at resonance and Quality factor of the circuit.



ANSWER 3.2:

a) Resonant frequency, f_r

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$
$$f_r = \frac{1}{2\pi\sqrt{100m \times 2\mu}} = 355.88Hz$$

b) Current at resonance, $I = \frac{V}{R} = \frac{240}{10} = 24A$

c) Voltage across inductor and capacitor at resonance,

$$V_L = V_C$$

$$V_L = IX_L = (I)(2\pi fL)$$

$$V_L = (8)[2\pi(355.88)(100m)]$$

$$V_L = 5366.54V$$

$$V_L = V_C = 5366.54V$$

b) Q - factor, $Q = \frac{X_L}{R} = \frac{[2\pi(355.88)(100m)]}{10} = 22.36A$






END OF CHAPTER

01

Explain the effect of changing the frequency on an RLC series circuit using an appropriate diagram

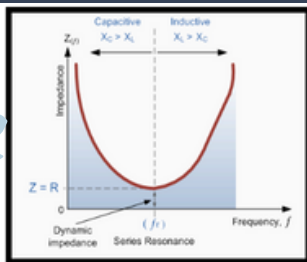

ANSWER 01:

- If $X_L < X_C$ and the circuit is primarily capacitive (Low frequencies)
- If $X_C < X_L$ and the circuit is primarily inductive (High frequencies)

02

An RLC series circuit has a resonance frequency of 2kHz and Q-factor of 40. Calculate the inductance, capacitance, bandwidth, lower and upper cut-off frequencies for a circuit with a 30Ω impedance at resonance.

At Resonant frequency, the circuit impedance, $Z = R = 30\Omega$

$$Q - \text{factor}, Q = \frac{X_L}{R} = \frac{2\pi fL}{R}$$

$$L = \frac{QR}{2\pi f} = \frac{(40)(30)}{2\pi(2k)} = 95.5\text{mH}$$

At Resonant, $X_L = X_C$

$$2\pi fL = \frac{1}{2\pi fC}$$

$$C = \frac{1}{(2\pi f)^2 L} = \frac{1}{(2\pi 2k)^2 \times 95.5\text{m}} = 0.0663\mu\text{F}$$

$$\text{Bandwidth, } BW = \frac{f_r}{Q} = \frac{2k}{40} = 50\text{Hz}$$

$$f_L = f_r - \frac{BW}{2} = 2k - \frac{50}{2} = 1975\text{Hz}$$

$$f_H = f_r + \frac{BW}{2} = 2k + \frac{50}{2} = 2025\text{Hz}$$

ANSWER 02:



A series resonance circuit with a $47\mu\text{F}$ capacitor, 100Ω resistor and 70mH inductor is connected to a sinusoidal source voltage produces a consistent output of 5V at all frequencies.

Calculate, Resonance frequency, Current resonance, Voltage across the inductor and capacitor at resonance and Quality factor, Q



Resonance Frequency, f_r

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$f_r = \frac{1}{2\pi\sqrt{(70\text{m})(47\mu)}} = 87.74$$

ANSWER 03:

Current at Resonance, I

$$Z_R = R = 100\Omega$$

$$I_{\text{max}} = \frac{V_T}{Z_R}$$

$$I = \frac{5}{100} = 0.05\text{A} @ 50\text{mA}$$

Voltage across inductor, V_L

$$V_L = I \times X_L$$

$$= 0.05 \times 38.6 = 1.93\text{V}$$

Voltage across capacitor, $V_C = V_L = 1.93\text{V}$

Quality Factor, Q

$$Q = \frac{X_L}{R} = \frac{2\pi fL}{R} = \frac{2\pi(87.74)(70\text{m})}{100}$$

$$Q = 0.39$$

A 100mH coil inductance is connected in series with a 10 μ F capacitor and a 100 Ω resistance across a 240V, variable frequency supply. Calculate the resonant frequency, the current at resonance, voltage across inductor and capacitor at resonance and Q-factor of the circuit.

ANSWER 04:

Resonance Frequency, f_r

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$f_r = \frac{1}{2\pi\sqrt{(100m)(10\mu)}} = 159\text{Hz}$$

Quality Factor, Q

$$Q = \frac{X_L}{R} = \frac{2\pi fL}{R} = \frac{2\pi(159)(100m)}{100}$$

$$Q = 1$$

Current at Resonance, I

$$Z_R = R = 100\Omega$$

$$I_{max} = \frac{VT}{Z_R}$$

$$I = \frac{240}{100} = 2.4A$$

Voltage across inductor, V_L

$$V_L = I \times X_L$$

$$= 2.4 \times 100 = 240V$$

Voltage across capacitor, $V_C = V_L = 240V$

A circuit with of a $900\mu\text{F}$ capacitor, 90mH inductor and 9Ω resistor is connected in series to a 150V AC source. Calculate the upper and lower cut-off frequencies. Then using the acquired value, draw a resonance graph of Current versus Frequency.

ANSWER 05:

Resonance Frequency, f_r

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$f_r = \frac{1}{2\pi\sqrt{(90\text{m})(900\mu)}} = 17.68\text{Hz}$$

Quality Factor, Q

$$Q = \frac{XL}{R} = \frac{2\pi fL}{R} = \frac{2\pi(17.68)(90\text{m})}{9}$$

$$Q = 1.11$$

Bandwidth, BW

$$BW = \frac{f_r}{Q} = \frac{17.68}{1.11}$$

$$= 15.91\text{Hz}$$

Lower cut - off frequency, f_L

$$f_L = f_r - \frac{BW}{2}$$

$$= 17.68 - \frac{15.91}{2}$$

$$= 9.72\text{Hz}$$

Upper cut - off frequency, f_H

$$f_H = f_r + \frac{BW}{2}$$

$$= 17.68 + \frac{15.91}{2}$$

$$= 25.64\text{Hz}$$


Current at Resonance, I

$$Z_R = R = 9\Omega$$

$$I_{\text{max}} = \frac{VT}{ZR}$$

$$I = \frac{150}{9} = 16.67\text{A}$$

Resonance Graph (Current vs Frequency)

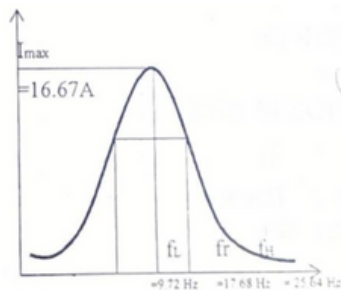

EXERCISE

1

A coil of inductance 120mH are connected in series with a capacitance of $2\mu\text{F}$ and a resistance of 12Ω across a 50V and variable frequency supply. Determine the bandwidth of the circuit during the resonance and voltage across each component.

ANSWER 01:

Frequency resonance = 324.87Hz
Quality factor, $Q = 20.4$
Bandwidth, $B_w = 15.92\text{Hz}$
Frequency Low, $F_L = 316.91\text{Hz}$
Frequency High, $F_H = 332.83\text{Hz}$

2

A series resonance circuit consists of $20.3\mu\text{F}$ capacitor, a coil 0.5H and a resistor 40Ω . When the circuit is connected to a 240V AC supply, calculate the frequency resonance, current of the circuit, voltage across each component, the bandwidth and the Q factor.

ANSWER 02:

Frequency resonance = 49.96Hz
Current, $I = 6\text{A}$ $V_R = 240\text{V}$
 $V_L = V_C = 941.7\text{V}$ $B_w = 12.74\text{Hz}$
Quality factor, $Q = 3.92$

3

A coil with 60mH inductance and 100Ω resistance are connected in series with a capacitance of $0.6\mu\text{F}$ across a 240V variable frequency supply. Calculate the upper and lower cut-off frequencies during resonance.

ANSWER 03:

Frequency resonance = 838.82Hz
Quality factor, $Q = 3.16$ $B_w = 265.45\text{Hz}$
Frequency Low, $F_L = 706.1\text{Hz}$
Frequency High, $F_H = 971.5\text{Hz}$

EXERCISE

4

A circuit which consists 25Ω resistor, 2.5mH inductor and 550pF capacitor is connected in series across 2.5V AC supply. Calculate the upper and lower cut-off frequency.

ANSWER 04:

Frequency resonance = 135.73kHz
Quality factor, $Q = 82.28$
Bandwidth, $B_w = 1.59\text{kHz}$
Frequency Low, $FL = 134.94\text{kHz}$
Frequency High, $FH = 136.53\text{kHz}$

5

A circuit with a 45mH inductor, $100\mu\text{F}$ capacitor and 12Ω resistor is connected in series across 220V AC supply. Calculate frequency resonance, quality factor, bandwidth, the upper and lower cut-off frequencies.

ANSWER 05:

Frequency resonance = 75.03Hz
Quality factor, $Q = 1.77$
Bandwidth, $B_w = 42.39\text{Hz}$
Frequency Low, $FL = 53.84\text{Hz}$
Frequency High, $FH = 96.23\text{Hz}$

6

A series resonance circuit consists of a $8\mu\text{F}$ capacitor, 40mH inductor and 50Ω resistor. When the circuit is connected to a 10V AC supply, calculate the current, frequency resonance, quality factor Bandwidth and the lower and upper cut-off frequencies during resonance.

ANSWER 06:

Current, $I = 0.2\text{A}$
Frequency resonance = 281.3Hz
Quality factor, $Q = 1.414$
Bandwidth, $B_w = 198.9\text{Hz}$
Frequency Low, $FL = 181.8\text{Hz}$
Frequency High, $FH = 380.8\text{Hz}$

EXERCISE



7

An RLC series circuit has a resonant frequency of 2kHz and Q-factor at resonance of 40. If the impedance of the circuit at resonance is 30Ω , determine the values of inductance, capacitance, bandwidth, lower and upper cut-off frequencies.

ANSWER 07:

Inductance, $L = 9.55\text{mH}$
Capacitance, $C = 0.0663\mu\text{F}$
Bandwidth, $Bw = 50\text{Hz}$
Frequency Low, $FL = 1975\text{Hz}$
Frequency High, $FH = 2025\text{Hz}$

8

A series of resonance circuit consists 80mH inductor, a capacitor of $16\mu\text{F}$ and a resistor of 100Ω . This circuit is connected to a 240V ac supply. Calculate resonance frequency, current during resonance, Quality Factor, bandwidth, lower and upper cut-off frequency.

ANSWER 08:

Frequency resonance = 140.67Hz
Current, $I = 2.4\text{A}$ Quality factor, $Q = 0.7$
Bandwidth, $Bw = 198.13\text{Hz}$
Frequency Low, $FL = 41.61\text{Hz}$
Frequency High, $FH = 239.74\text{Hz}$

9

A $2\mu\text{F}$ capacitor is connected in series with a 100mH inductor and a 10Ω resistor across a 240V variable frequency power supply. Determine the resonant frequency, the current at resonance, Q-factor, voltages across inductor and capacitor at resonance of the circuit.

ANSWER 09:

Frequency resonance = 355.88Hz
Current, $I = 24\text{A}$
Quality factor, $Q = 22.36$
 $V_L = V_C = 5366.51\text{V}$

REFERENCES:

- Bird, J. (2022). Bird's Electrical Circuit Theory and Technology. 7th Edition. London, United Kingdom: Taylor & Francis Ltd.
- Floyd, T. L., Buchla, D.M. (2021). Principles of Electric Circuits: Conventional Current .10th Edition. Upper Saddle River, NJ, United States: Pearson Education (US).
- Hambley, A. R. (2019). Electrical Engineering: Principles & Applications, 7th Edition. Harlow, United Kingdom: Pearson Education Limited.
- Wang, M. (2019). Understandable Electric Circuits: Key concepts. 2nd Edition. Stevenage, United Kingdom: Institution of Engineering and Technology.
- Bird, J. (2017). Electrical and Electronic Principles and Technology. 6th Edition. London, United Kingdom: Taylor & Francis Ltd.
- Ashby, D. (2012). Electrical Engineering 101. 3rd Edition. Oxford, United Kingdom: Elsevier Science & Technology.



Cataloguing-in-Publication Data

Perpustakaan Negara Malaysia

A catalogue record for this book is available
from the National Library of Malaysia

eISBN 978-629-7643-45-8