



BAHAGIAN PEPERIKSAAN DAN PENILAIAN
JABATAN PENDIDIKAN POLITEKNIK
KEMENTERIAN PENDIDIKAN TINGGI

JABATAN KEJURUTERAAN ELEKTRIK

PEPERIKSAAN AKHIR

SESI DISEMBER 2015

DEE1012: MEASUREMENT

TARIKH : 7 APRIL 2016

MASA : 8.30 AM – 10.30 AM (2 JAM)

Kertas ini mengandungi **SEBELAS (11)** halaman bercetak.

Bahagian A: Objektif (10 soalan)


Bahagian B: Struktur (4 soalan)

Bahagian C: Esei (2 soalan)

Dokumen sokongan yang disertakan : Tiada

JANGAN BUKA KERTAS SOALAN INI SEHINGGA DIARAHKAN

(CLO yang tertera hanya sebagai rujukan)



SECTION B: 60 MARKS
BAHAGIAN B: 60 MARKAH

INSTRUCTION:

This section consists of **FOUR (4)** structured questions. Answer **ALL** questions.

ARAHAN:

Bahagian ini mengandungi EMPAT (4) soalan berstruktur. Jawab SEMUA soalan. terminologies

QUESTION 1

SOALAN 1

- CLO1
C1
- (a) Define measurement.
Beri definisi Pengukuran.
- [3 marks]
[3 markah]
- CLO1
C2
- (b) Explain the terminology of scale and range.
Terangkan terminologi bagi skala dan julat.
- [6 marks]
[6 markah]
- CLO1
C2
- (c) Explain the characteristics of measurement for accuracy and precision.
Terangkan ciri-ciri ketepatan dan kejituan dalam pengukuran.
- [6 marks]
[6 markah]

QUESTION 2

SOALAN 2

- CLO1
C1
- (a) Describe basic principle of DC and AC Meter.
Jelaskan prinsip asas Meter AT dan AU.
- [3 marks]
[3 markah]

- CLO2
C3 (b) Calculate the value of the multiplier resistance for the multiple range DC voltmeter circuit shown in Figure B 2(b) if $I_m = 100\mu\text{A}$ and $R_m = 10\text{k}\Omega$.
Kirakan nilai perintang pelbagai untuk julat pelbagai dalam litar meter volt AT dalam Rajah B 2(b) jika diberi $I_m = 100\mu\text{A}$ dan $R_m = 10\text{k}\Omega$.

[6 marks]

[6 markah]

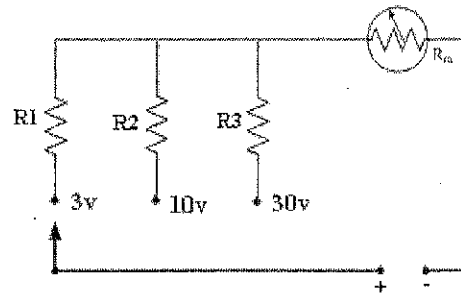


Figure B 2(b)/ Rajah B 2(b)

- CLO2
C3 (c) With the aid of a diagram, describe the basic construction and operating principle of Permanent Magnet Moving Coil (PMMC).
Dengan bantuan gambarajah, jelaskan binaan asas dan prinsip operasi bagi Magnet Kekal Gelung Bergerak (MKGB).

[6 marks]

[6 markah]

QUESTION 3 SOALAN 3

- CLO1
C1 (a) Describe the basic functions of analogue and digital oscilloscope.
Jelaskan fungsi-fungsi asas osiloskop analog dan digital.

[3 marks]

[3 markah]

- CLO2
C3 (b) Refer to Figure B 3(b), determine the peak to peak voltage (V_{PP}), the peak voltage (V_P) and frequency if the Volt/div control is adjusted at 0.5V and Time/div control is adjusted at $50\mu\text{s}$.

Merujuk kepada Rajah B 3(b), tentukan nilai voltan puncak ke puncak (V_{PP}), voltan puncak (V_P) dan frekuensi jika pelaras Volt/div dilaraskan pada $0.5V$ dan pelaras Time/div dilaraskan pada $50\mu s$.

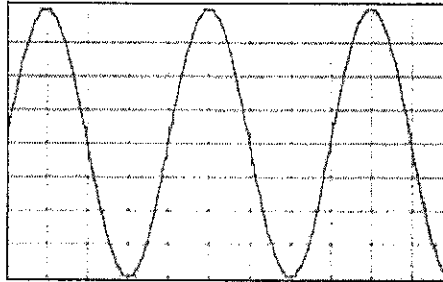


Figure B 3(b)/ Rajah B 3(b)

[6 marks]

[6 markah]

CLO2
C3

- (c) An oscilloscope with Volt/div and Time/div is set to $5mV/div$ and $20\mu sec/div$ respectively and is used to measure two input signals. Figure B3(c) shows the displayed waveform. Calculate Peak to peak voltage (V_{pp}), period 1 cycle (T) and phase angle (θ) for both waveform A and B.

Osiloskop dengan Volt/div dan Time/div ditetapkan pada $5mV/div$ and $20\mu sec/div$ dan ia digunakan untuk mengukur dua isyarat masukan. Rajah B3(c) ditunjukkan dalam gelombang yang dipaparkan. Kirakan Voltan puncak ke puncak (V_{pp}), Tempoh 1kitar lengkap (T) dan beza fasa (θ) untuk gelombang A dan B.

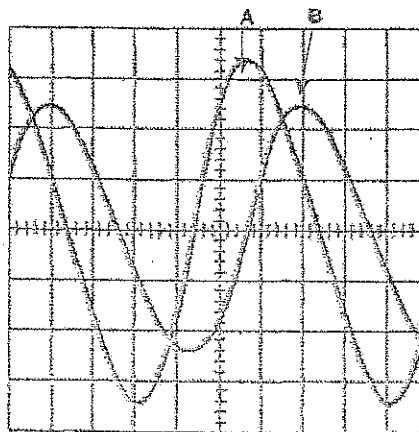


Figure B3(c) / Rajah B3(c)

[6 marks]

[6 markah]

QUESTION 4
SOALAN 4

- CLO1
C1 (a) Define power meters.
Beri definisi Meter Kuasa.
[3 marks]
[3 markah]
- CLO1
C3 (b) Describe basic principle of analogue wattmeter with construction of electro-dynamometer.
Jelaskan prinsip asas meter watt analog dengan binaan meter dynamo Elektro.
[5 marks]
[5 markah]
- CLO2
C3 (c) Illustrate the application of clamp meters in measuring alternating current with a suitable diagram.
Ilustrasikan penggunaan meter clamp dalam mengukur arus ulang alik dengan gambarajah yang sesuai.
[7 marks]
[7 markah]

SECTION C: 30 MARKS
BAHAGIAN C: 30 MARKAH

INSTRUCTION:

This section consists of **TWO (2)** essay questions. Answer **ALL** questions.

ARAHAN:

Bahagian ini mengandungi DUA (2) soalan esei. Jawab SEMUA soalan.

QUESTION 1

SOALAN 1

CLO2
C3

Permanent Magnet Movement Coil(PMMC) instrument with an internal resistance of 10Ω and a full scale deflection current of 10mA is to be used in the design of multirange DC voltmeter with voltage ranges of $0\text{-}10\text{V}$ and $0\text{-}25\text{V}$. Sketch the circuit and express the equations of multiplier resistor. From the equations, calculate the value of the multiplier resistors.

Sebuah instrumen Gegeleung Bergerak Magnet Kekal (GBMK) dengan rintangan dalaman 10Ω dan pesongan semasa skala penuh 10mA digunakan dalam rekabentuk meter voltan AT pelbagai julat dengan julat voltan $0\text{-}10\text{V}$ dan $0\text{-}25\text{V}$. Lukiskan litar tersebut dan nyatakan persamaan perintang pendarab. Dari persamaan, kira nilai perintang pendarab.

[15marks]

[15 markah]

QUESTION 2

SOALAN 2

CLO2
C3

A stable Wheatstone bridge consists of a network of four resistance arms which are R_1 , R_2 , R_3 and R_X . A current is applied to two opposite junctions. The current detector is connected to the other two junctions. Given that the value of $R_1 = 4\text{k}\Omega$, $R_2 = 12\text{k}\Omega$ and $R_3 = 8\text{k}\Omega$. Draw and label the Wheatstone bridge completely. Express the bridge balance equation for R_X and calculate the value of R_X . If R_2 is two times the value of R_1 , find the new value of R_x .

Tetimbang Wheatstone stabil terdiri daripada satu rangkaian yang mempunyai empat rintangan iaitu R_1 , R_2 , R_3 dan R_x . Arus dikenakan ke atas dua persimpangan bertentangan. Pengesan arus disambungkan kepada dua persimpangan lain. Diberi nilai $R_1 = 4k\Omega$, $R_2 = 12k\Omega$ dan $R_3 = 8k\Omega$. Lukis dan labelkan tetimbang Wheatstone dengan lengkap. Nyatakan persamaan bagi perintang R_x dan kira nilai R_x . Jika R_2 adalah dua kali ganda nilai R_1 , cari nilai R_x yang baru.

[15 marks]

[15 markah]

SOALAN TAMAT