

SULIT



**BAHAGIAN PEPERIKSAAN DAN PENILAIAN
JABATAN PENGAJIAN POLITEKNIK
KEMENTERIAN PENDIDIKAN MALAYSIA**

JABATAN KEJURUTERAAN ELEKTRIK

PEPERIKSAAN AKHIR

SESI DISEMBER 2013

EE602: CIRCUIT ANALYSIS

TARIKH : 07 APRIL 2014

TEMPOH : 8.30 AM – 10.30 AM (2 JAM)

Kertas ini mengandungi **SEMBILAN (9)** halaman bercetak.
Bahagian A: Struktur (10 soalan)
Bahagian B: Esei (3 soalan)
Dokumen sokongan yang disertakan : *Laplace Transform Table*

JANGAN BUKA KERTAS SOALAN INI SEHINGGA DIARAHKAN

(CLO yang tertera hanya sebagai rujukan)

SULIT

©COPYRIGHT PMU

SECTION A : 40 MARKS

BAHAGIAN A : 40 MARKAH

INSTRUCTION:

This section consists of TEN (10) structured questions. Answer ALL questions.

ARAHAN:

Bahagian ini mengandungi SEPULUH (10) soalan berstruktur. Jawab semua soalan.

QUESTION 1

CLO1
C3

Solve Mesh 1 and Mesh 2 equations for the circuit in Figure A1.

SOALAN 1

Selesaikan persamaan Jaringan 1 dan Jaringan 2 bagi litar pada Rajah A1.

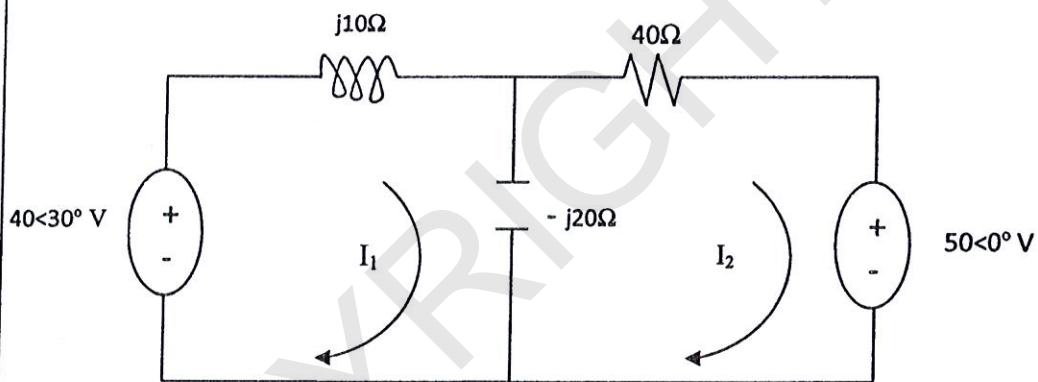


Figure A1 / Rajah A1

(4 marks)

(4 markah)

QUESTION 2

CLO1
C3Referring to Figure A2 below, calculate the value of voltage, V .

SOALAN 2

Merujuk kepada Rajah A2 di bawah, kirakan nilai bagi voltan, V .

[4 Marks]

[4 Markah]

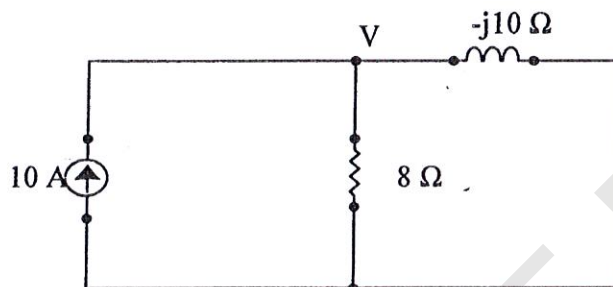


Figure A2 / Rajah A2

QUESTION 3

CLO1
C3Calculate the value of Norton Current, I_N in diagram A4 at terminal $a-b$

SOALAN 3

Kirakan nilai arus Norton, I_N di dalam Rajah A4 pada terminal $a-b$.

[4 marks]

[4 markah]

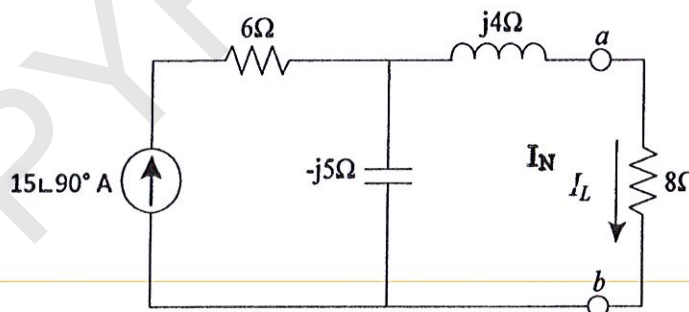


Figure A3 / Rajah A3

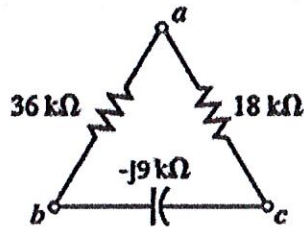
QUESTION 4CLO1
C2Referring to Figure A4, transform the circuit from Δ to Y configuration.**SOALAN 4**Berdasarkan Rajah A4, tukarkan litar daripada konfigurasi Δ kepada konfigurasi Y.

Figure A4 / Rajah A4

[4 marks]

[4 markah]

QUESTION 5CLO1
C3Solve the Laplace Transformation of the following functions $f(t)$ by using Laplace Transformation Table.**SOALAN 5**Dapatkan Jelmaan Laplace bagi fungsi $f(t)$ berikut dengan menggunakan Jadual Jelmaan Laplace.

$$f(t) = 3e^{-2t} + 4 \cos 4t - 9 \sin 3t$$

[4 marks]

[4 markah]

QUESTION 6CLO1
C3Calculate the Inverse Laplace Transformation of the following function $F(s)$ by using Partial Fraction.**SOALAN 6**Kirakan Jelmaan Laplace Songsang bagi fungsi $F(s)$ berikut dengan menggunakan Pecahan Separa.

$$F(s) = \frac{s+10}{s^2-4s-12}$$

[4 marks]


[4 markah]

©COPYRIGHT PMU

QUESTION 10

CLO2
C3

Produce the analytical expression for the periodic waveform shown in Figure A10.

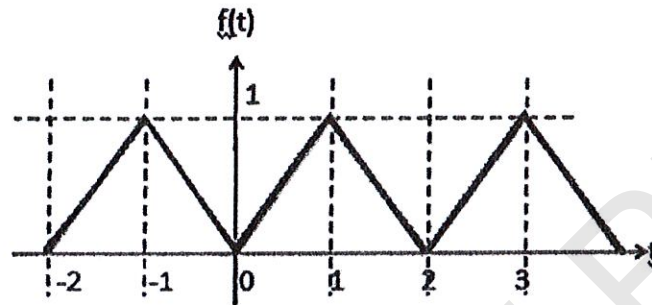*SOALAN 10**Dapatkan ungkapan analitik bagi gelombang berkala seperti ditunjukkan di Rajah A10.*Figure A10 / *Rajah A10*

[4 marks]

[4 markah]

SECTION B : 60 MARKS
BAHAGIAN B : 60 MARKAH

INSTRUCTION:

This section consists of **THREE (3)** essay questions. Answer **ALL** questions.

ARAHAN:

Bahagian ini mengandungi **TIGA (3)** soalan esei. Jawab **SEMUA** soalan.

QUESTION 1
SOALAN 1

CLO2
C3

(a) Calculate the value of I_x in the circuit in Figure B(1a) using Thevenin Analysis.

Kirakan nilai I_x bagi litar dalam Rajah B(1a) menggunakan Analisa Thevenin.

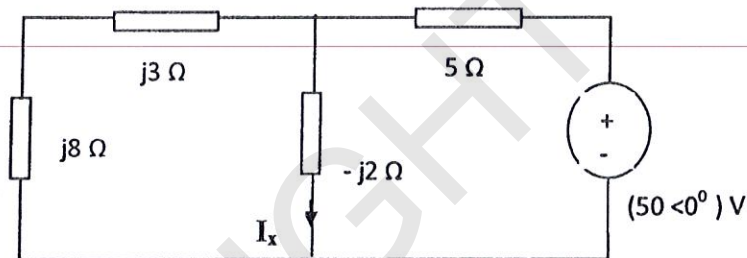


Figure B(1a) / Rajah B(1a)

[10 marks]
[10 markah]

CLO2
C3

(b) Calculate the value of I_x in the circuit in Figure B(1b) using Mesh Analysis.

Kirakan nilai I_x bagi litar dalam Rajah B(1b) menggunakan Analisa Mesh.

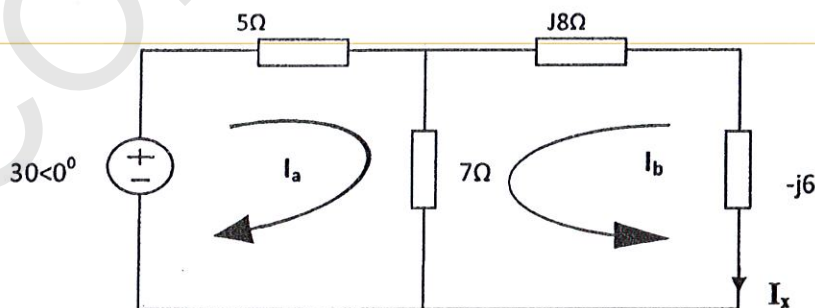


Figure B(1b) / Rajah B(1b)

[10 marks]
[10 markah]

CLO3
C3QUESTION 2
SOALAN 2

(a) Solve $\frac{dx}{dt} - 4x = 8$, given $x = 2$ [or $f(0)=2$] when $t=0$

Selesaikan $\frac{dx}{dt} - 4x = 8$, diberi $x = 2$ pada masa $t=0$

[9 marks]

[9 markah]

(b) Based on Figure B(2b), calculate the value of $i(t)$ by using Laplace transformation when S1 switch is closed. Given $t = 0$, $q_0 = 2.5\text{mC}$

Berdasarkan Rajah B(2b), kira nilai $i(t)$ dengan menggunakan Jelmaan Laplace apabila suiz S1 ditutup. Diberi pada masa $t=0$, $q_0 = 2.5\text{mC}$

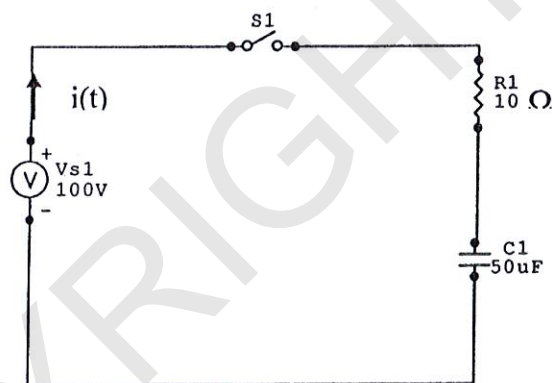


Figure B(2b)

[11 marks]

[11 markah]

QUESTION 3

SOALAN 3

CLO3
C3

- a) Produce the trigonometric Fourier series expression.
Dapatkan persamaan Siri Fourier Trigonometri.

[10 marks]
[10 markah]

- b) Referring to Diagram B(3b), calculate A_0 .
Merujuk kepada Rajah B(3b), kirakan nilai A_0 .

[10 marks]
[10 markah]

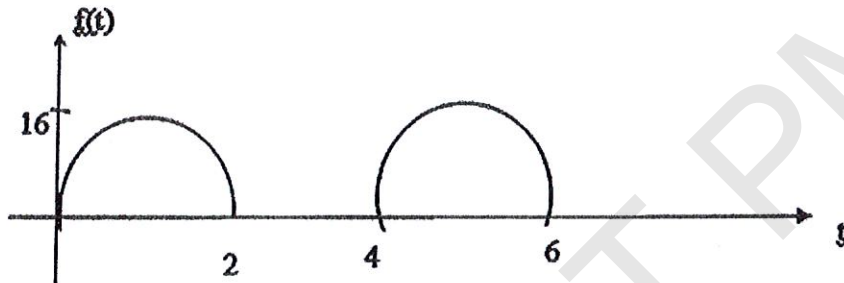


Figure B(3b) / Rajah B(3b)

SOALAN TAMAT

connection	Phase voltages/currents	Line voltages/currents
Y - Δ	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ $I_{AB} = V_{AB} / Z_\Delta$ $I_{BC} = V_{BC} / Z_\Delta$ $I_{CA} = V_{CA} / Z_\Delta$	$V_{ab} = V_{AB} = \sqrt{3}V_p \angle 30^\circ$ $V_{bc} = V_{BC} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{CA} = V_{ab} \angle +120^\circ$ $I_a = I_{AB} \sqrt{3} \angle -30^\circ$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Δ - Y	$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$	Same as phase voltages
	same as line currents	$I_a = \frac{V_n \angle -30^\circ}{\sqrt{3}Z_Y}$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$

<p>First derivative :</p> $\mathcal{L}[f'(t)] = s \mathcal{L}[f(t)] - f(0)$	<p>Overview of Fourier analysis :</p> $f(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos(2\pi n f_0 t) + b_n \sin(2\pi n f_0 t))$
<p>Second derivative :</p> $\mathcal{L}[f''(t)] = s^2 \mathcal{L}[f(t)] - s f(0) - f'(0)$	<p>Alternative form of the Fourier series :</p> $A_n = \sqrt{a_n^2 + b_n^2} \quad \text{and} \quad \phi_n = \tan^{-1} \frac{-b_n}{a_n}$

	$\mathcal{L}^{-1}\{F(s)\} = f(t)$	$F(s) = \mathcal{L}\{f(t)\}$
i.	1	$\frac{1}{s}$
ii.	k	$\frac{k}{s}$
iii.	e^{at}	$\frac{1}{s-a}$
iv.	$\sin at$	$\frac{a}{s^2 + a^2}$
v.	$\cos at$	$\frac{s}{s^2 + a^2}$
vi.	t	$\frac{1}{s^2}$
vii.	t^2	$\frac{2!}{s^3}$
viii.	t^n	$\frac{n!}{s^{n+1}}$
ix.	$\sinh at$	$\frac{a}{s^2 - a^2}$
x.	$\cosh at$	$\frac{s}{s^2 - a^2}$
xi.	$e^{at} t^n$	$\frac{n!}{(s-a)^{n+1}}$
xii.	$e^{at} \sin \omega t$	$\frac{\omega}{(s-a)^2 + \omega^2}$
xiii.	$e^{at} \cos \omega t$	$\frac{s-a}{(s-a)^2 + \omega^2}$
xiv.	$e^{at} \sinh \omega t$	$\frac{\omega}{(s-a)^2 - \omega^2}$
xv.	$e^{at} \cosh \omega t$	$\frac{s-a}{(s-a)^2 - \omega^2}$

Waveform	Fourier coefficients	waveform	Fourier coefficients
Constant (dc)	$\alpha_0 = A$ $\alpha_n = 0$ all n $b_n = 0$ all n	Sawtooth wave	$\alpha_0 = \frac{A}{2}$ $\alpha_n = 0$ all n $b_n = -\frac{A}{n\pi}$ all n
Cosine wave	$\alpha_0 = 0$ $\alpha_1 = A$ $\alpha_n = 0$ n $\neq 1$ $b_n = 0$ all n	Triangular wave	$\alpha_0 = 0$ $\alpha_n = \frac{8A}{(n\pi)^2}$ n odd $\alpha_n = 0$ n even $b_n = 0$ all n
Sine wave	$\alpha_0 = 0$ $\alpha_n = 0$ all n $b_1 = A$ $b_n = 0$ n $\neq 1$	Half – wave rectified sine wave	$\alpha_0 = \frac{A}{\pi}$ $\alpha_n = \frac{2A/\pi}{1-n^2}$ n even $\alpha_n = 0$ n odd $b_1 = \frac{A}{2}$ n = 1 $b_n = 0$ n $\neq 1$
Square wave	$\alpha_0 = 0$ $\alpha_n = 0$ all n $b_n = \frac{4A}{n\pi}$ n odd $b_n = 0$ n even	Full – wave rectified sine wave	$\alpha_0 = \frac{2A}{\pi}$ $\alpha_n = \frac{4A/\pi}{1-n^2}$ n even $\alpha_n = 0$ n odd $b_n = 0$ all n
Rectangular pulse	$\alpha_0 = \frac{AT}{T_0}$ $\alpha_n = \frac{2A}{n\pi} \sin\left(\frac{n\pi T}{T_0}\right)$ $b_n = 0$ all n	Parabolic wave	$\alpha_0 = 0$ $\alpha_n = 0$ all n $b_n = \frac{32A}{(n\pi)^3}$ n odd $b_n = 0$ n even

©COPYRIGHT PMU