

ELECTRICAL CIRCUIT 1

CAPACITORS

CAPACITANCE



ROHAILA BINTI MOHD RADI
SAFIRA BINTI DIN
FADZLIDA BINTI SHAMSUDIN

ELECTRICAL CIRCUIT 1

CAPACITORS

CAPACITANCE

QUICK NOTES & EXERCISES

ROHAILA BINTI MOHD RADI
FADZLIDA BINTI SHAMSUDIN
SAFIRA BINTI DIN



First Edition 2025

@ Perpustakaan Negara Malaysia, 2025

EDITOR:

Rohaila Binti Mohd Radi

AUTHORS:

Rohaila Binti Mohd Radi

Fadzlida binti Shamsudin

Safira Binti Din

All rights reserved. No part of this publication may be reproduced, stored in a retrieval system, or transmitted in any form or by any means, electronic, mechanical, photocopying, recording, or otherwise, without the prior permission of the Director General of the National Library of Malaysia.

PUBLISHED BY:

Politeknik Port Dickson

KM 14 Jalan Pantai, 71050 Si Rusa

Negeri Sembilan

Jabatan Kejuruteraan Elektrik



06-662 2023 (Librarian)

06-662 2048 (Counter)

suzilawati@polipd.edu.my



Cataloguing-in-Publication Data

Perpustakaan Negara Malaysia

A catalogue record for this book is available
from the National Library of Malaysia

eISBN 978-629-7643-70-0

ACKNOWLEDGEMENT

PATRON

Tuan Haji Wan Zulkifly bin Wan Zakaria
Director Port Dickson Polytechnic

ADVISORS

Ts. Dr. Engku Shahrulerizal bin Engku Ab Rahman
Deputy Director (Academic), Port Dickson Polytechnic

Izwan Kamal bin Abdul Wahab
Head of Electrical Engineering Department,
Port Dickson Polytechnic

EDITOR

Rohaila Binti Mohd Radi

WRITERS

Rohaila Binti Mohd Radi
Fadzlida binti Shamsudin
Safira Binti Din

We would like to convey our utmost gratitude to the Department of Polytechnics and Community College Education (DPCCE), particularly the E-Learning and Instructional Division for funding our e-book project. We hereby declare that this module is our original work. To the best of our knowledge, it contains no materials previously written or published by another person. However, if there is any, due acknowledgement and credit are mentioned accordingly in the e-book.

PREFACE

This book introduces the basics of capacitors and their role in electric/electronic circuits. It covers the structure, functionality, and behavior of capacitors in various configurations. By examining the principles of capacitance, dielectric properties, and the equations that govern capacitor performance, readers will develop the ability to analyze and apply these components in practical scenarios. The charging and discharging processes are explained with clarity to foster intuitive and technical mastery of time-dependent circuit behavior.

This chapter blends foundational theory with hands-on insight, making it ideal for students and anyone aiming to understand capacitors in a simple way.

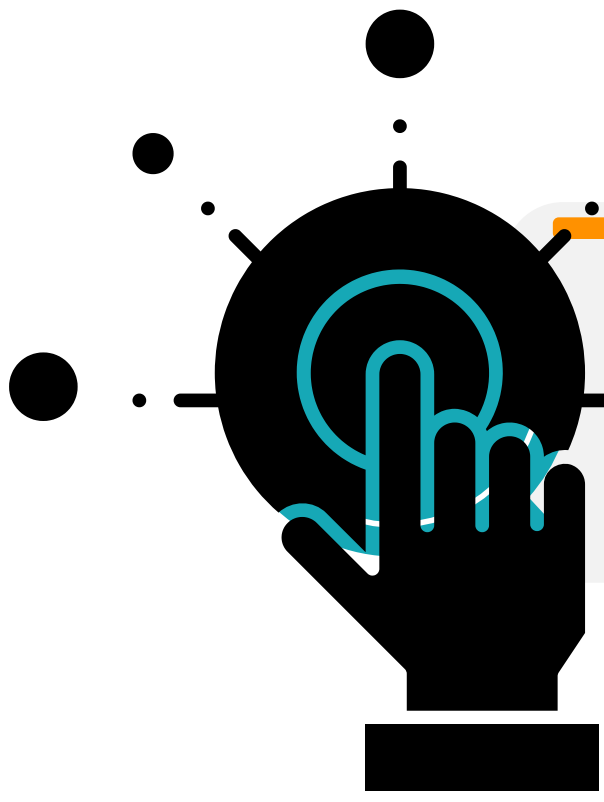


TABLE OF CONTENTS

CAPACITORS AND CAPACITANCE

CAPACITOR

8

CAPACITOR CONSTRUCTION

9

CAPACITORS AND CAPACITANCE IN A CIRCUIT

10

CAPACITOR APPLICATIONS

11

TYPES OF CAPACITORS

12

CAPACITIVE CIRCUIT QUANTITY

13

DIELECTRIC MATERIAL

16

PERMITTIVITY

20

CAPACITANCE EQUIVALENT CIRCUITS FOR SERIES AND PARALLEL

31

CIRCUITS WITH CAPACITIVE

32

- CHARGING AND DISCHARGING IN A CAPACITO

CAPACITOR





symbol



- Capacitor is an electrical component that stores electrical charge/energy.
- It stores electrical energy in the form of an electric field between its plates
- capacitors can help stabilize voltage and reduce noise.

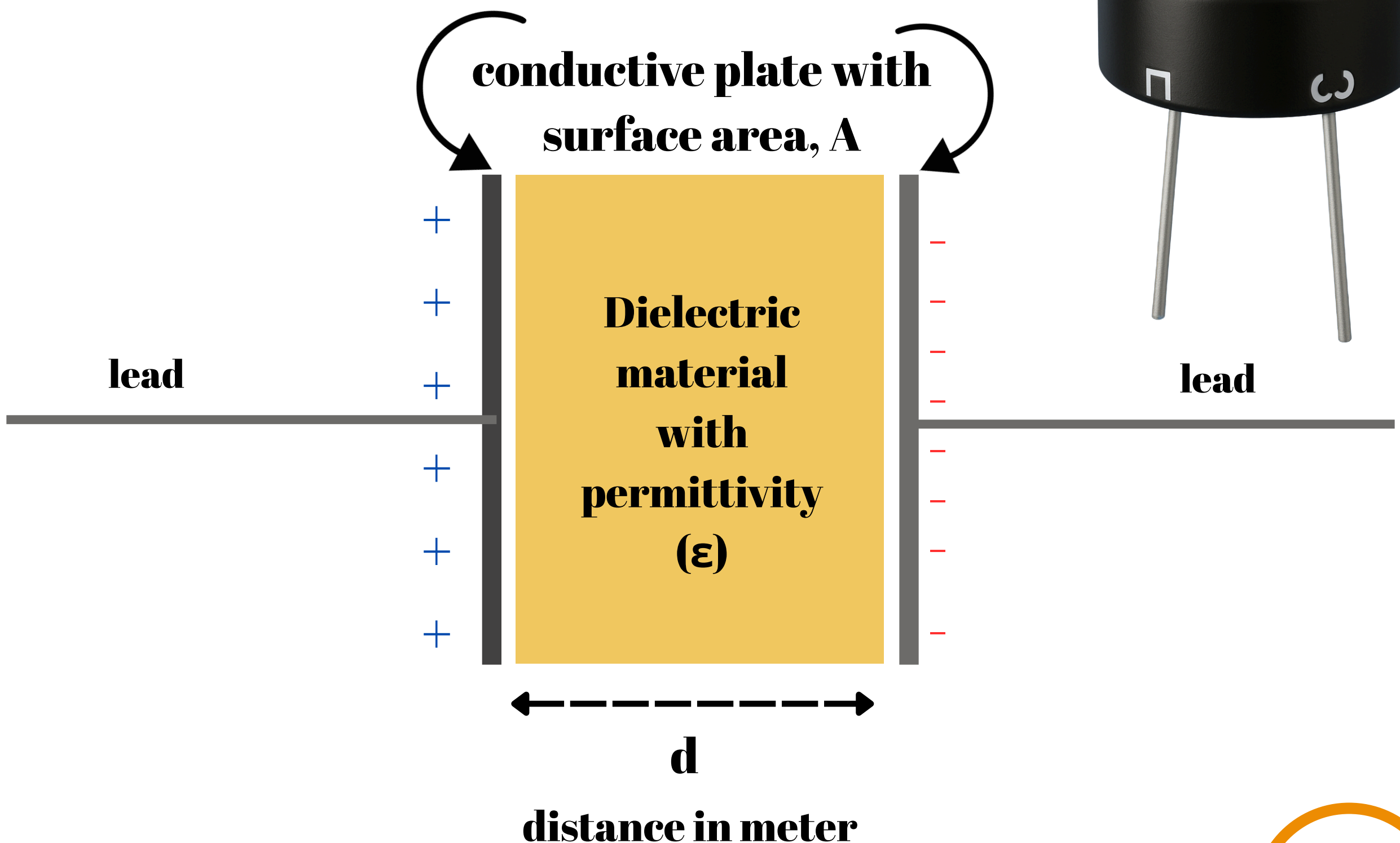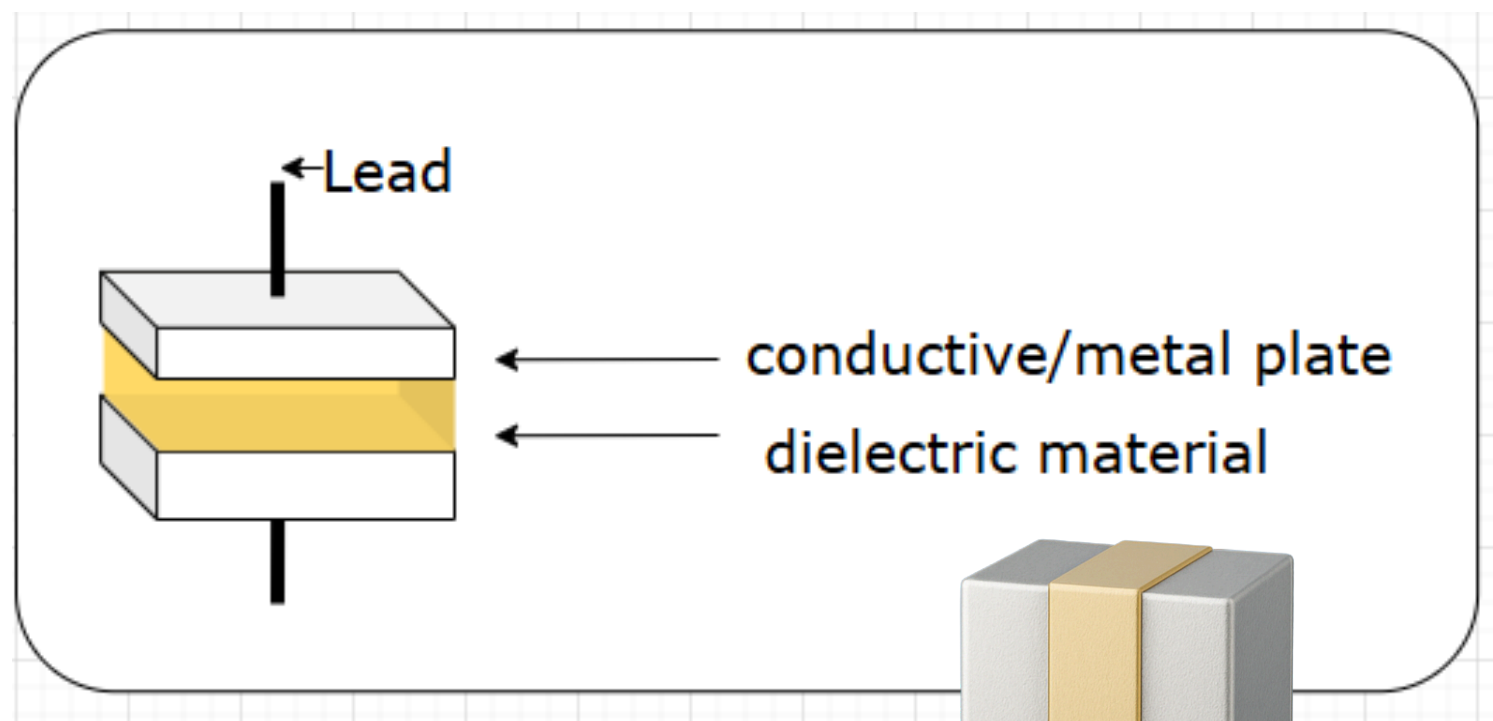A Capacitor consists of two conducting plates separated by an insulator (or dielectric).



CONSTRUCTION

CAPACITOR

HOW IT WORKS

A capacitor is made of two conductive metal plates separated by an insulating material called a dielectric. When voltage is applied across the plates, one plate accumulates positive charge, and the other collects an equal amount of negative charge. The electric field created between these plates stores energy.


Capacitors are often classified based on the type of dielectric.

dielectric (ceramic, paper, vacuum) determines the capacitor's performance.

Permittivity (ϵ) describes how much a dielectric material permits electric field lines to pass through it.

$$\epsilon = \epsilon_r \times \epsilon_0$$

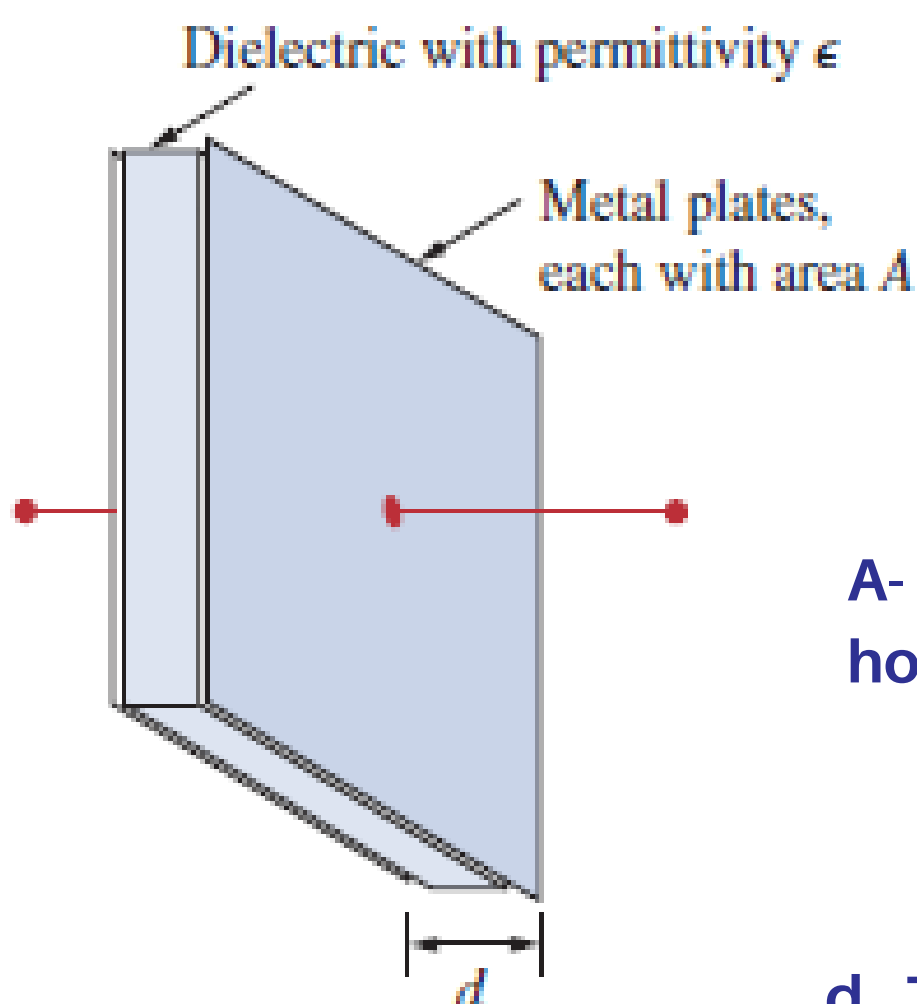- Vacuum Permittivity (ϵ_0):
- The permittivity of free space is $8.85 \times 10^{-12} \text{F/m}$
- Relative Permittivity (ϵ_r)
- Absolute Permittivity (ϵ) - The actual permittivity of a material.



the conducting plates : aluminium foil

The metal plates store the electric charges.

A- the larger the plate area, the more charge it can hold.

d, The closer the plates, the stronger the electric field and higher the capacitance.

Figure 6.1
A typical capacitor.

The distance between the plates, their surface area, and the type of dielectric between them determine how much charge they can store (the capacitance).



CAPACITOR CONSTRUCTION


- Metal plates serve as surfaces where electric charge can accumulate.
- creating an electric field between them.

dielectric material
(mica, paper, glass, ceramic, other non conductive material)



d , distance in meter

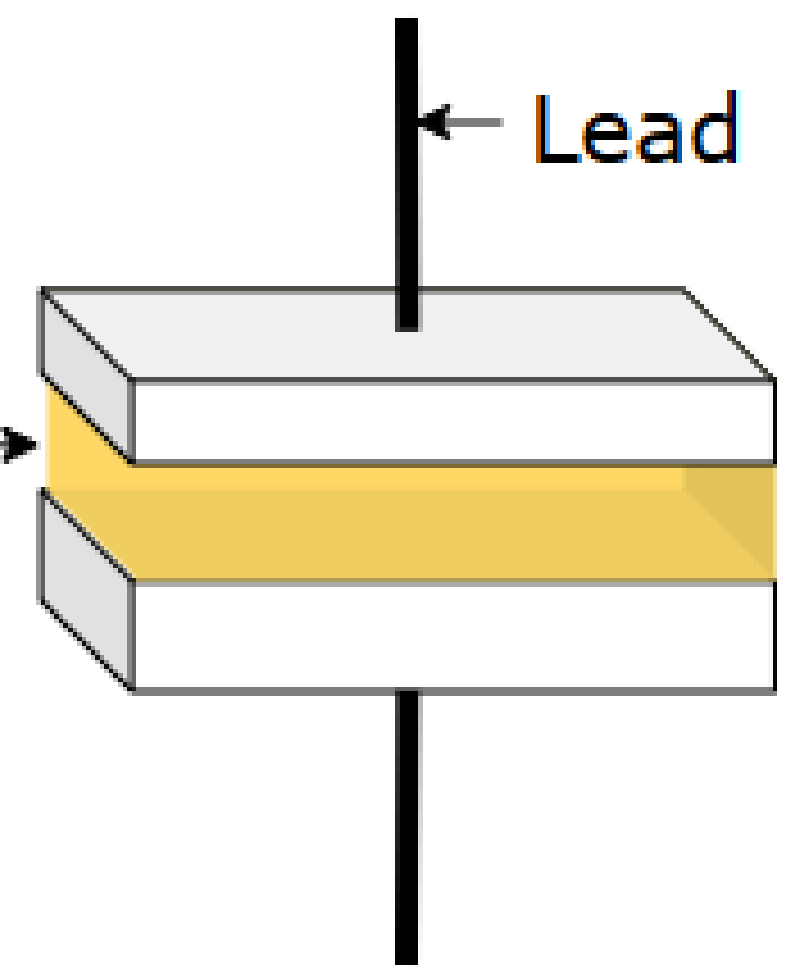Each material has its own **permittivity, ϵ**




Conductive plate/Metal plate
(aluminium, copper, silver, others)

cross sectional area, A in meter


width

length

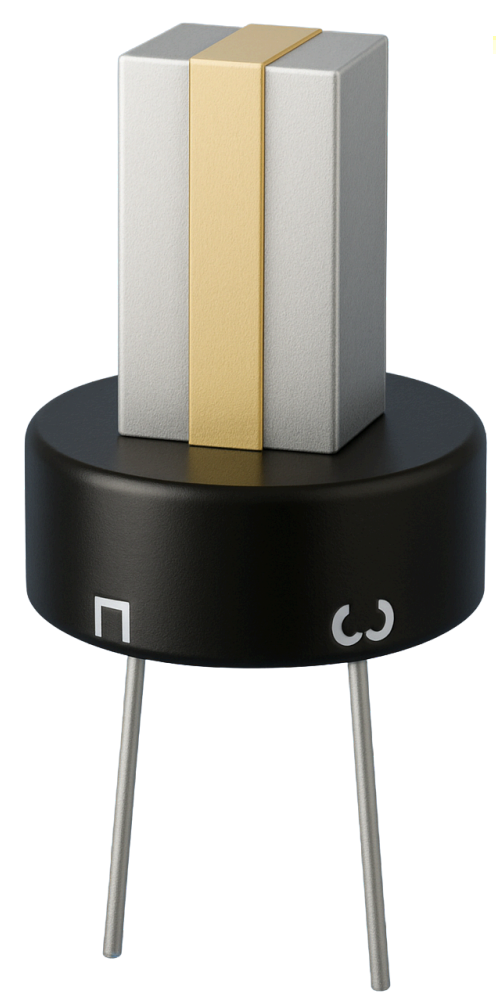

- dielectric is an insulator, not allow current to flow through it easily
- allows more charge to accumulate on the plates when its molecules is polarized

CAPACITORS & CAPACITANCE IN A CIRCUIT

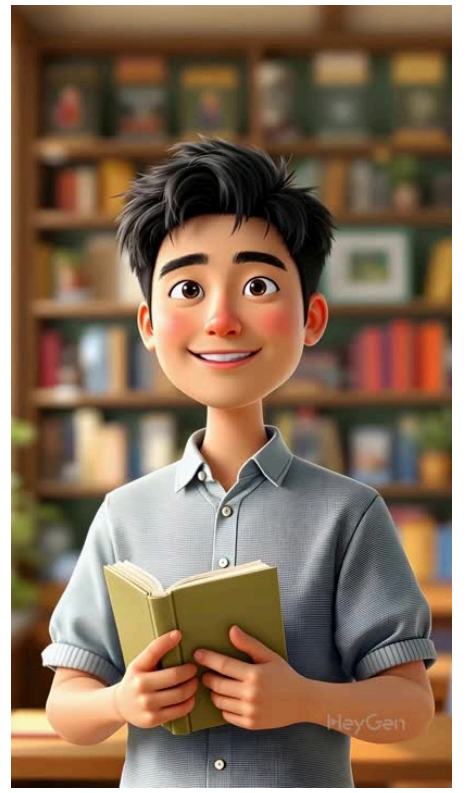

Capacitor, C

- A capacitor is a passive element designed to store energy in its electric field.
- A capacitor consists of two conducting plates separated by an insulator (or dielectric).
- The amount of charge stored, represented by Q , is directly proportional to the applied voltage and can be expressed mathematically as :

$$Q = Cv$$


- Q is the electric charge stored on the capacitor (in coulombs, C),
- C is the capacitance of the capacitor (in farads, F),
- V is the voltage across the capacitor (in volts, V)

Capacitance, unit: Farad



- The property of a CAPACITOR to store electricity in a form of electric charge is called its CAPACITANCE, measured in Farad (F).
- Capacitance is the ratio of the charge on one plate of a capacitor to the voltage difference between the two plates, measured in farads (F).

CAPACITOR APPLICATIONS

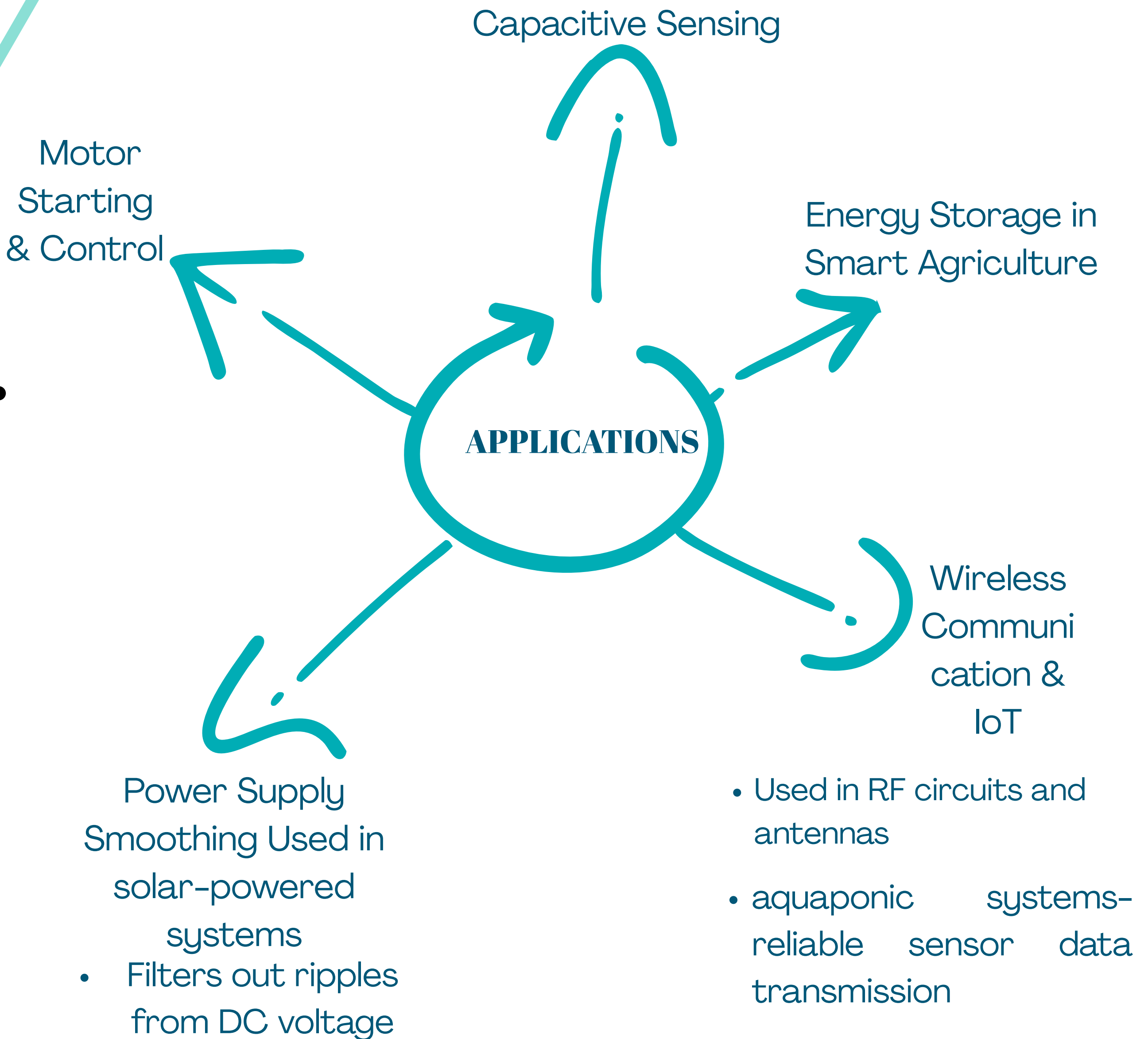


HOW CAPACITORS STORE ENERGY

Capacitors store energy by accumulating electric charge on their plates.

The electric field between the plates holds this energy.

CAPACITOR APPLICATIONS

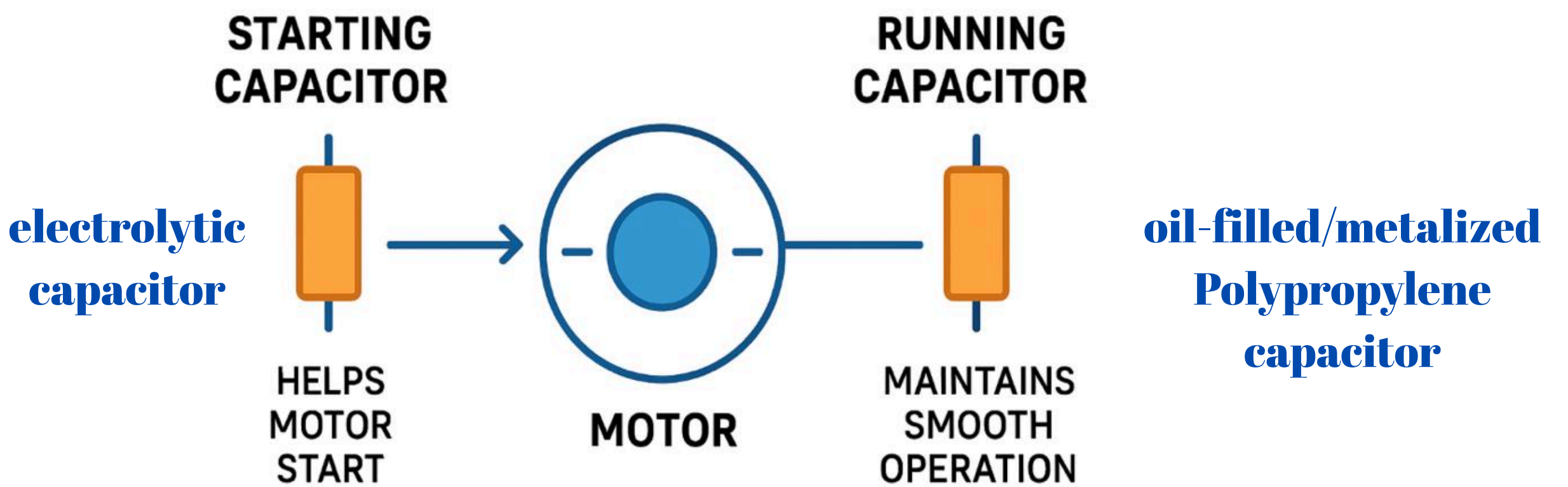FUNCTION OF CAPACITOR IN AIR CONDITIONING COMPRESSOR



Fluorescent Lamps




Oil-Filled Capacitor

Metallized Polypropylene Film Capacitor

Electrolytic Capacitor

- **Power Factor Correction: Improves efficiency by reducing reactive power**
- **boosting voltage**
- **Noise Reduction**

TYPES OF CAPACITOR

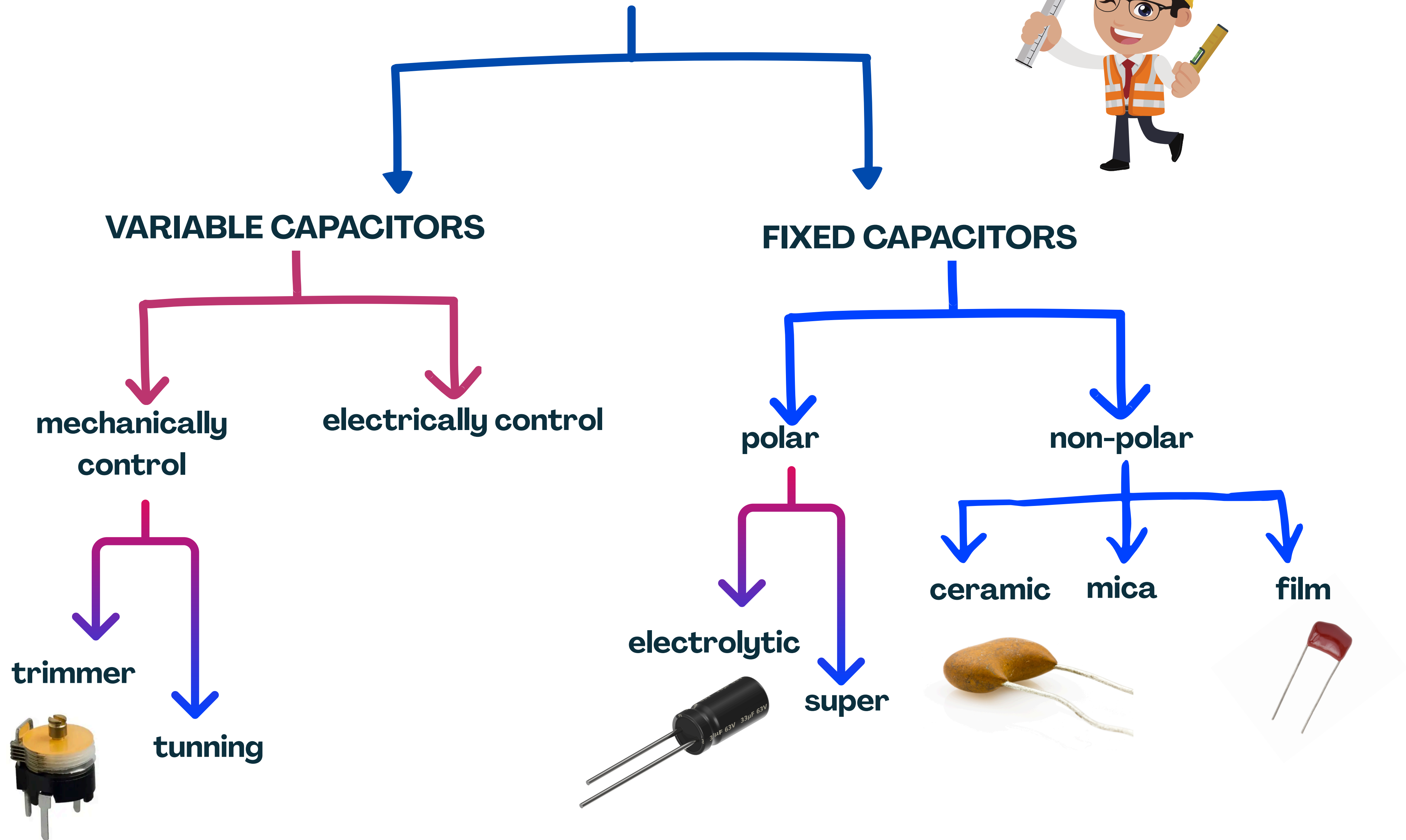

TYPES OF CAPACITOR

Feature	Fixed Capacitor	Variable (Flexible) Capacitor
Capacitance Value	Constant / Cannot be changed	Can be adjusted / changed manually or automatically
Structure	Simple, compact	More complex, with movable parts
Polarity	Can be polarized or non-polarized	Usually, non-polarized
Common Types	Ceramic, Electrolytic, Film, Tantalum	Tuning Capacitor, Trimmer Capacitor
Application	Power supply, filtering, decoupling	Radio tuning, oscillators, frequency adjustment
Cost	Generally cheaper	Usually more expensive
Size	Small to large	Typically, small



Non-Polarized Capacitor



Polarized Capacitor



Variable Capacitor

CAPACITIVE CIRCUIT

CAPACITIVE CIRCUIT QUANTITY

PERMITTIVITY

- Permittivity is the ability of a material to store an electric field in the polarization of the medium.
- The ratio of electric flux density (D) to the electric field strength (E) is called absolute permittivity (ϵ) of a dielectric and can be expressed as

$$\epsilon = \frac{D}{E} \text{ (Unit : } \frac{\text{Farad}}{\text{metre}} \text{)}$$

ELECTRIC FLUX (Φ)


- Known as the total of electric lines of force that moves out from positive charge in electric field
- electric flux, ϕ is measured in coulombs
- electric flux is propotional with electric field line

$$\therefore \text{Electric Flux, } \phi = \text{Charge, } Q$$

ELECTRIC FIELD STRENGTH (E)

- the ratio between the potential difference (V) or voltage and the thickness of the dielectric (d), it can be expressed as
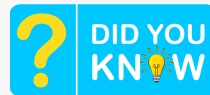
$$E = \frac{V \text{ (unit:Volt)}}{d \text{ (unit:metre)}}$$



voltage gradient/potential gradient
= unit is Volt/meter
A **voltage gradient** is a difference in electrical potential across a distance or space


ELECTRIC FLUX DENSITY (D)

Electric flux density is the ratio between the charge of the capacitor and the surface area of the capacitor plates and can be expressed as

$$D = \frac{Q \text{ (unit:Coulomb)}}{A \text{ (unit:metre}^2\text{)}}$$


FACTOR INFLUENCE CAPACITANCE
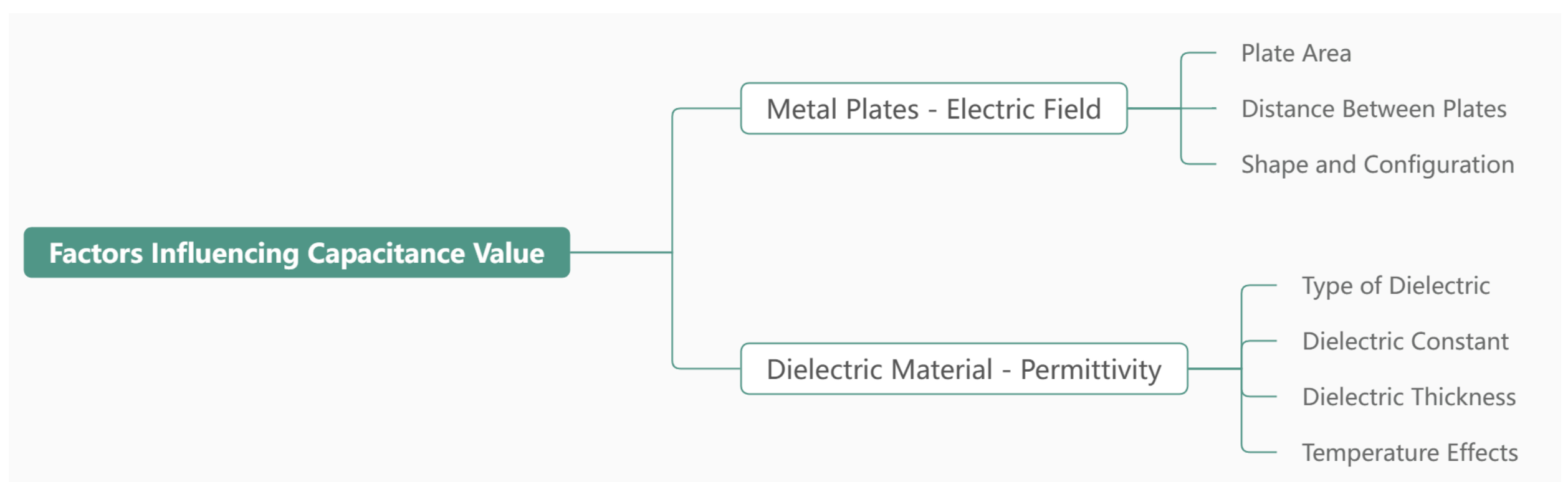
$$\text{capacitance, } C = \frac{Q}{V_c} = \frac{\epsilon_0 \epsilon_r A}{d} \text{ (unit : F)}$$






CAPACITIVE CIRCUIT

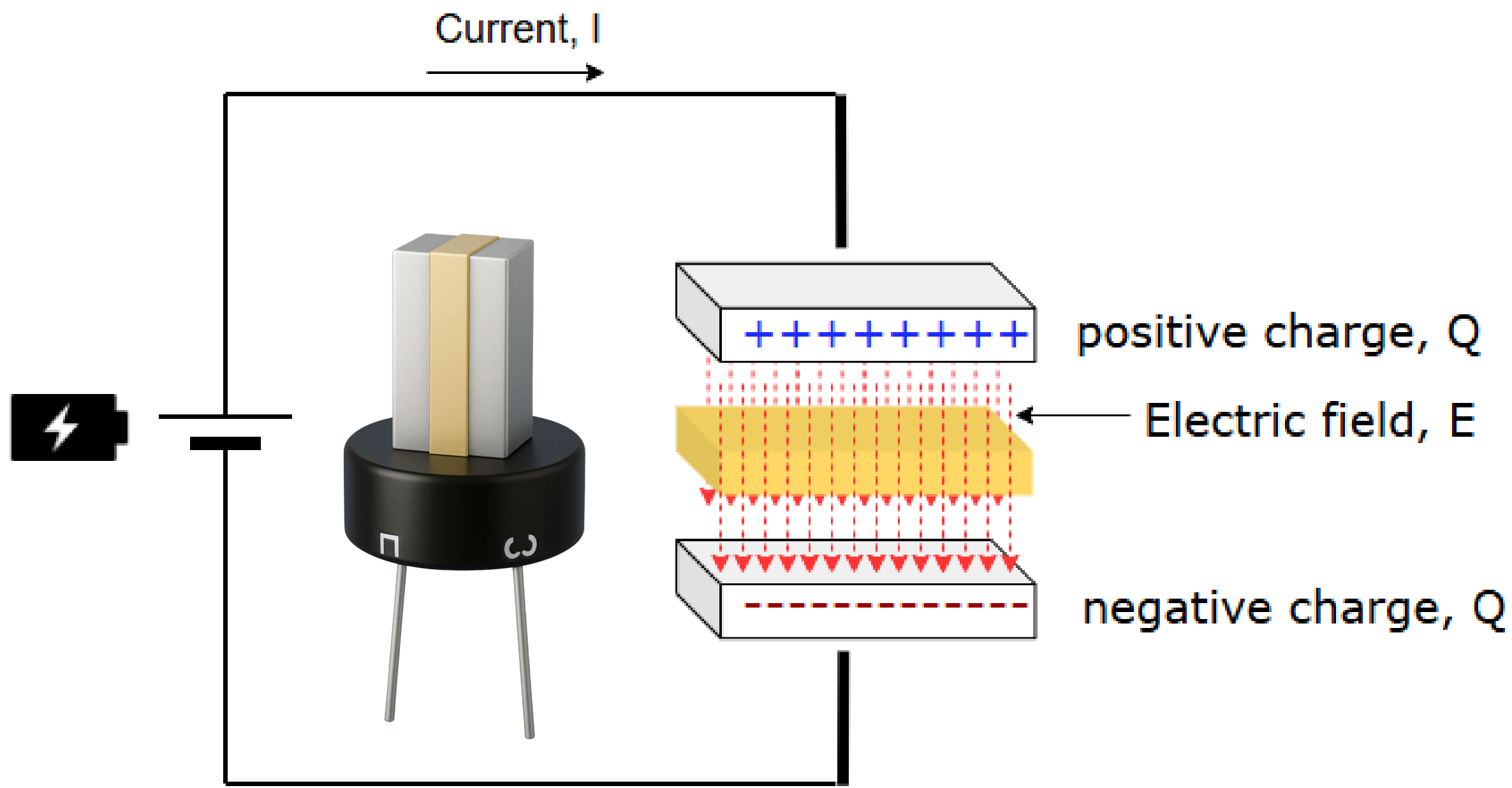



when a voltage is applied across a capacitor's plates

HOW CHARGE CAN BE STORED?

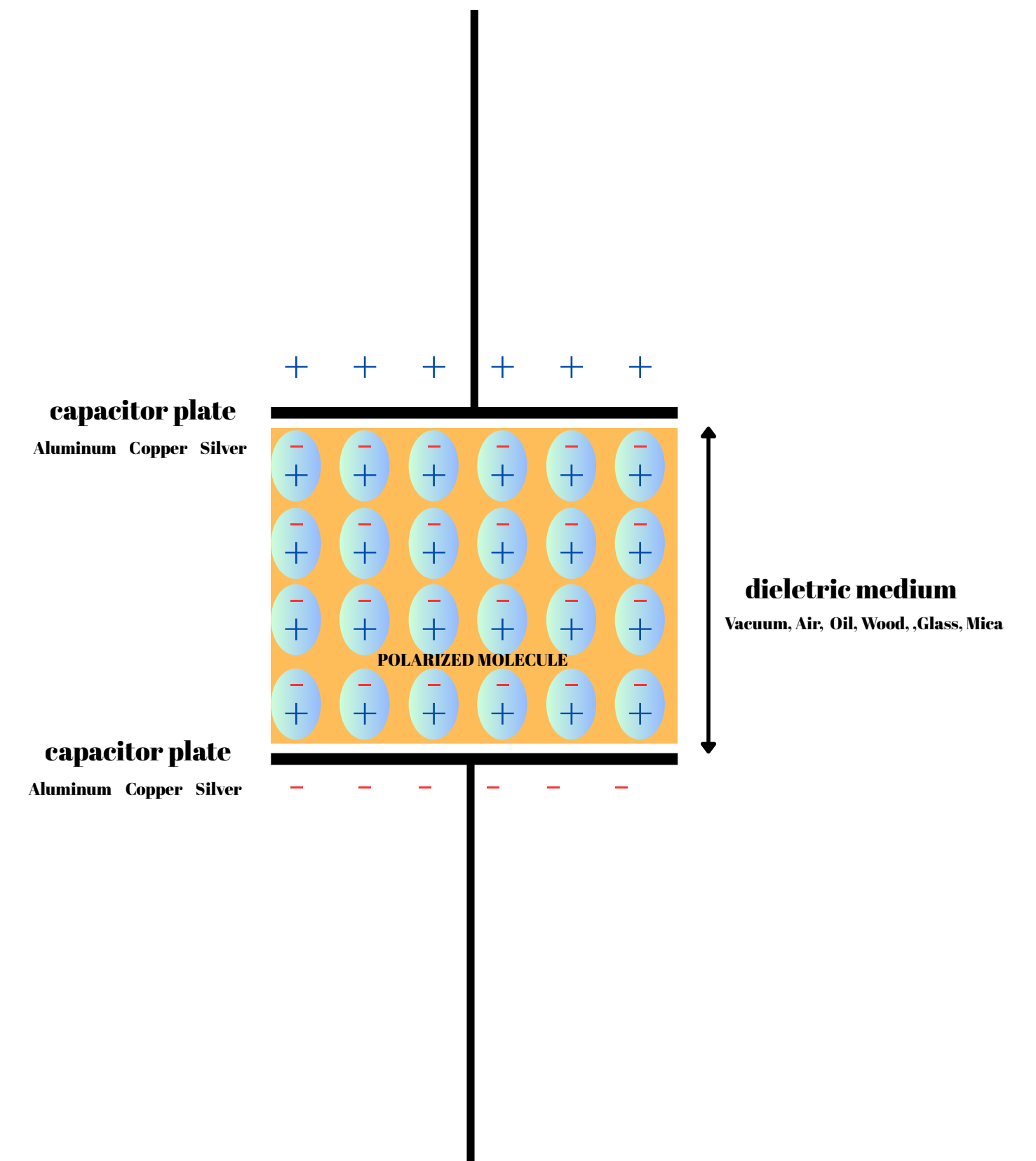

Charge separation → Electric field formation → Dielectric polarization → charge can be stored


CAPACITIVE CIRCUIT

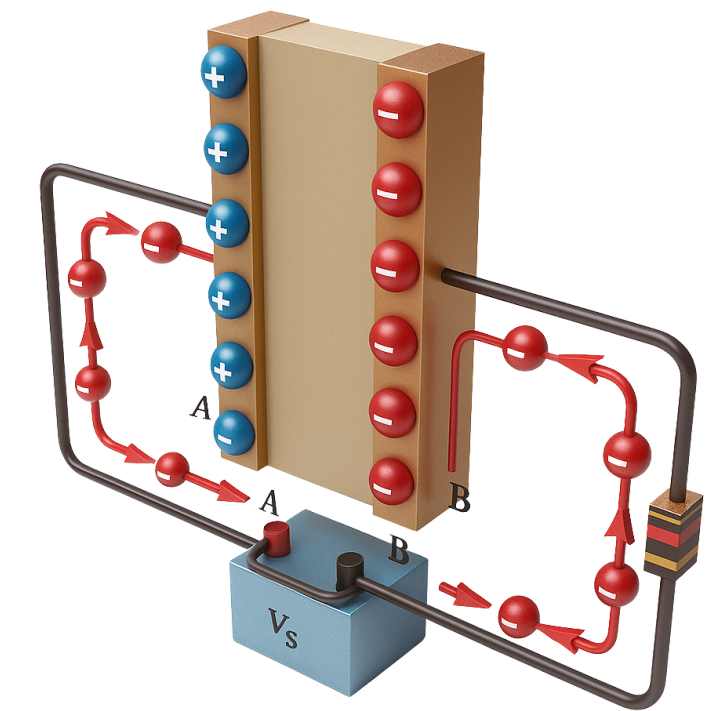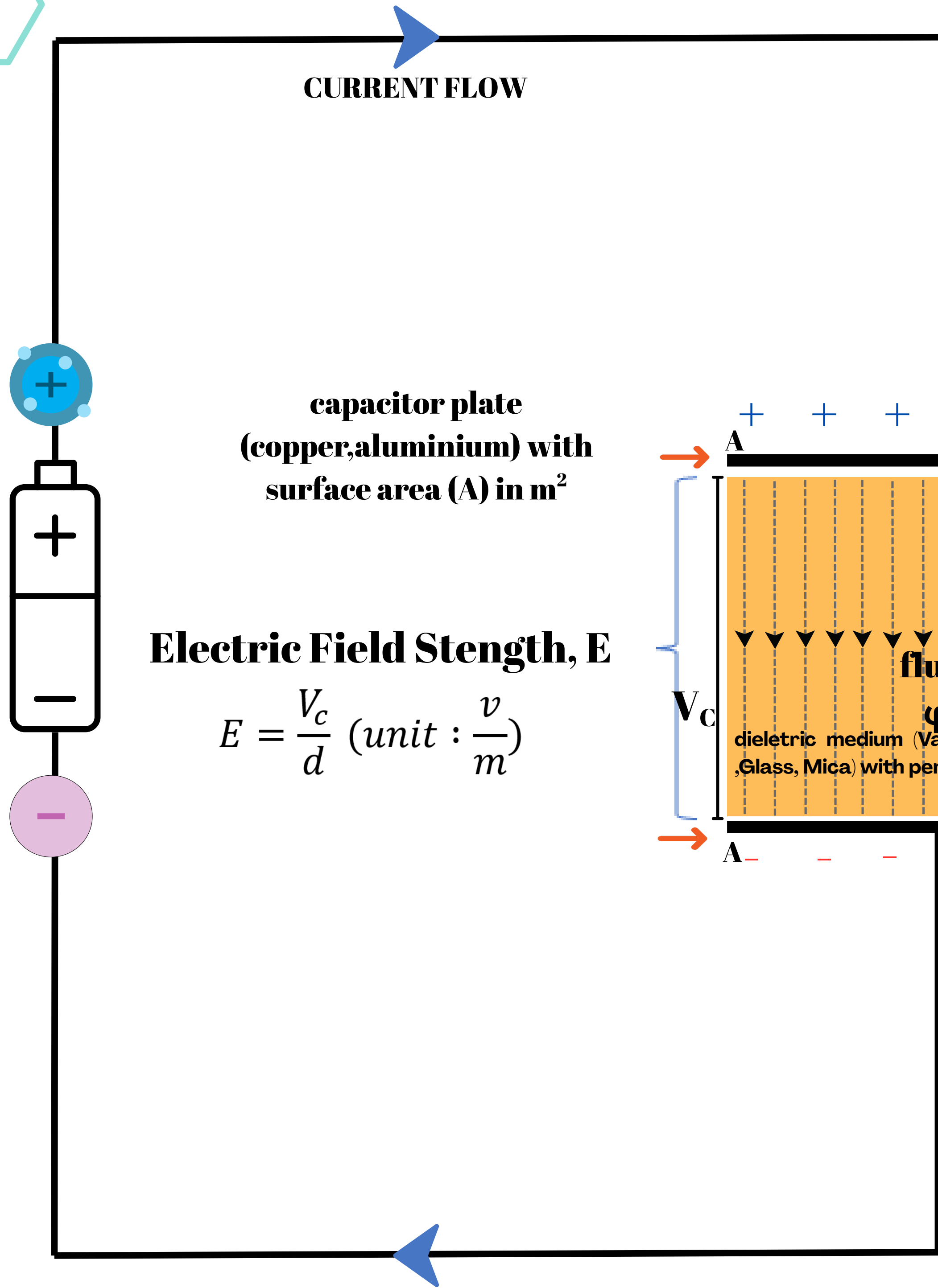

electrons flow from plate A to plate B as the capacitor charges when connected to a battery.

Electric Field Stength, E
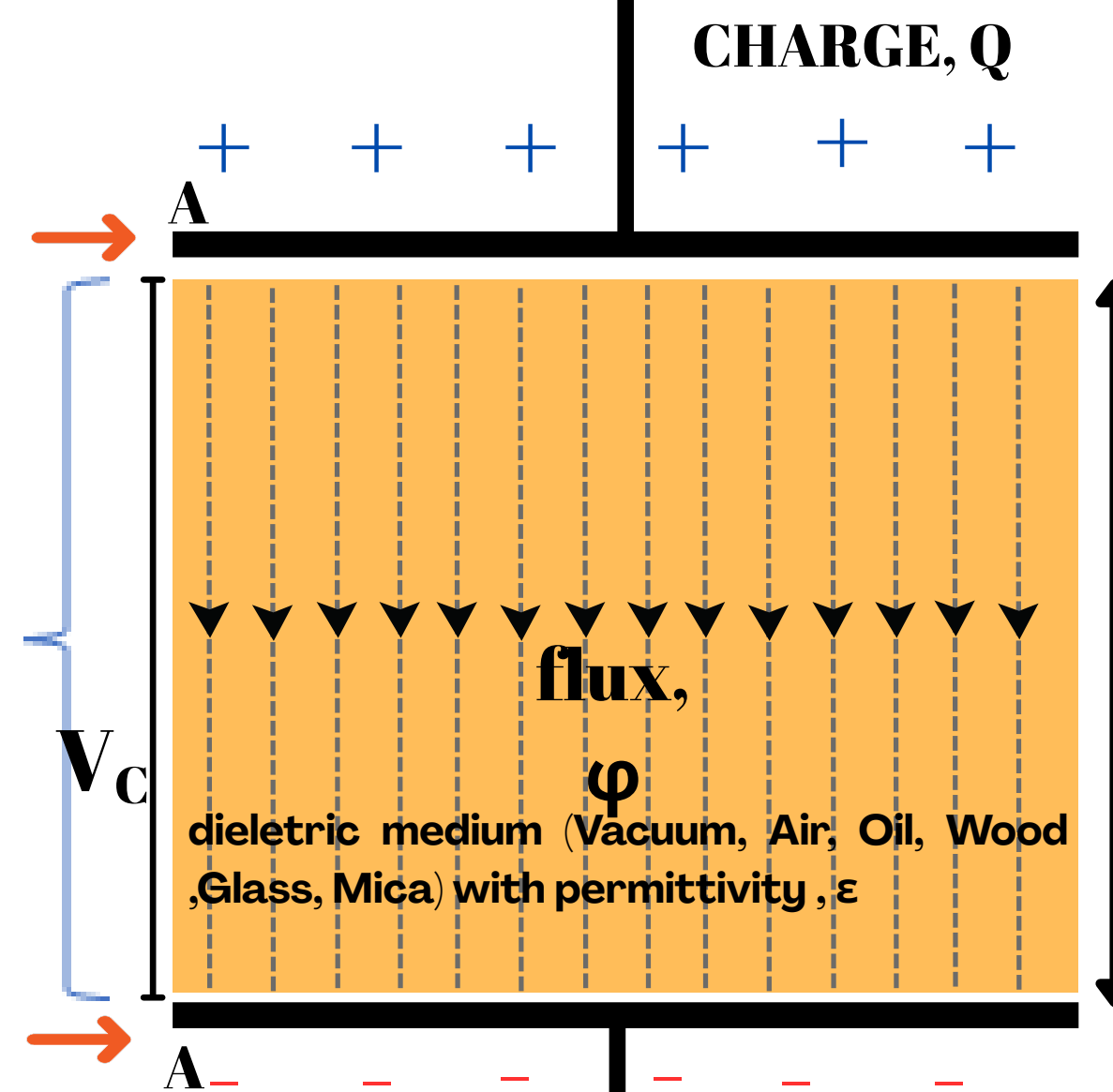
$$E = \frac{V_c}{d} \text{ (unit : } \frac{v}{m} \text{)}$$



d : distance/dielectric thicknes in meter

$$\epsilon = \epsilon_0 \times \epsilon_r = \frac{D}{E} \text{ (unit : } \frac{F}{m} \text{)}$$

CHARGE, Q

$$Q = C \times V_c$$

$$\text{capacitance, } C = \frac{Q}{V_c} = \frac{\epsilon_0 \epsilon_r A}{d} \text{ (unit : } F \text{)}$$



CAPACITIVE CIRCUIT

DIELECTRIC MATERIAL

The purpose of permittivity is to describe how well a material can store electrical energy when exposed to an electric field.

DIELECTRIC

- A dielectric in a capacitor is a type of insulating material placed between the two conducting plates of the capacitor, or
- insulating material that is sandwiched between the two conducting plates.
-Examples : air, mica, ceramic, paper

DIELECTRIC ROLE :

- to increase the capacitor's ability to store electrical energy
- to reduce the electric field between the plates
- preventing charge from directly passing through.

HOW A CAPACITOR ABLE TO HOLD CHARGE ??



insulating material become polarized (molecular polarization- molecules can shift slightly) when placed in an electric field. The polarization enhances the capacitor's performance by increasing its capacitance. Higher permittivity means greater capacitor.

CAPACITIVE CIRCUIT

DIELECTRIC MATERIAL


Every dielectric has a maximum electric field it can withstand - dielectric strength

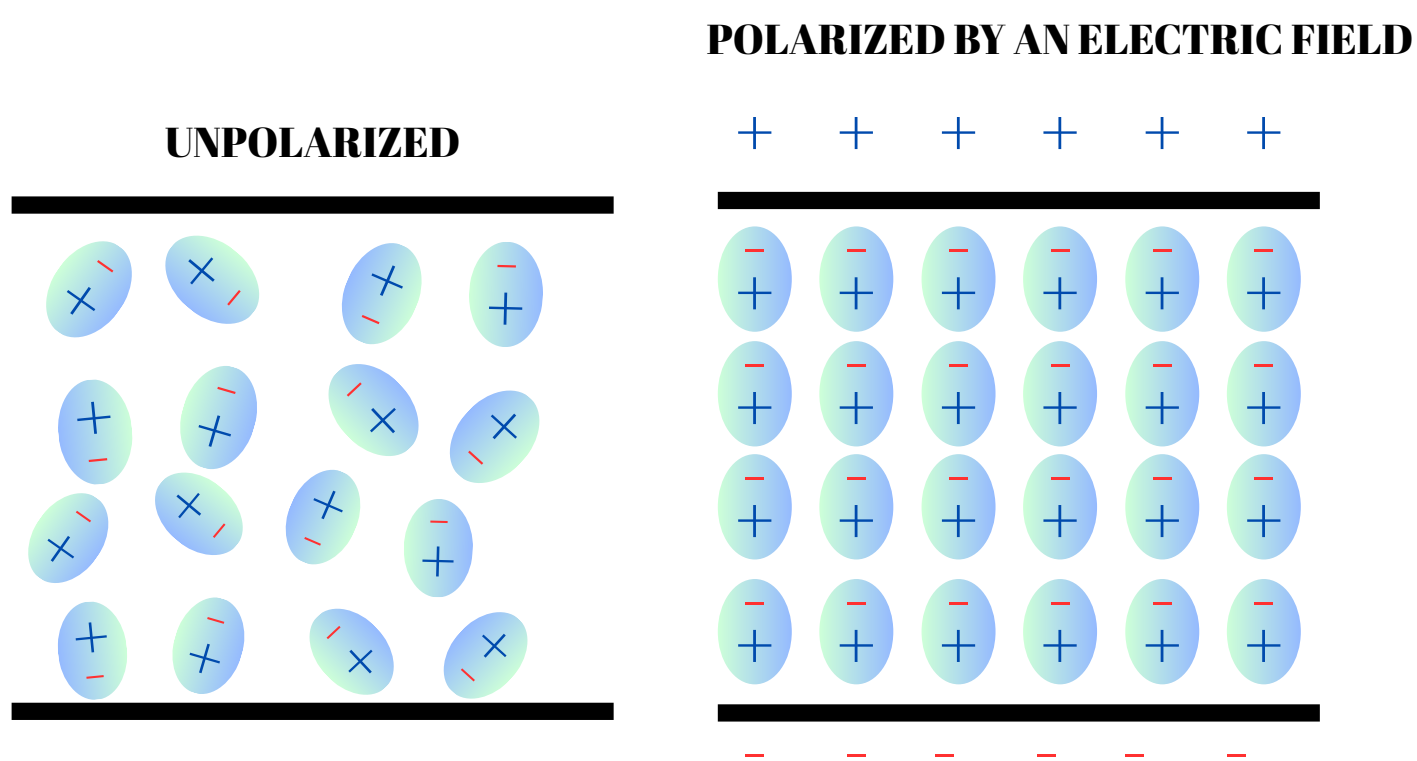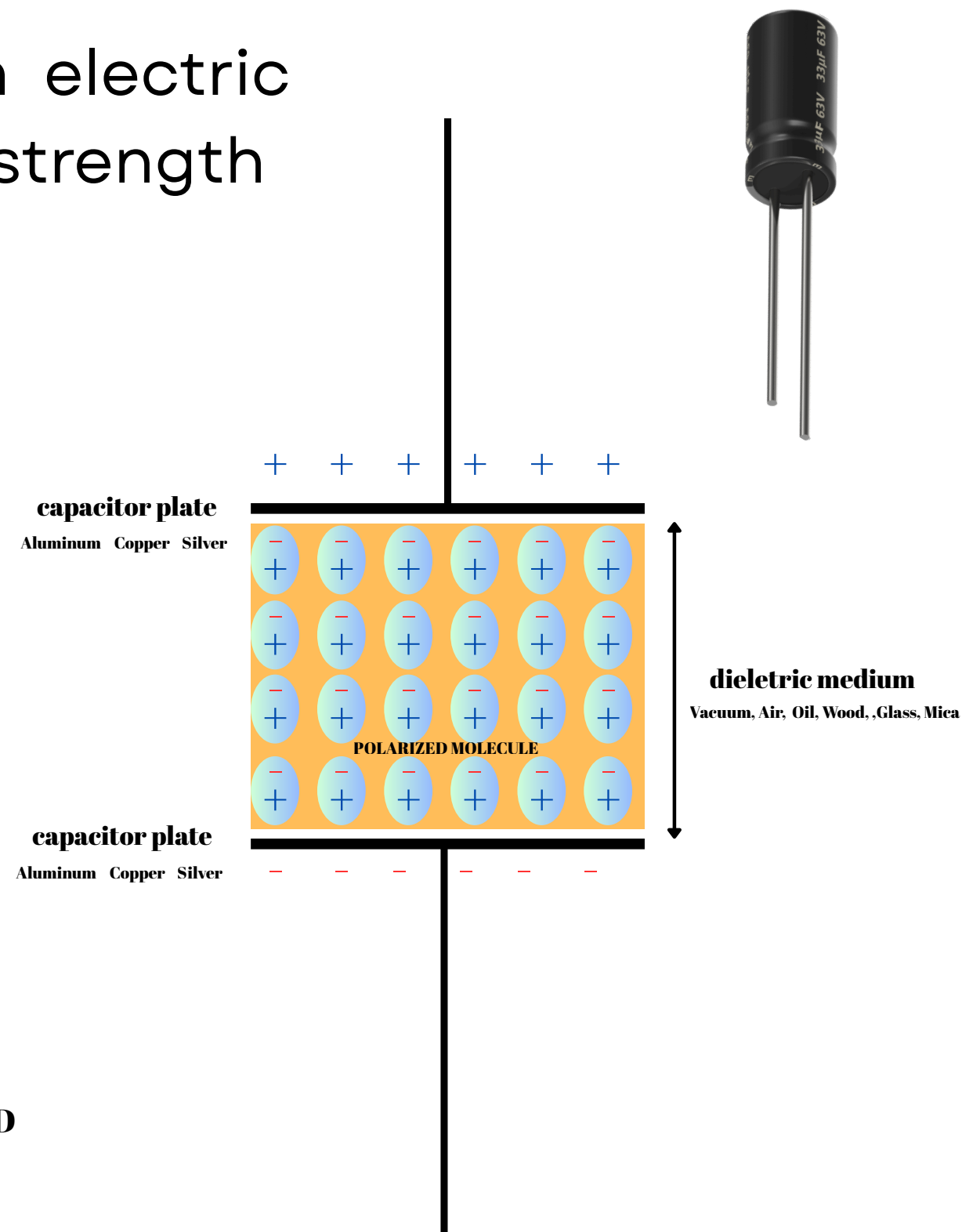- external electric field is created when voltage applied across the capacitor plates.
- free charges accumulated on the plates.
- dielectric molecule is polarized



A dielectric material in a capacitor serves to polarize its molecules when placed within an electric field between the metal plates

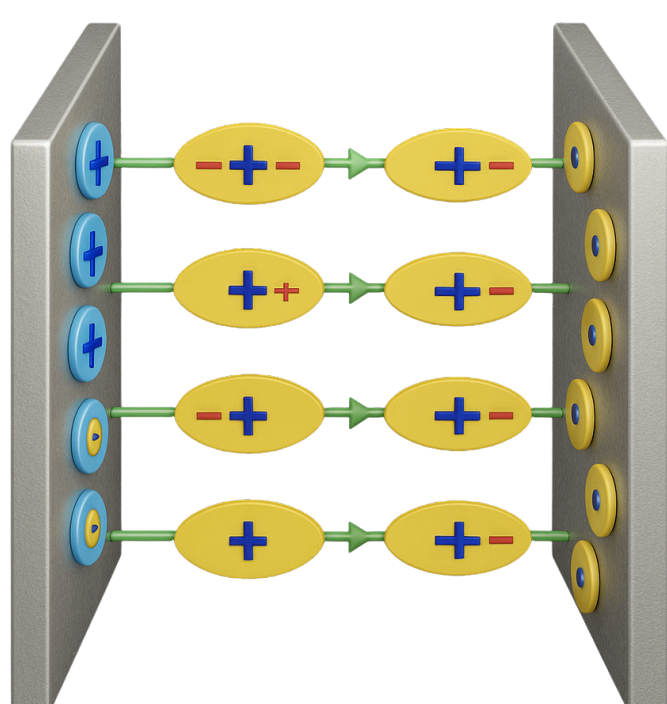
dielectric to weaken the field (external field) when its being polarized.




induced field opposes the external electric field.

CAPACITIVE CIRCUIT

DIELECTRIC

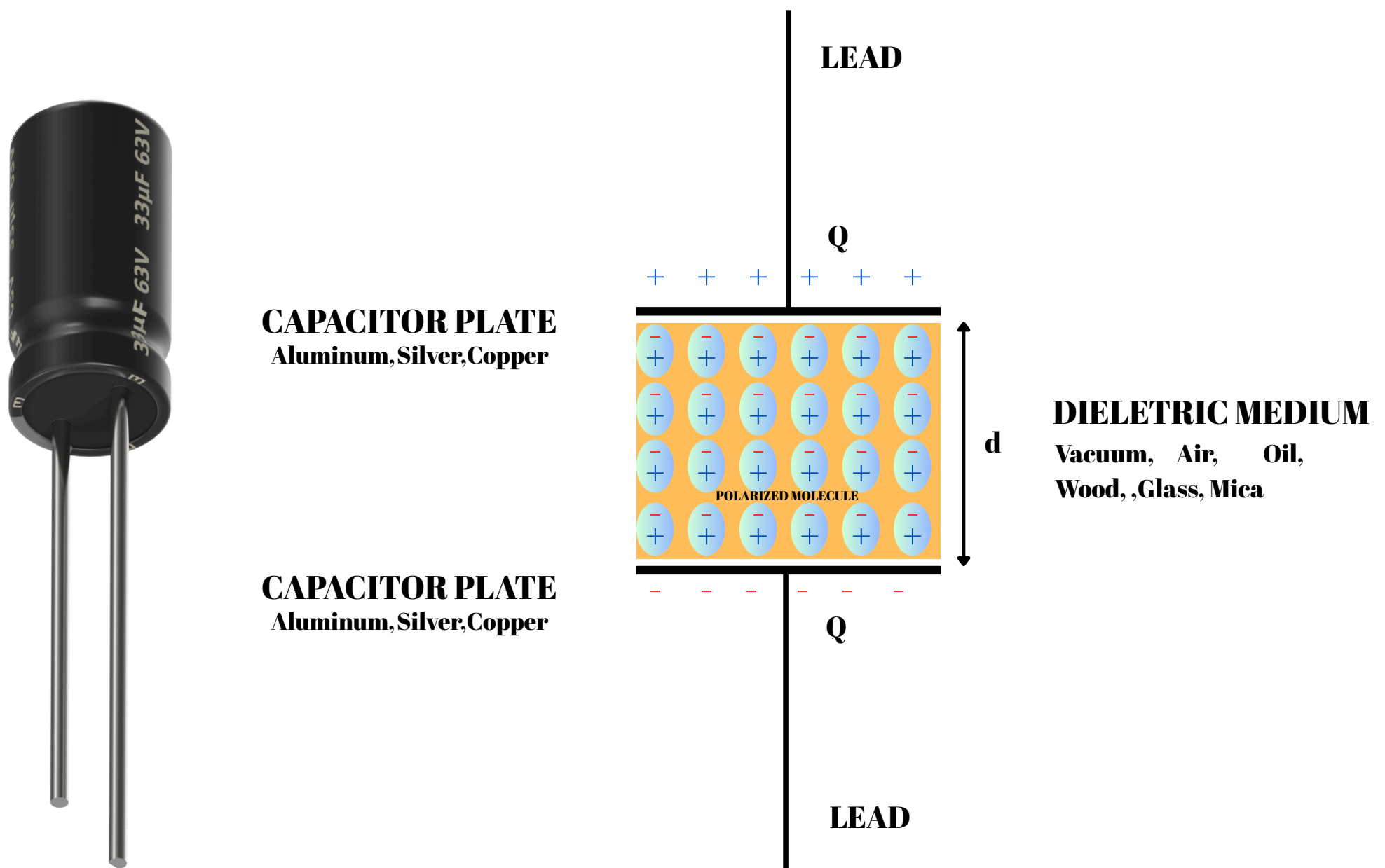

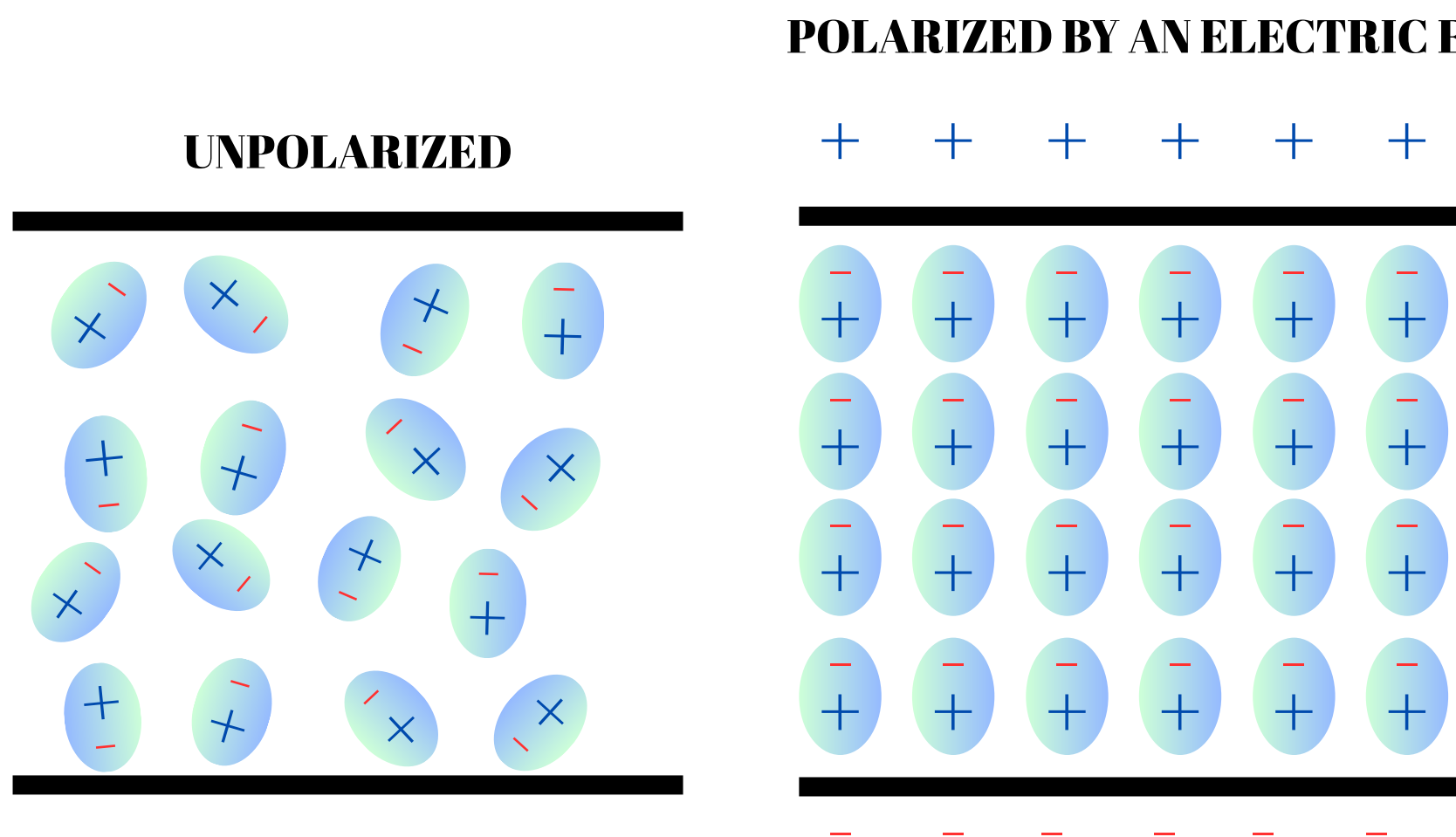Dielectric materials consist of molecules that can become polarized—their positive and negative charges slightly separate—when placed in an electric field.



- This polarization opposes the external electric field, effectively reducing the net electric field within the capacitor
- A material with higher permittivity can polarize more strongly, which means it provides greater opposition to the electric field, leading to more charge storage for the same voltage.
- higher permittivity - increases the ability of a dielectric to weaken the internal electric field, which results in increased capacitance

$$C = \frac{\epsilon_0 \epsilon_r A}{d} \text{ (unit : F)}$$

higher permittivity \Rightarrow lower internal electric field \Rightarrow higher capacitance.

CAPACITIVE CIRCUIT

PERMITTIVITY (ϵ)

- Permittivity is the ability of a material to store an electric field in the polarization (*surface flux density*) of the medium.
- The ratio of electric flux density (D) to the electric field strength (E) is called absolute permittivity (ϵ) of a dielectric and can be expressed as :

$$\epsilon = \frac{D}{E} \text{ (Unit : } \frac{\text{Farad}}{\text{metre}} \text{)}$$

$$D = \frac{Q}{A} ;$$

$$E = \frac{D}{\epsilon} = \frac{Q}{A\epsilon} ; \epsilon = \epsilon_0 \epsilon_r$$



Permittivity of the medium
(how well the medium can
support an electric field)

In a capacitor, if you insert a dielectric with high permittivity, the surface flux density increases – allowing the plates to store more charge without increasing the voltage.




“

Surface flux density, often called electric flux density (D) or displacement flux, describes how much electric field (or electric flux) passes through a given area in a material (the "medium").

”

TYPES OF PERMITTIVITY

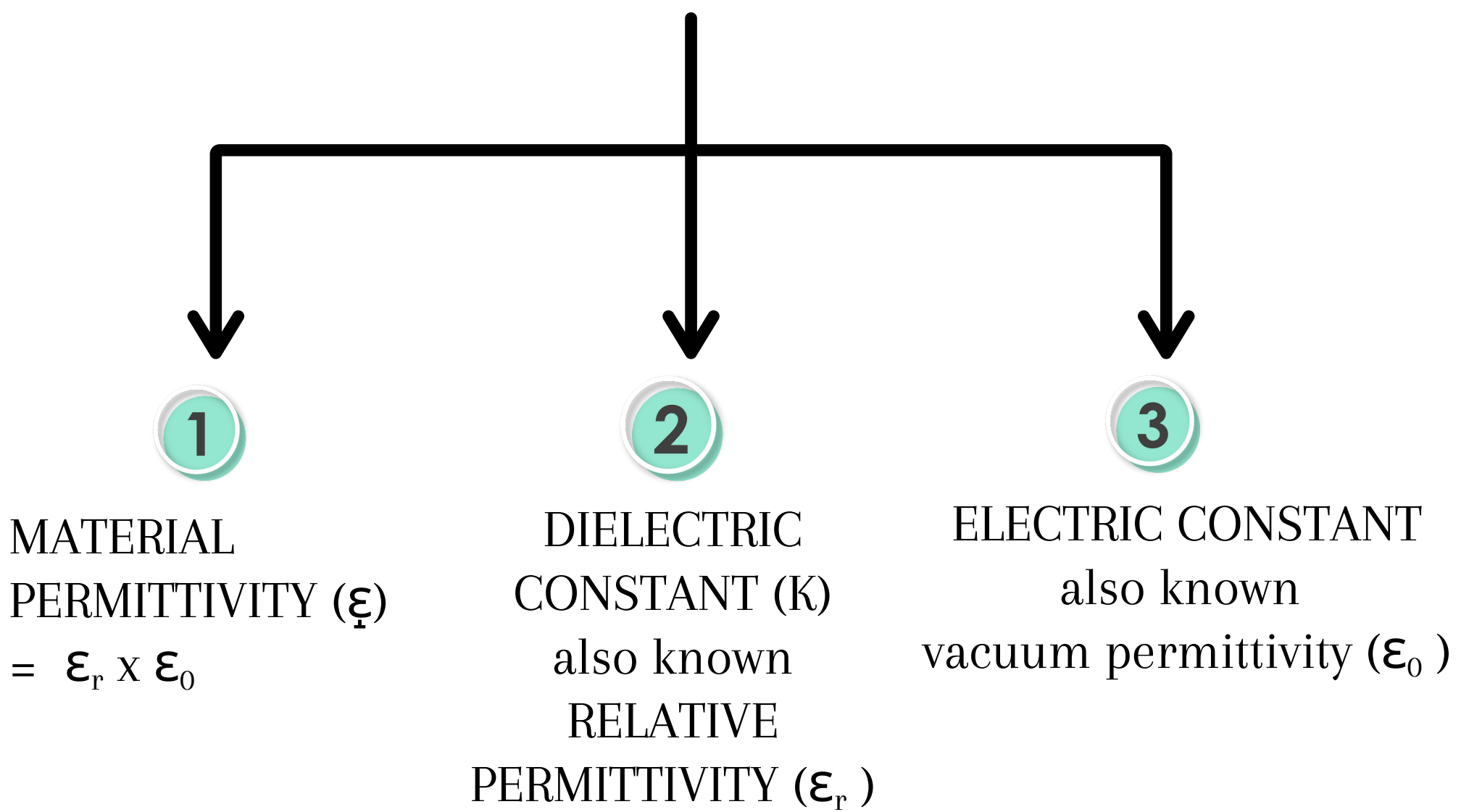

DIELECTRIC CONSTANT = RELATIVE PERMITTIVITY

$$K = \epsilon_r = \frac{\epsilon}{\epsilon_0}$$

1 MATERIAL PERMITTIVITY

2

3 VACCUMM PERMITTIVITY
 $8.854 \times 10^{-12} \text{ F/m}$

$$\epsilon = \epsilon_0 \times \epsilon_r = \frac{D}{E} \text{ (unit : } \frac{F}{m} \text{)}$$

the dielectric constant (K) is a measure of the ability of a material to store electrical energy and is defined as the ratio of the capacitance (or permittivity) of the dielectric material to the capacitance of a vacuum. Therefore, all the capacitance values are related to the permittivity of vacuum. Each different dielectric material has its own value of permittivity.

$$\frac{\epsilon_m}{\epsilon_0} = \text{dielectric constant}(K) = \text{relative permittivity}(\epsilon_r) \text{ (no unit)}$$

$$\epsilon_r = \frac{\epsilon_m}{\epsilon_0} \quad ; \quad \epsilon_m = \epsilon = \epsilon_r \times \epsilon_0 \text{ [unit } \frac{F}{m} \text{]}$$

The permittivity of a dielectric material, ϵ_m or ϵ (is measured in Farad per meter) (F/m or F.m⁻¹)

The permittivity of vacuum, ϵ_0 , sometimes called the electric constant is $8.85 \times 10^{-12} \text{ F/m}$.

Relative permittivity ϵ_r of free space/vacuum is 1



DIELECTRIC CONSTANT ALSO KNOWN AS RELATIVE PERMITTIVITY

(ϵ_r)

No.	Dielectric Material	Relative Permittivity (ϵ_r)
1	Vacuum	1
2	Air	1.0006 \approx 1.0
3	Paper	2.0 – 3.0
4	Mica	5.0 – 7.0
5	Glass	4.0 – 10.0
6	Ceramic (Class I)	6.0 – 12.0
7	Ceramic (Class II)	100 – 10,000
8	Teflon (PTFE)	2.1
9	Polyester (Mylar)	3.0 – 3.5
10	Polypropylene	2.2 – 2.3
11	Polystyrene	2.5 – 2.7
12	Barium titanate (BaTiO ₃)	1,000 – 7,000+

where $\epsilon_0 = 8.854 \times 10^{-12}$ F/m (vacuum permittivity).

$$\epsilon = \epsilon_r \times \epsilon_0$$

PERMITTIVITY (ϵ) VERSUS CAPACITANCE (C)

Thus, the capacitance of a capacitor also could be obtained from:

$$\epsilon = \frac{D}{E}; E = \frac{D}{\epsilon}$$

$$D = \frac{Q}{A}; Q=DA \quad \epsilon = \epsilon_0 \times \epsilon_r$$

$$E = \frac{V}{d}; V = Ed$$

$$C = \frac{Q}{V} = \frac{Q}{Ed} = \frac{Q}{Ed} = \frac{DA}{Ed} = \frac{DA}{\left(\frac{D}{\epsilon}\right)d} = \frac{\epsilon A}{d} = \frac{\epsilon_0 \times \epsilon_r \times A}{d}$$


$$C = \frac{\epsilon_r \epsilon_0 A}{d}$$

ϵ_r = relative permittivity

ϵ_0 = permittivity of free space / electric constant (F/m)

A = surface area of plate (m^2)

d = distance between the plate (m)

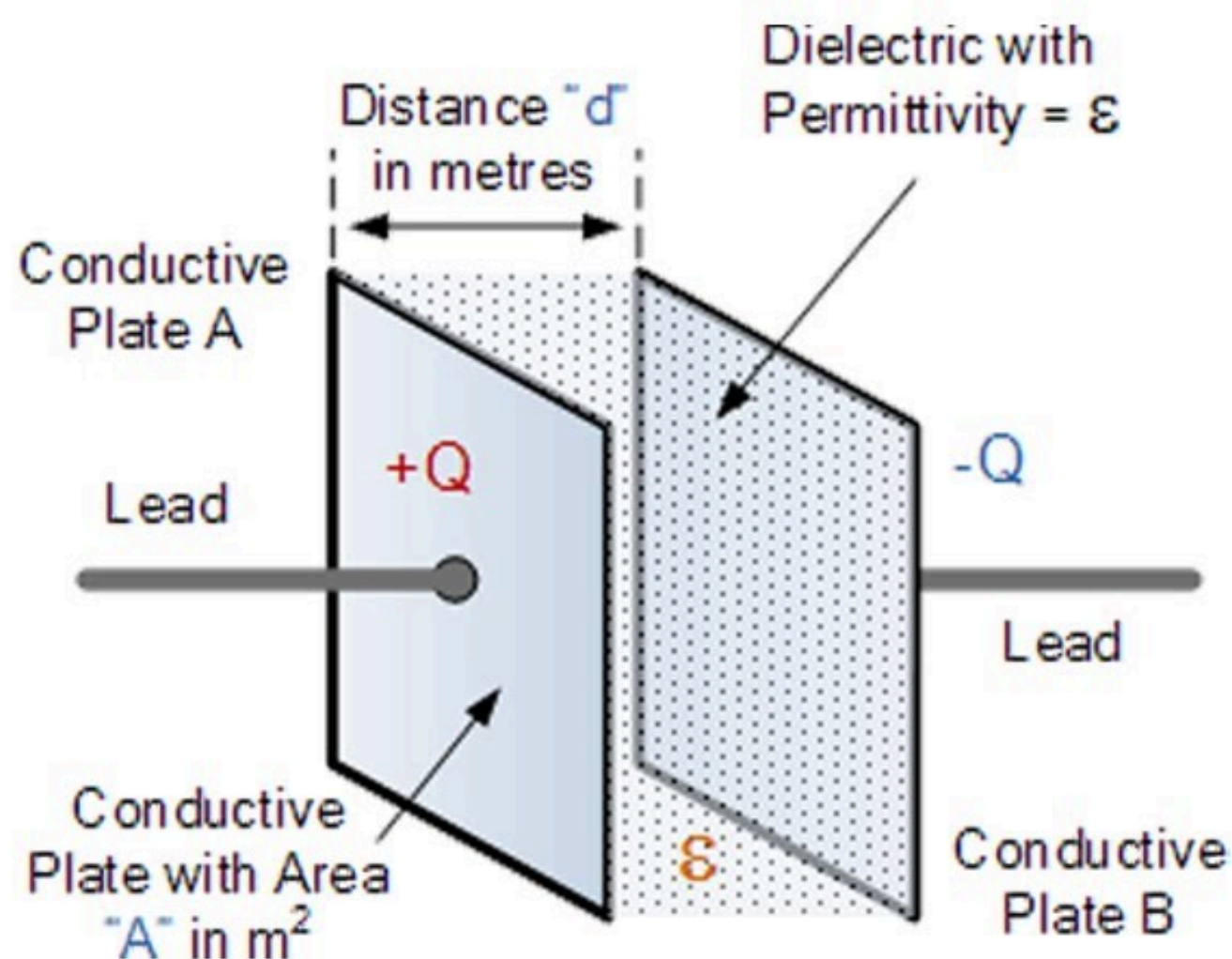

$$\text{capacitance, } C = \frac{Q}{V_c} = \frac{\epsilon_0 \epsilon_r A}{d} \quad (\text{unit : } F)$$

•CAPACITANCE

capacitance, C of a capacitor is the ratio of the charge Q per plate to the applied voltage.

$$C = \frac{Q}{V_C}$$

C = Capacitance

V_C = Potential Different of capacitance

Q = charge (coulombs)

$$C = \frac{Q}{V_C} = \frac{\epsilon A}{d}$$

C = Capacitance

d = spacing between the plates (m)


A = surface area (m^2)

ϵ = permittivity (*farad/meter*)

3 factors determine the value of the capacitance:

1. The surface area of the plates—the larger the area, the greater the capacitance.
2. The spacing between the plates—the smaller the spacing, the greater the capacitance.
3. The permittivity of the material—the higher the permittivity, the greater the capacitance.

CAPACITIVE CIRCUIT - EQUATION

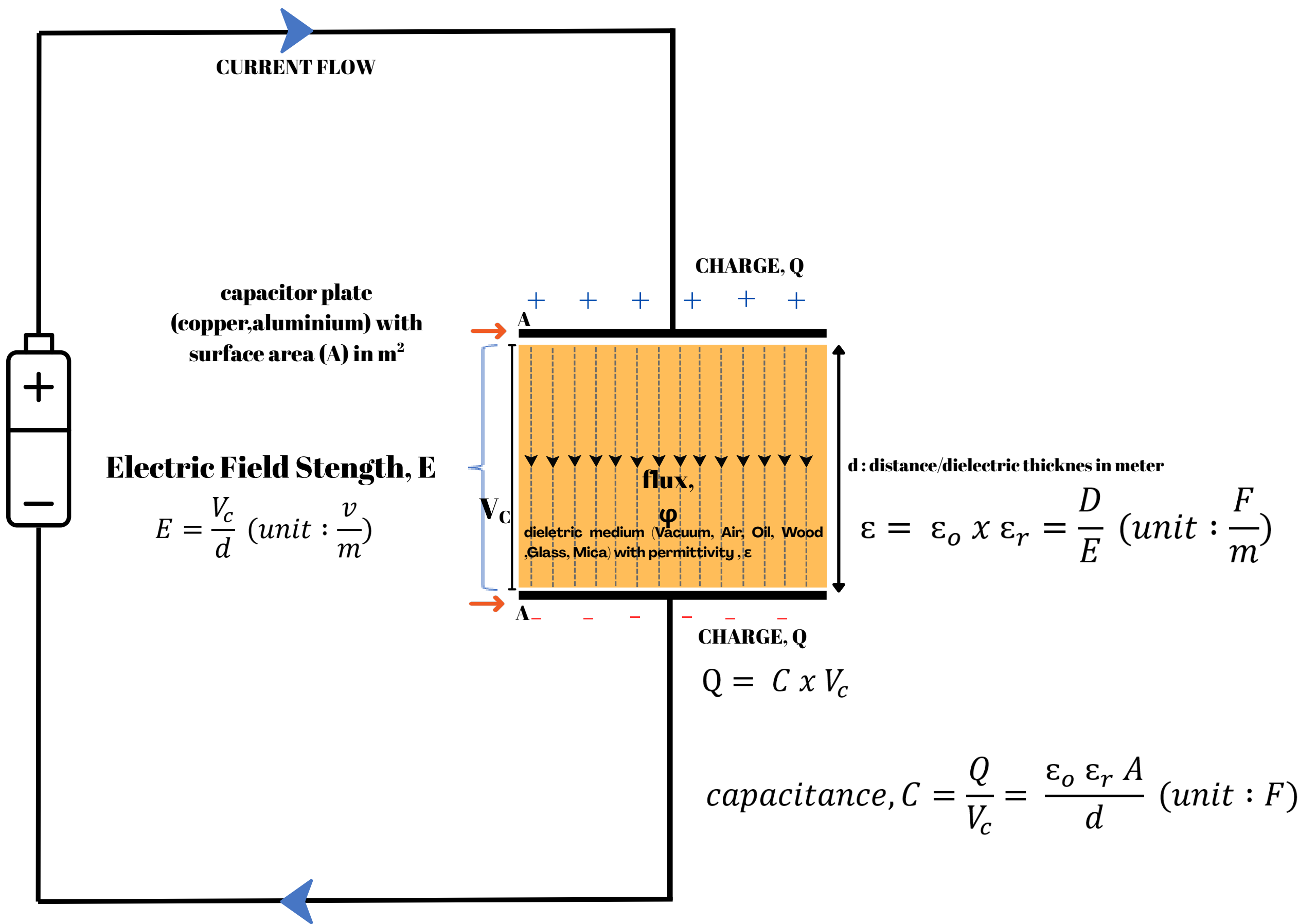

permittivity

$$\epsilon = \frac{D}{E} \text{ (Unit : } \frac{\text{Farad}}{\text{metre}} \text{)}$$

permittivity

$$\epsilon = \epsilon_r \times \epsilon_0 \text{ (Unit : } \frac{\text{Farad}}{\text{metre}} \text{)}$$

$\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$

permittivity

$$\epsilon_r \times \epsilon_0 = \frac{D}{E} \text{ (Unit : } \frac{\text{Farad}}{\text{metre}} \text{)}$$

ELECTRIC FIELD STRENGTH (E)

$$E = \frac{V \text{ (unit:Volt)}}{d \text{ (unit:metre)}}$$

Flux density

$$D = \frac{Q \text{ (unit:Coulomb)}}{A \text{ (unit:metre}^2\text{)}}$$

capacitance

$$C = \frac{\epsilon_r \epsilon_0 A}{d}$$

$$I = \frac{Q(\text{charge})}{t(\text{time})}, \text{ thus } Q = It$$

Q = charge (coulomb)

t = time (second)

$$C = \frac{Q \text{ (Charge)}}{V \text{ (Potential Diff.)}}$$



EXERCISE

1. The flux density between two plates separated by mica of relative permittivity 5 is $2 \mu\text{C}/\text{m}^2$. Find the voltage gradient between the plates.

Ans : $45.2 \text{ Kv}/\text{m}$

2. Two parallel plates having a potential difference of 200V between them are spaced 0.8mm apart. What is the electric field strength? Find also the electric flux density when the dielectric between the plates is (a) air, and (b) polythene of relative permittivity 2.3

Ans:
 $250 \text{ Kv}/\text{m}$
 $2.213 \mu\text{Cm}^{-2}$
 $5.089 \mu\text{Cm}^{-2}$




QUICK TIPS

$$E = \frac{v}{d} \text{ (Unit : } \frac{\text{volt}}{\text{meter}} \text{)}$$

$$\epsilon = \frac{D}{E} \text{ (Unit : } \frac{\text{Farad}}{\text{metre}} \text{)}$$

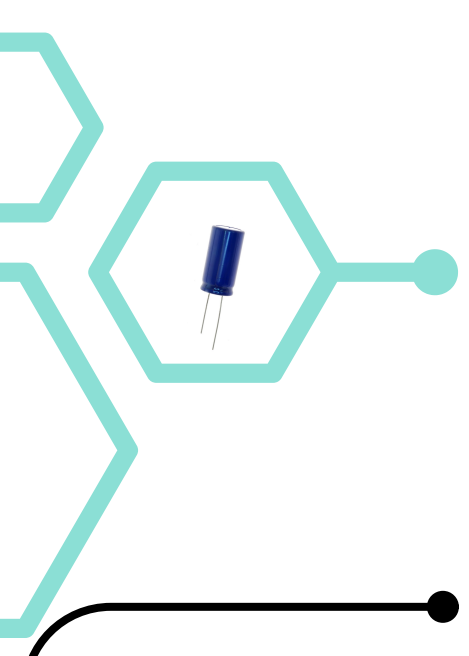
voltage gradient means the electric field strength between the plates



EXERCISE

FINAL SESI 2 : 2022/2023

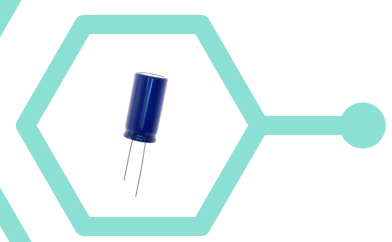1. With the aid of a diagram, describe the construction of a capacitor.
2. With aid of circuit diagram, express the formula for the total capacitance in series and parallel connections.
3. A capacitor is charged to 150V and then discharged through a $60\text{k}\Omega$ resistor. If the time constant of the circuit is 0.8s, calculate the value of the capacitor, the time for the capacitor voltage to fall to 20V, the current flowing when the capacitor has been discharging for 0.5s and the voltage drop across the resistor when the capacitor has been discharging for one second.



EXERCISE

• **SESI 2 : 2023/2024**

a) List TWO (2) types of polarity capacitor and TWO (2) types of non-polarity capacitor.

b) With the aid of related formula, explain the factors affecting capacitance.

c) Based on Figure A2(c), when switch is closed, calculate the time constant, current and potential difference through the capacitor after 6 seconds and energy stored in capacitor.


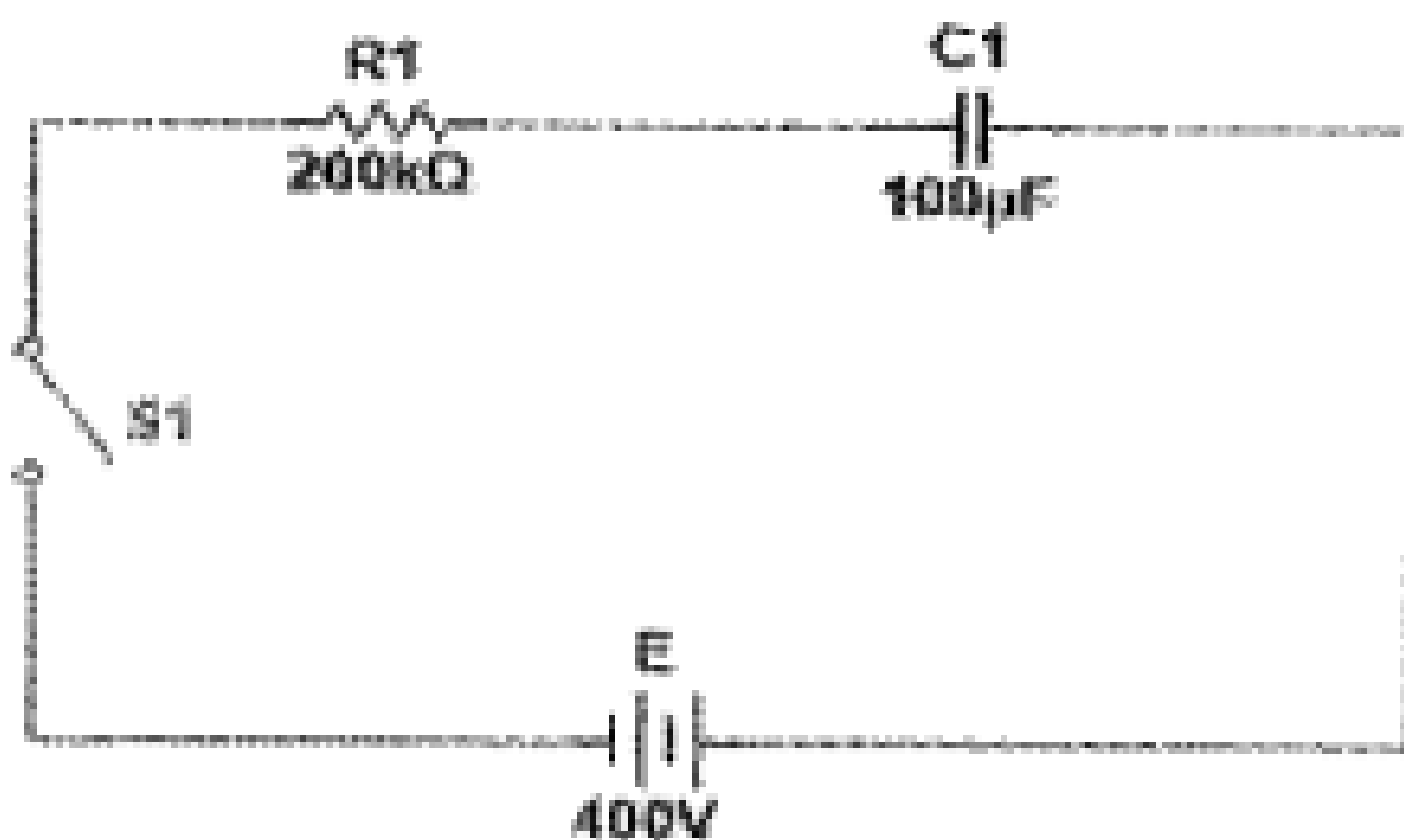



Figure A2(c)/ *Rajah A2(c)*

CIRCUIT'S CONNECTION


SERIES

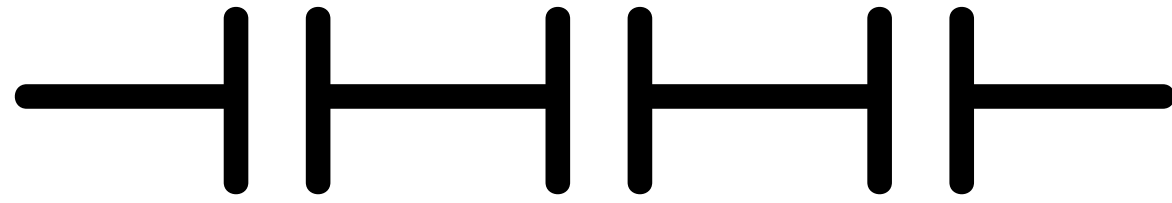

PARALLEL

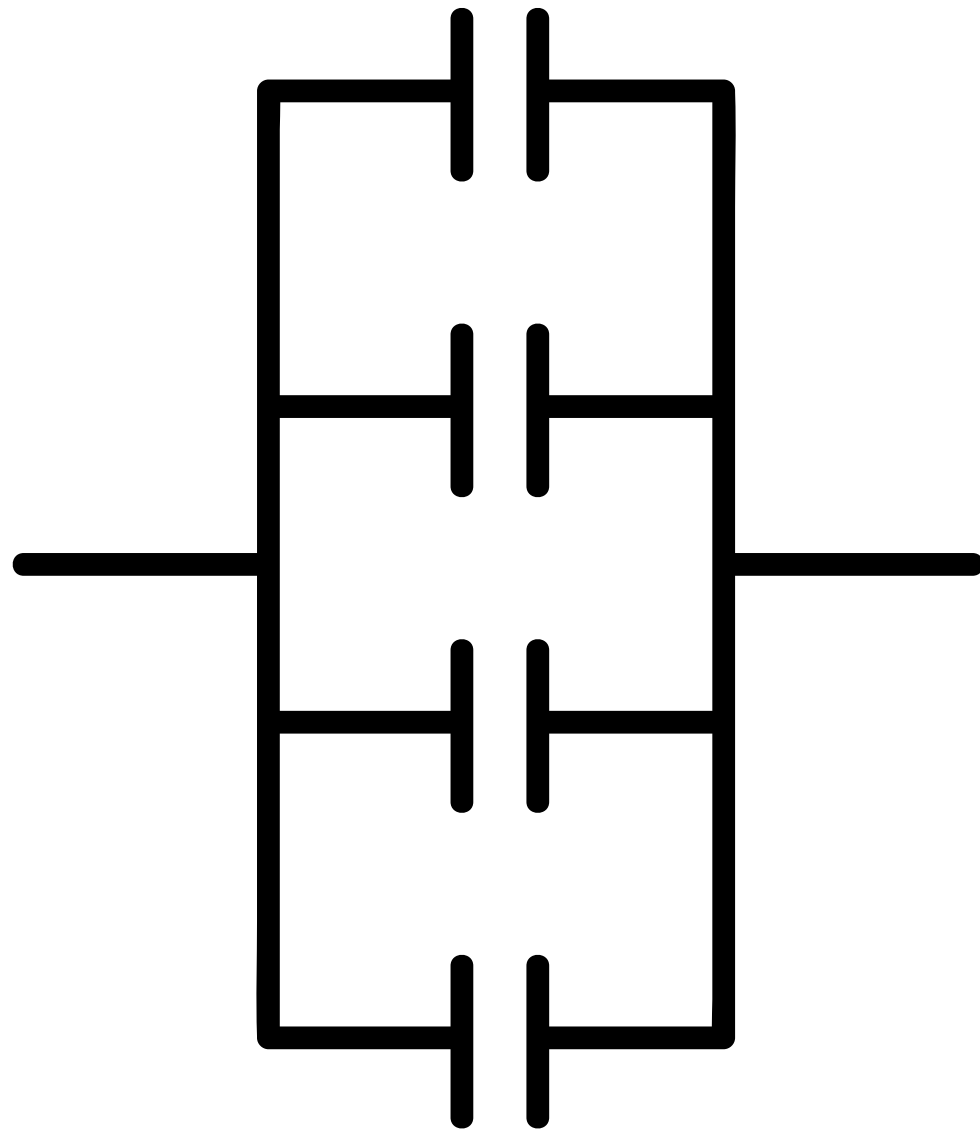


SERIES - PARALLEL

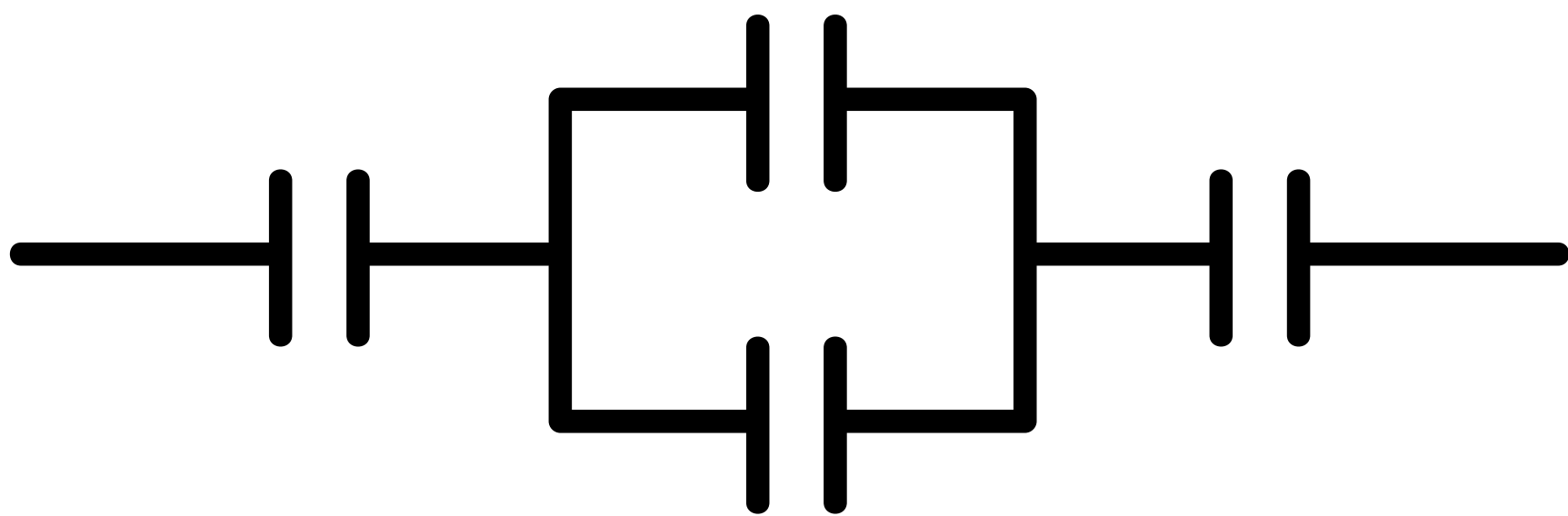

CAPACITANCE EQUIVALENT FOR SERIES AND PARALLEL CONNECTIONS

CIRCUITS

SERIES

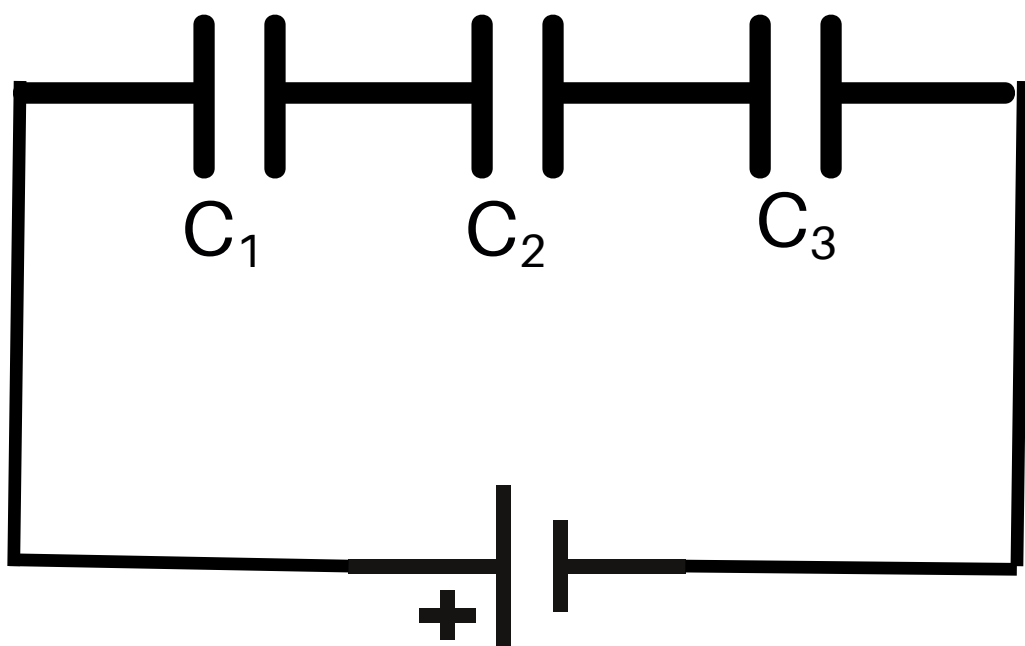


TOTAL CAPACITANCE

$$C_T = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)^{-1}$$

UNIT: FARAD

Equivalent resistance in parallel (2 resistors case)

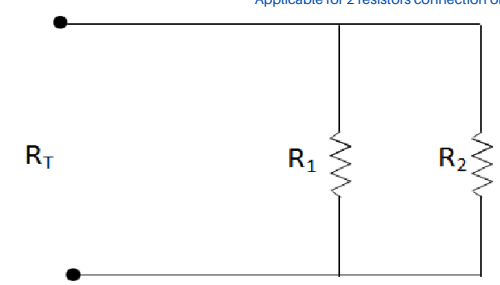Applicable for 2 resistors connection only.




$$R_T = \frac{R_1 \times R_2}{R_1 + R_2}$$

For two capacitors only:

$$C_T = \frac{C_1 \times C_2}{C_1 + C_2} \text{ (unit : F)}$$

PARALLEL

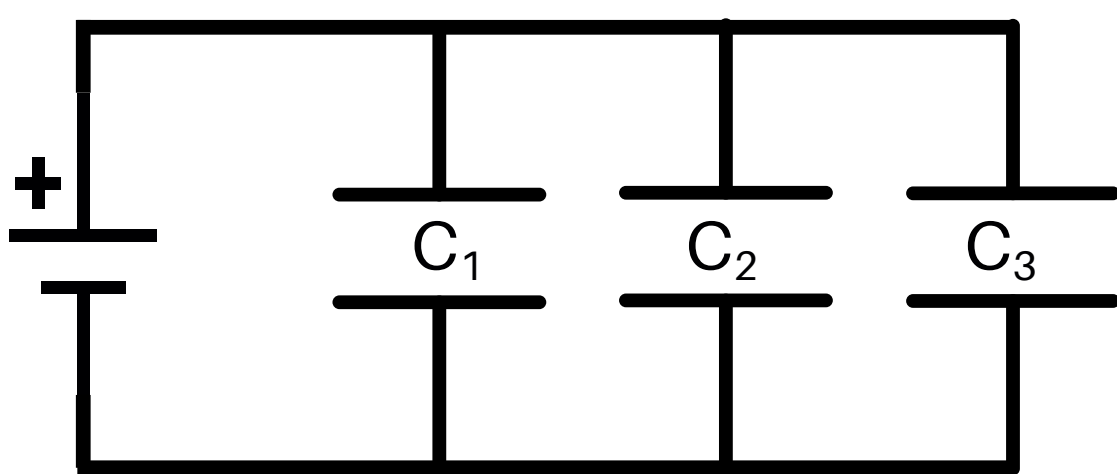

$$C_T = C_1 + C_2 + C_3$$

UNIT : FARAD

CAPACITANCE EQUIVALENT CIRCUITS FOR SERIES AND PARALLEL CONNECTIONS

EXERCISE FINAL SESI 1 2023/2024

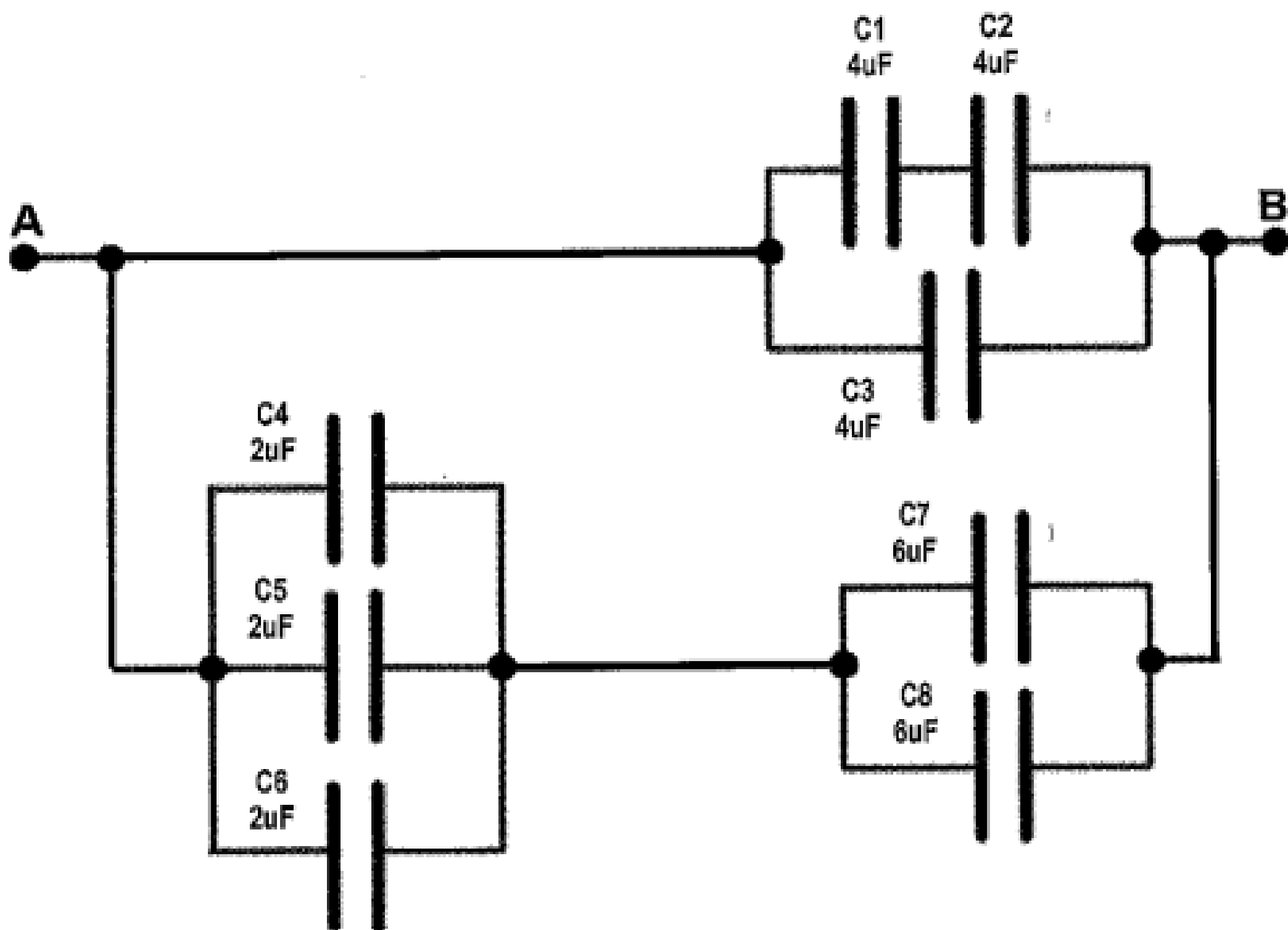


Figure A2(b) / *Rajah A2(b)*

By referring to Figure A2(b), simplify the circuit to obtain the equivalent capacitance value, C_r at terminal A-B.

CAPACITANCE EQUIVALENT CIRCUITS FOR SERIES AND PARALLEL CONNECTIONS

EXERCISE FINAL SESI 1 2023/2024

Define a capacitor and label the construction of a capacitor shown in Figure 2(a).
Takrifkan pemuat dan labelkan pembinaan pemuat seperti yang ditunjukkan dalam Rajah 2(a).

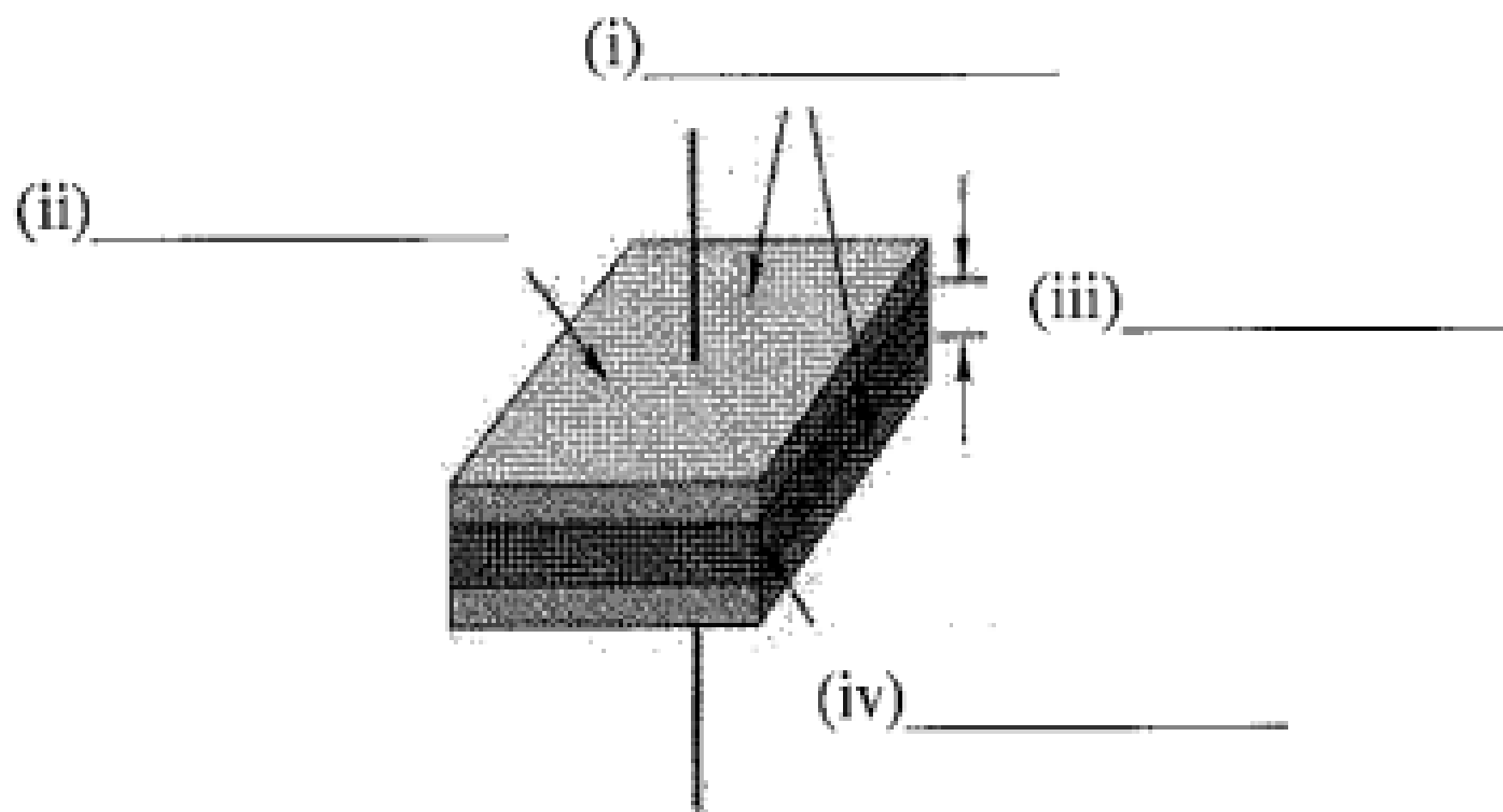


Figure 2(a) / *Rajah 2(a)*

Figure A2(c) shows a schematic diagram that consists of resistive and capacitive loads. If the switch, SW is switched to node a at $t = 0$ s, calculate the time constant, the instantaneous value of current when $t = 2$ ms and the maximum energy stored by the capacitor.

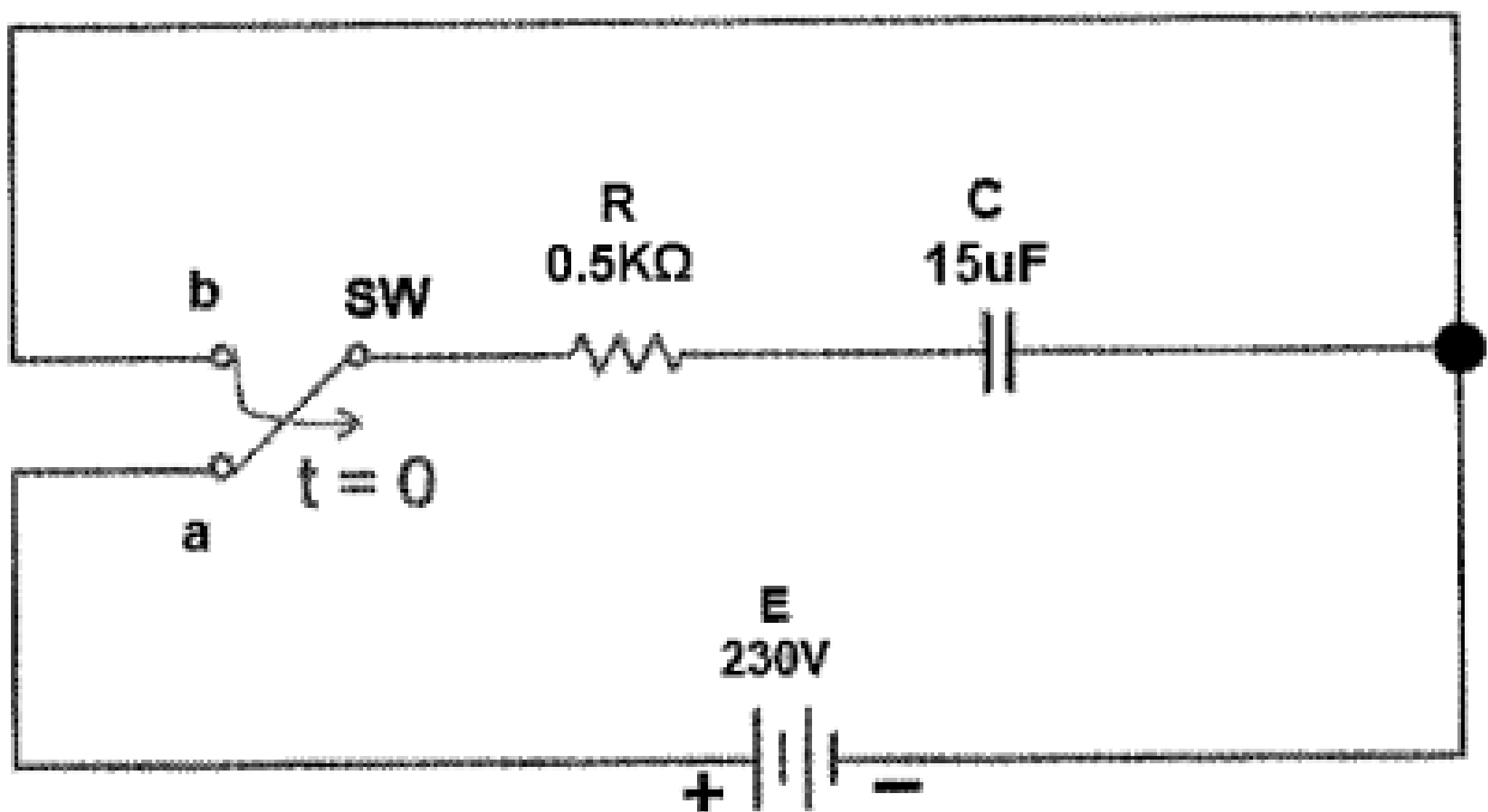


Figure A2(c) / *Rajah A2(c)*

CIRCUIT'S CONNECTION

- b) Calculate the total capacitance C_{XY} of the network in Figure 2(b).
Kira jumlah kemuatan C_{XY} bagi rangkaian dalam Rajah 2(b).

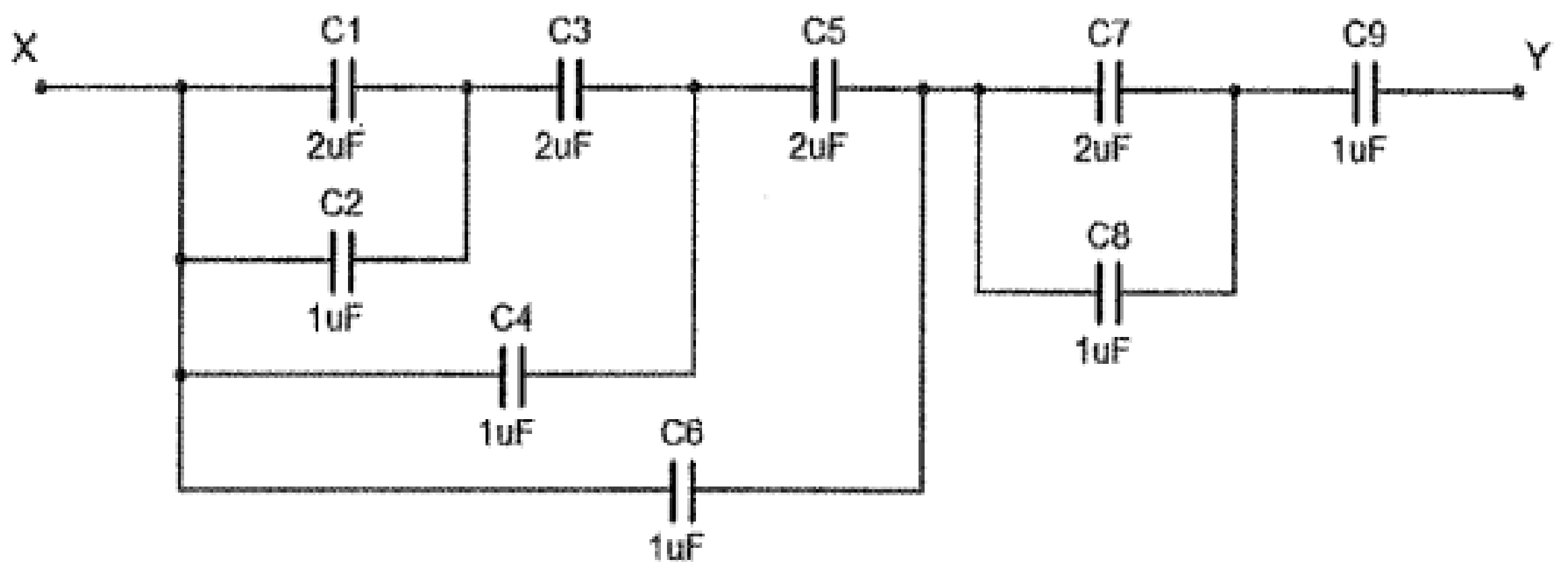


Figure 2(b) / Rajah 2(b)

Based on Figure A2 (b), simplify the circuit with capacitors as below.
Merujuk kepada Rajah A2 (b), permudahkan litar dengan pemuat seperti di bawah.


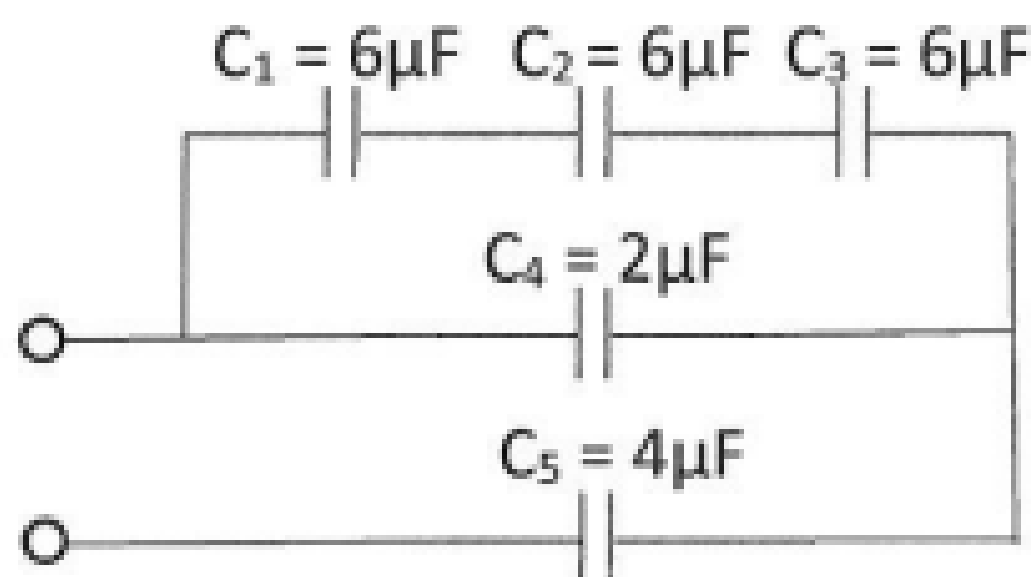



Figure A2 (b) / Rajah A2 (b)

CAPACITIVE LOAD


CHARGING

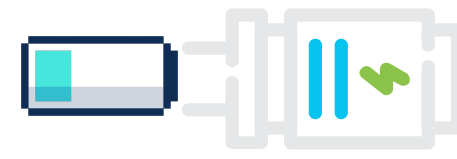

WHAT HAPPEN WHEN SWITCH (S) IS PRESSED?

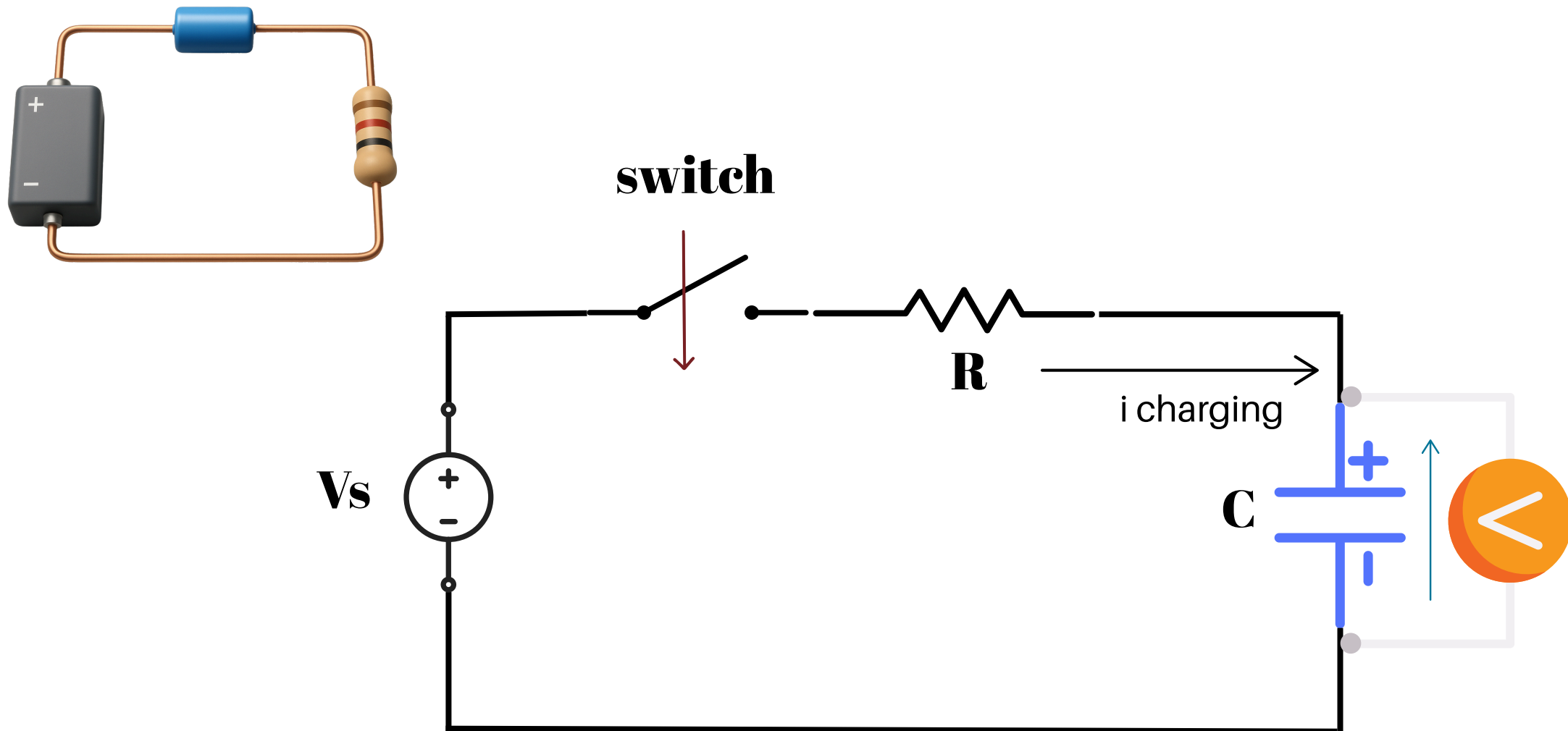

The capacitor is in charging mode when the switch is turned on. When the switch is turned on, the capacitor starts to charge. The circuit is connected to a battery (V_s), so current flows through it. At first ($t=0$, initial time), the capacitor acts like a wire, so the voltage across it is almost zero ($V_c = 0$). As it charges, the voltage across the capacitor increases until it reaches the same as the battery, and the current stops flowing

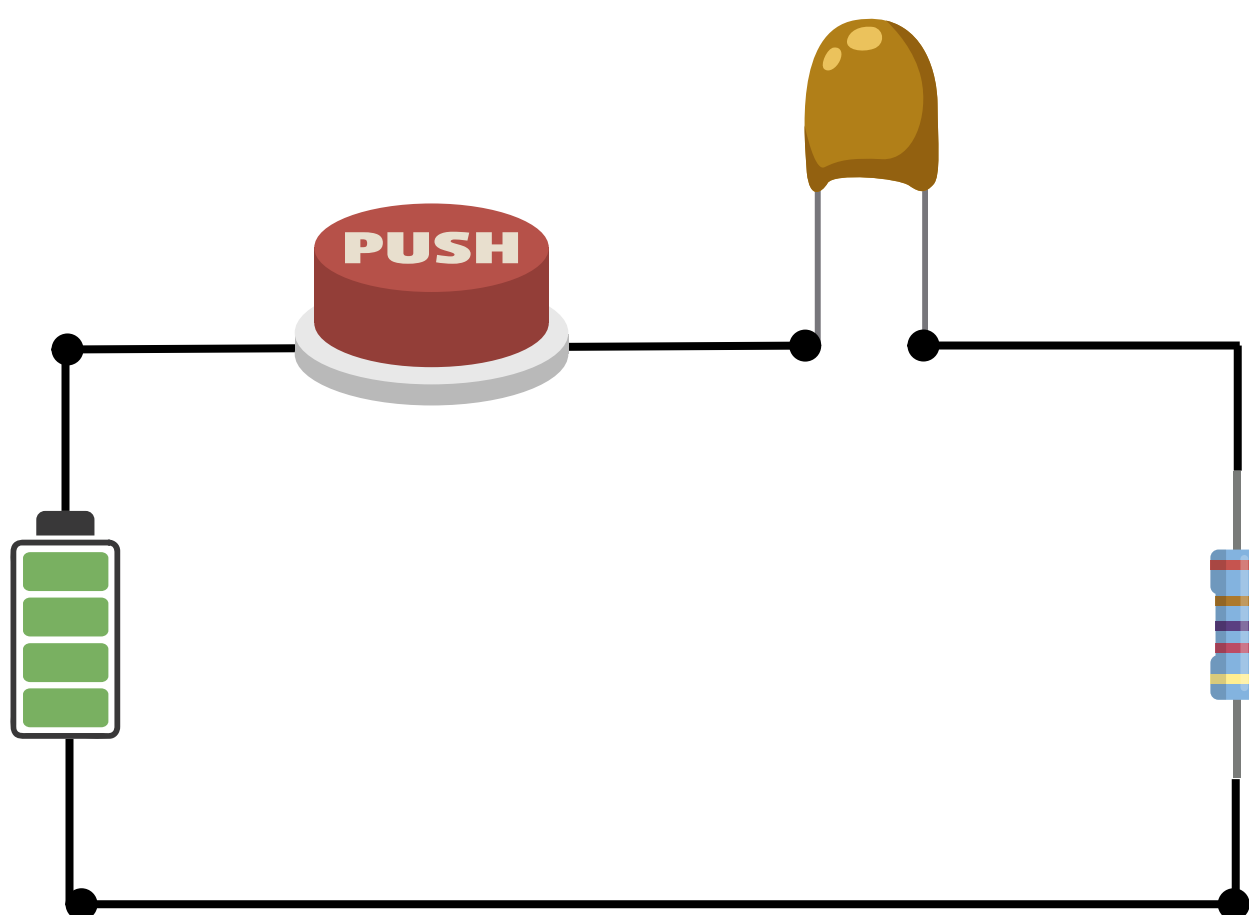



CHARGING

KVL

$$-V_S + V_R + V_C = 0$$

$$V_S = V_R + V_C$$

When a battery connected to circuit, at first (short time), capacitor like a short circuit, $V_C = 0$.

$$V_S = V_R + 0$$

$$V_S = V_R$$

$$\text{Initial current, } i_0 = \frac{V_S}{R}$$

$$i_0 = i_{\max}$$

$$i = i_{\max} e^{-\frac{t}{RC}}$$

Capacitor charging,



$$V_C = V_S (1 - e^{-\frac{t}{\tau}})$$

$$\text{Time constant, } \tau = RC$$

At long time, capacitor like an open circuit, $V_C = V_S, i=0 ; t=\infty$

CHARGING

CHARGING CAPACITOR VOLTAGE

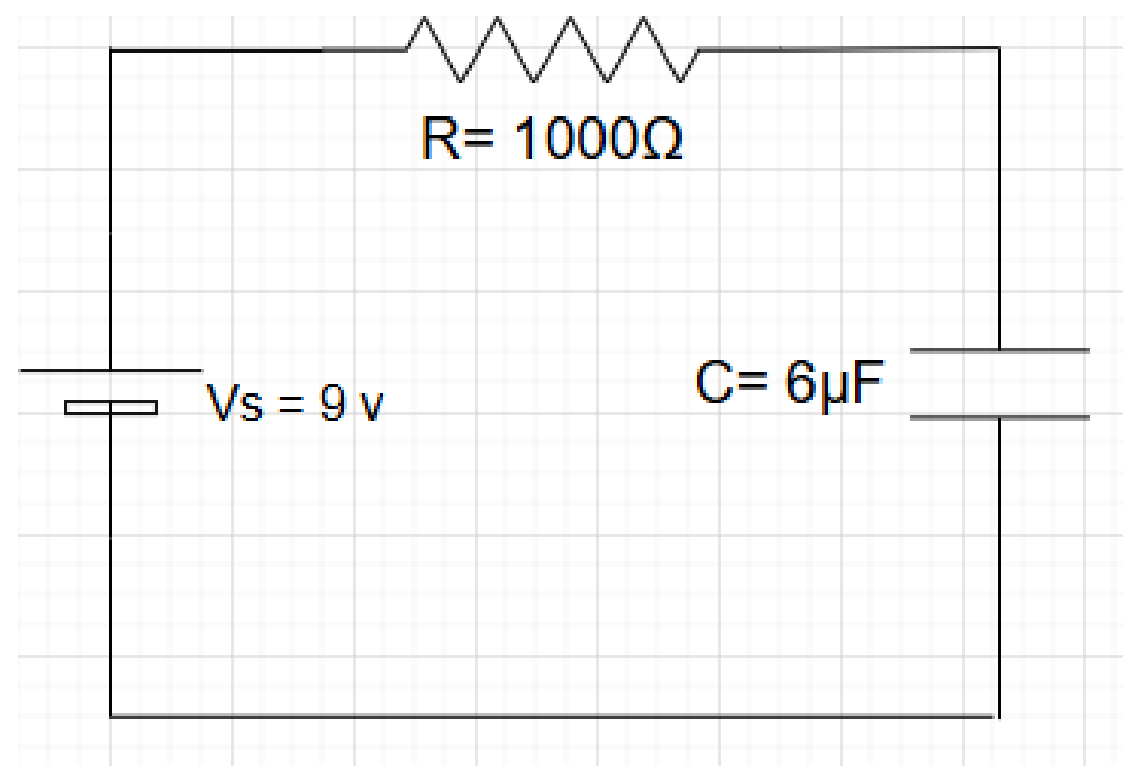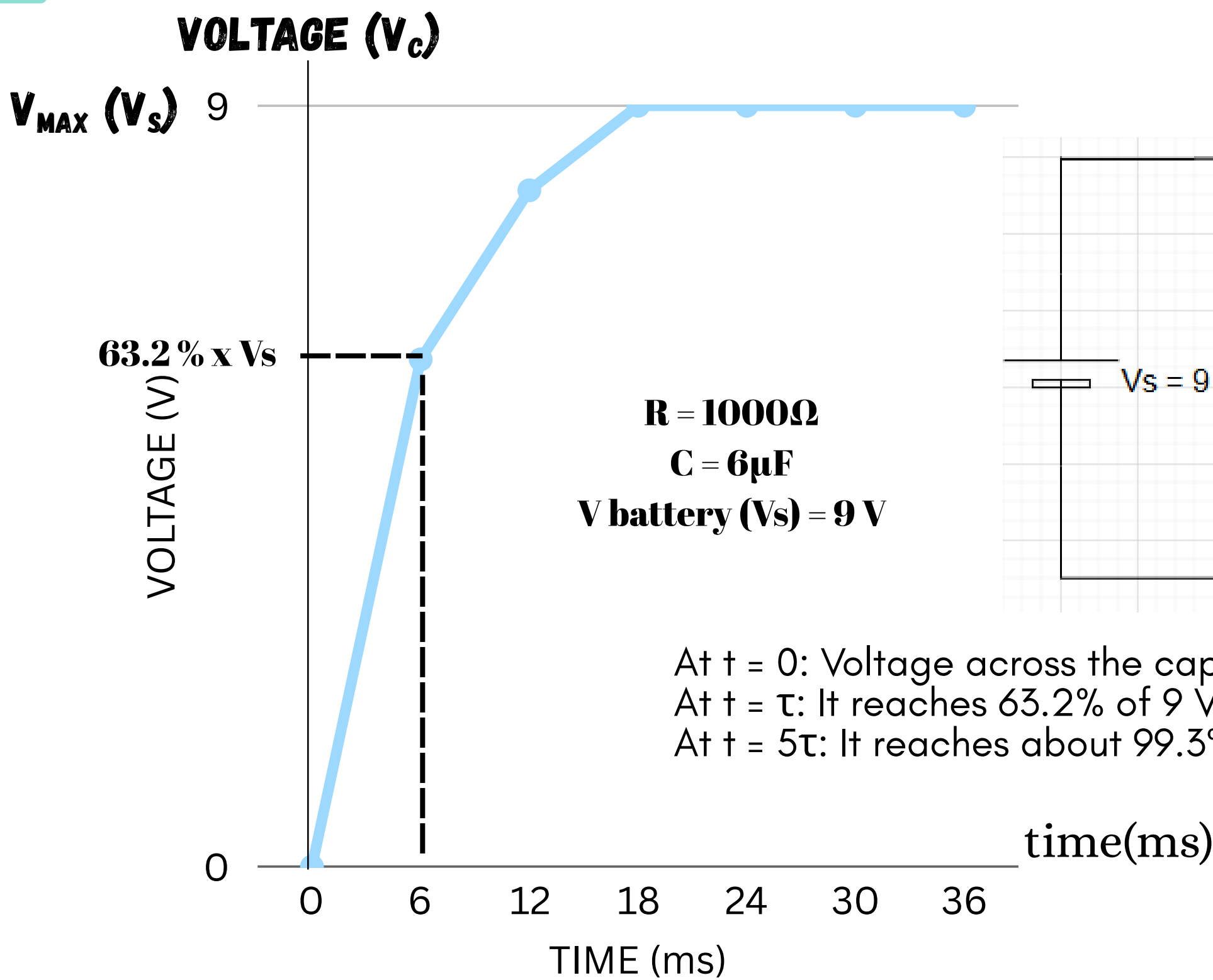

Capacitor charging,

$$V_C = V_S (1 - e^{-\frac{t}{\tau}})$$

Charging

V_c versus Time


t	$e^{-\frac{t}{RC}}$	$\frac{V_C}{V_S} = (1 - e^{-\frac{t}{RC}})$	$V_C = V_S (1 - e^{-\frac{t}{RC}})$
0	1	0	0
$\tau_1 = 6ms$	$e^{-\frac{t}{RC}} = e^{-\frac{6ms}{6ms}} = e^{-1} = 0.368$	$1 - 0.368 = 0.632$	5.688
$\tau_2 = 12ms$	$e^{-2} = 0.135$	0.865	7.785
$\tau_3 = 18ms$	$e^{-3} = 0.0498$	0.95	8.55
$\tau_4 = 24ms$	$e^{-4} = 0.0183$	0.982	8.835
$\tau_5 = 30ms$	$e^{-5} = 0.0067$	0.9933	8.94
....100% / $t = \infty$	0	1 ($V_C = V_S$)	9.00

$$V_S = 9v \quad \text{Time constant, } \tau = RC \quad RC = 1000 \times 6\mu F = 6ms$$

Voltage	Component
V_s	Battery
V_C	Capacitor
V_R	Resistor


CHARGING

CHARGING CAPACITOR CURRENT

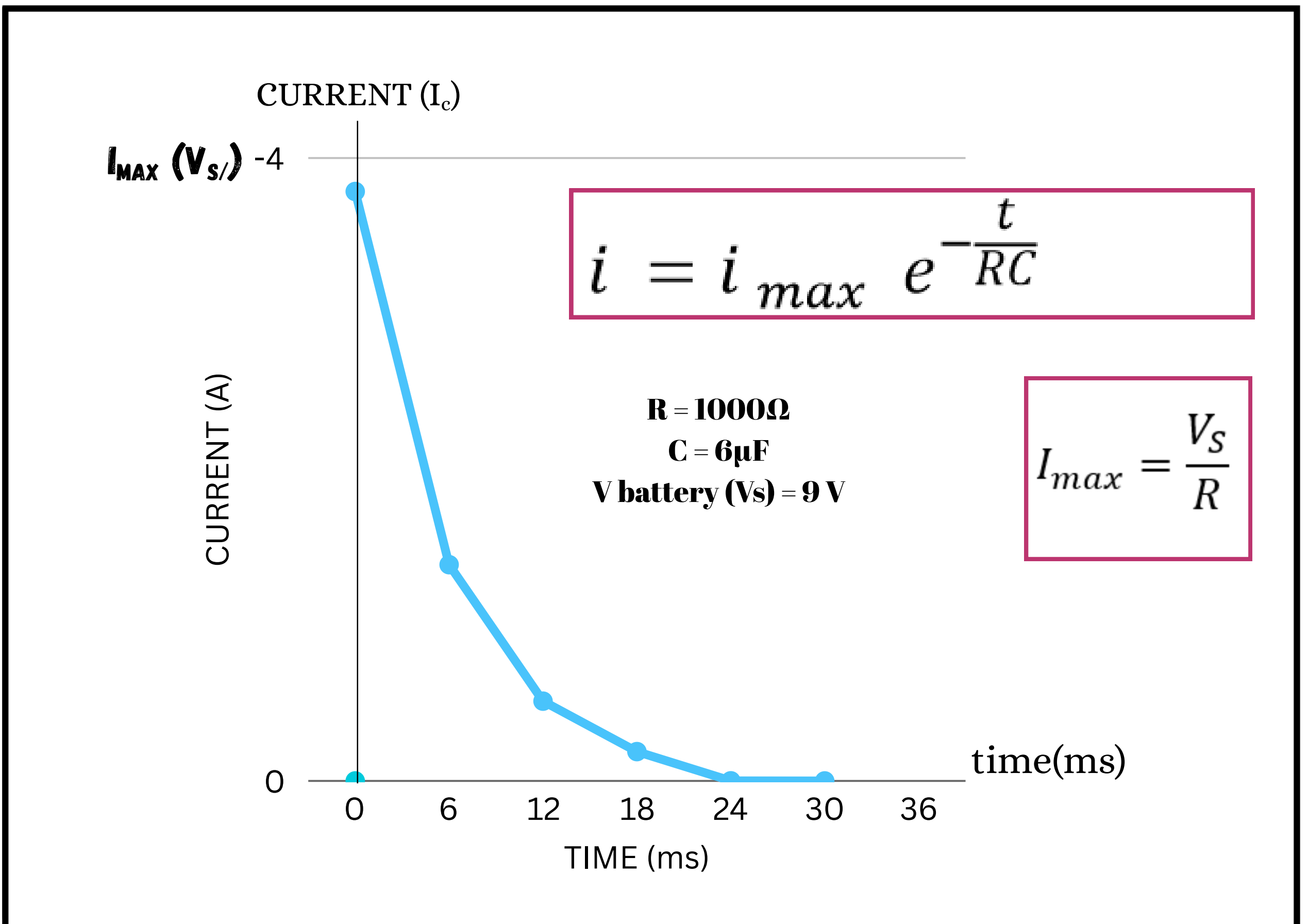


		$\tau = RC = 1000 \times 6\mu = 6ms$						
		0	τ	2τ	3τ	4τ	5τ	T= INFINITI
		0	6ms	12ms	18ms	24ms	30ms	
		e-0	e-1	e-2	e-3	e-4	e-5	
$e^{-\frac{t}{RC}}$		1	0.368	0.135	0.0498	0.0183	0.0067	0
$1 - e^{-\frac{t}{RC}}$		0	0.632	0.865	0.95	0.982	0.9933	1
$I_{max} = \frac{V_S}{R}$	A	0.009	0.009	0.009	0.009	0.009	0.009	
$I_c = \frac{V_S}{R} \times e^{-\frac{t}{RC}}$	mA	9	3.312	1.215	0.4482	0.1647	0.0603	
$V_c = V_S \times (1 - e^{-\frac{t}{RC}})$	V	0	5.688	7.785	8.55	8.835	8.94	9

CHARGING

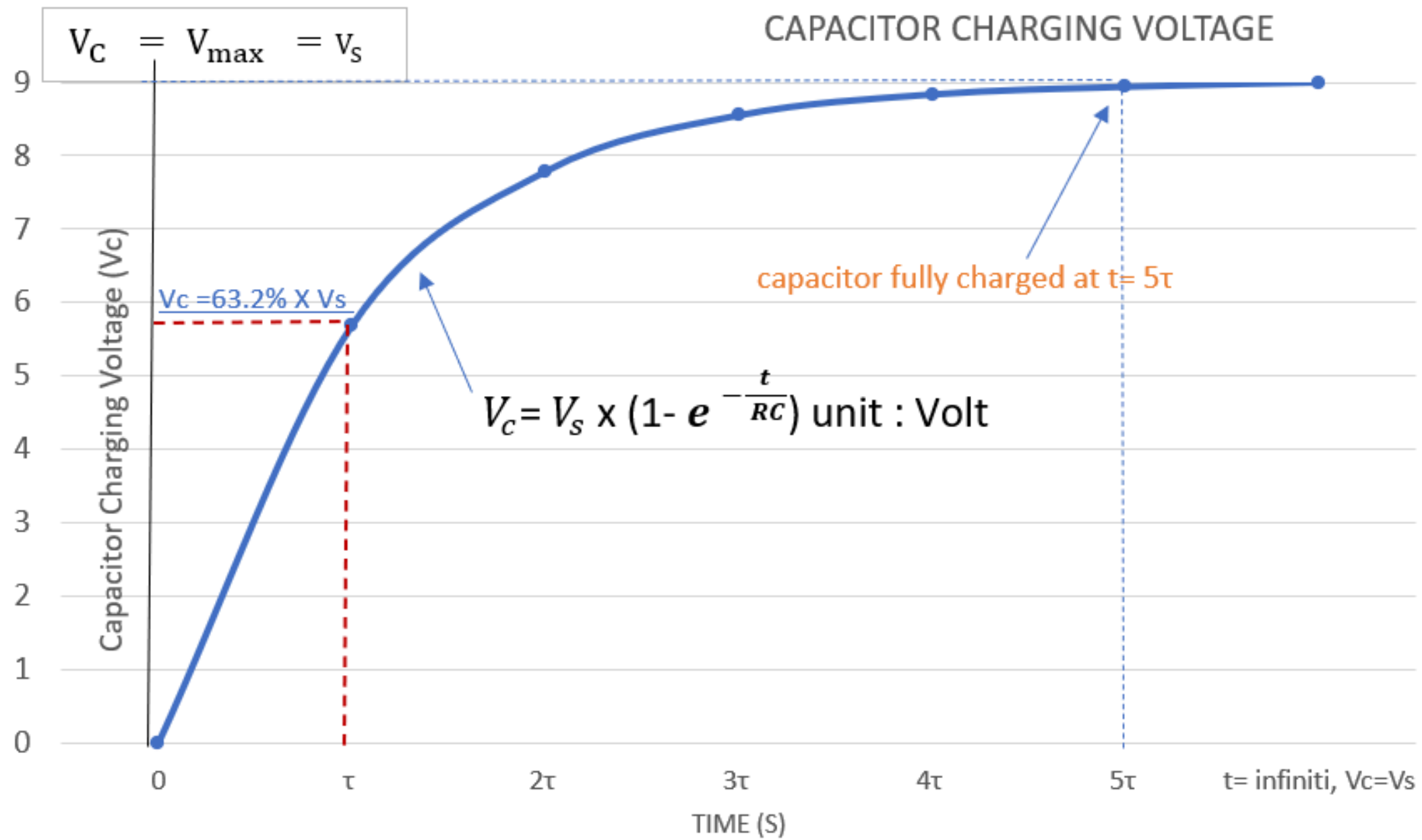

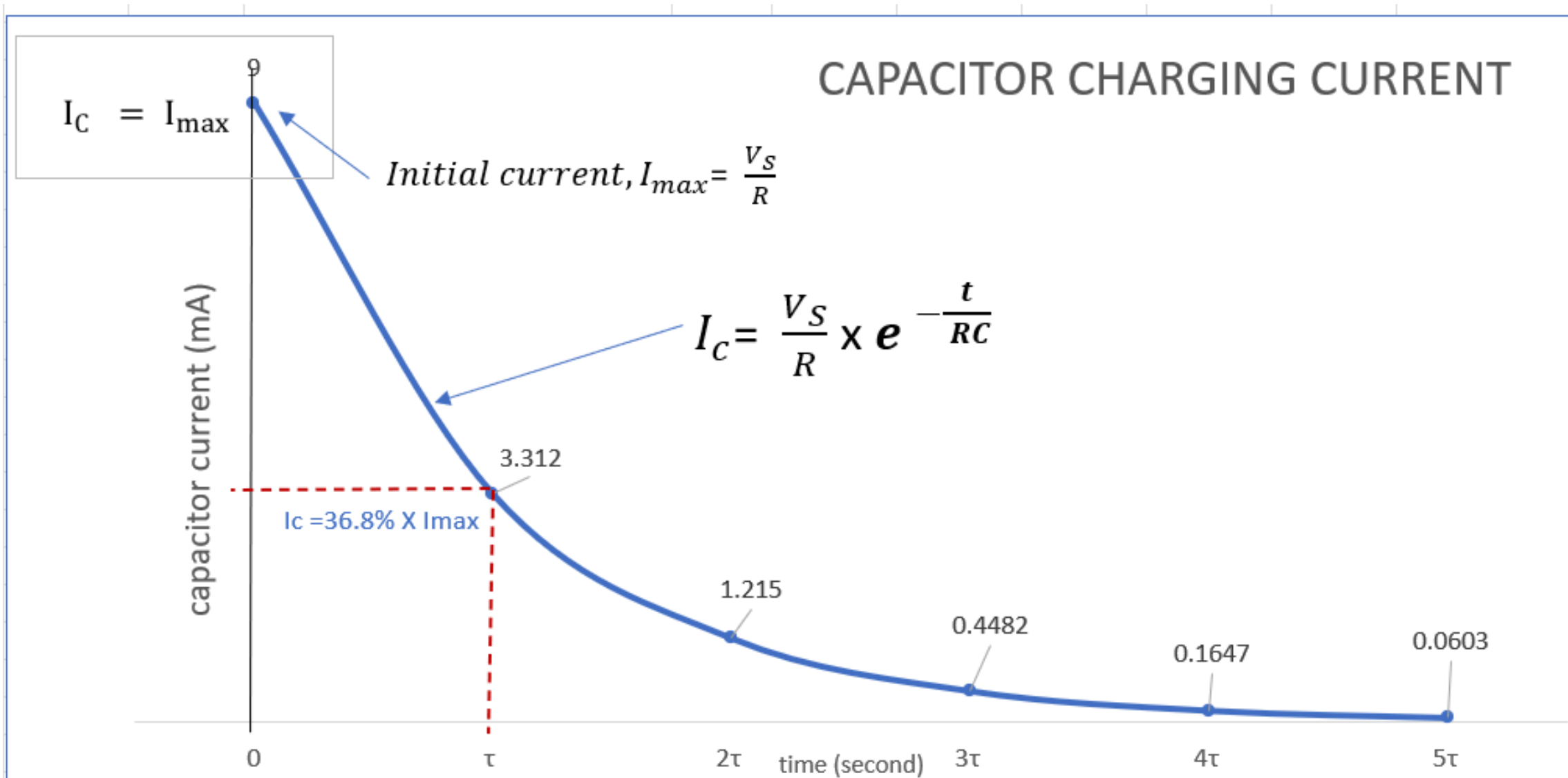At long time, capacitor like an open circuit,
 $V_C = V_S, i = 0 ; t = \infty$



		$\tau = RC = 1000 \times 6\mu = 6\text{ms}$						
		0	τ	2τ	3τ	4τ	5τ	T= INFINITI
		0	6ms	12ms	18ms	24ms	30ms	
		e-0	e-1	e-2	e-3	e-4	e-5	
$e^{-\frac{t}{RC}}$		1	0.368	0.135	0.0498	0.0183	0.0067	0
$1 - e^{-\frac{t}{RC}}$		0	0.632	0.865	0.95	0.982	0.9933	1
$I_{max} = \frac{V_S}{R}$	A	0.009	0.009	0.009	0.009	0.009	0.009	
$I_C = \frac{V_S}{R} \times e^{-\frac{t}{RC}}$	mA	9	3.312	1.215	0.4482	0.1647	0.0603	
$V_C = V_S \times (1 - e^{-\frac{t}{RC}})$	V	0	5.688	7.785	8.55	8.835	8.94	9



CHARGING

At long time, capacitor like an open circuit,
 $V_c = V_s, i=0 ; t=\infty$


Capacitor charging,

$$V_c = V_s (1 - e^{-\frac{t}{\tau}})$$

Time constant, $\tau = RC$

$$i = i_{max} e^{-\frac{t}{RC}}$$

$$I_{max} = \frac{V_s}{R}$$

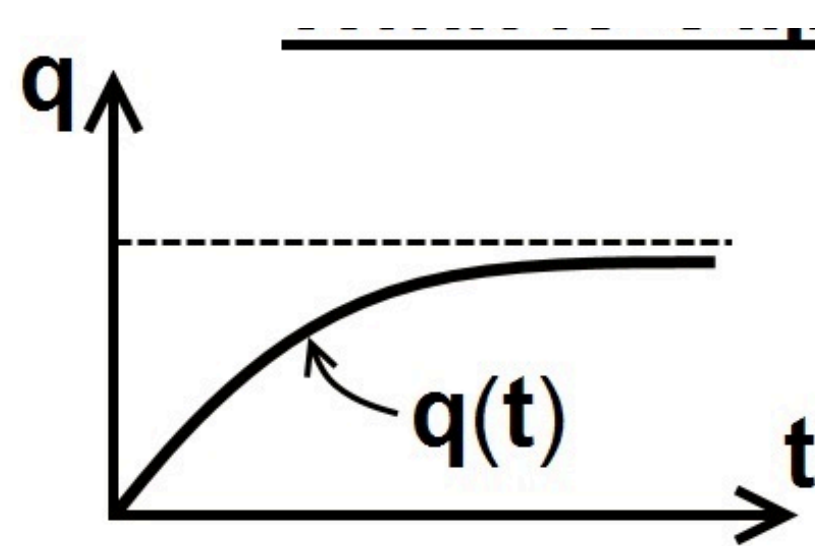

or $Q = CV$

$$C = \frac{Q}{V}$$

time constant (τ)



describes how quickly the circuit responds to a change



the time constant is defined as $\tau = RC$ for an RC circuit, and $\tau = L/R$ for an RL circuit.



After one time constant, the voltage or current decays to about 36.8% of its initial value. (discharge or decay)



After one time constant, the voltage or current has reached about 63.2% of its final value. (charging or rising)



After about 5τ , the response is considered to have settled, reaching over 99% of its final value.



Resistor Functions:

- Controls Charging Speed
- as a discharge path
- It prevents a sudden rush of current when the switch is turned on (limit currents).
- Defines Time Constant (RC).

A capacitor stores energy in the form of an electric field.

If there is no path (like a resistor or wire) for current to flow and no leakage, the stored energy stays in the capacitor.

-retains its charge



UNDERSTANDING THE CAPACITOR CHARGING EQUATION

$$V_s = V_R + V_C = i(t)R + \frac{q(t)}{C}$$

$$dQ = \left[\frac{V_s}{R} - \frac{Q}{RC} \right] dt = \left[\frac{CV_s}{RC} - \frac{Q}{RC} \right] dt$$

$$\frac{dq}{dt} + \frac{1}{RC}q = \frac{V_s}{R}$$

$$V_C(t) = \frac{q(t)}{C} = V_s \left(1 - e^{-t/RC} \right)$$

$$q(t) = C \cdot V_s \cdot \left(1 - e^{-\frac{t}{RC}} \right)$$

rate of change of current is precisely governed by that exponential

$$e^{-\frac{t}{\tau}} = e^{-\frac{t}{RC}}$$



$$C = \frac{Q}{V_C} = \frac{\epsilon A}{d}$$

increasing current doesn't increase capacitance

$$V_C = \frac{Q}{C}$$

capacitor voltage depends on charge . Charge is depending on current value.

$$I_t = \frac{dQ}{dt}$$


current is the rate of change of charge over time.

If current flows, charge accumulates—and that increases the voltage across the capacitor.

current influences charge, and charge determines voltage.


DISCHARGING

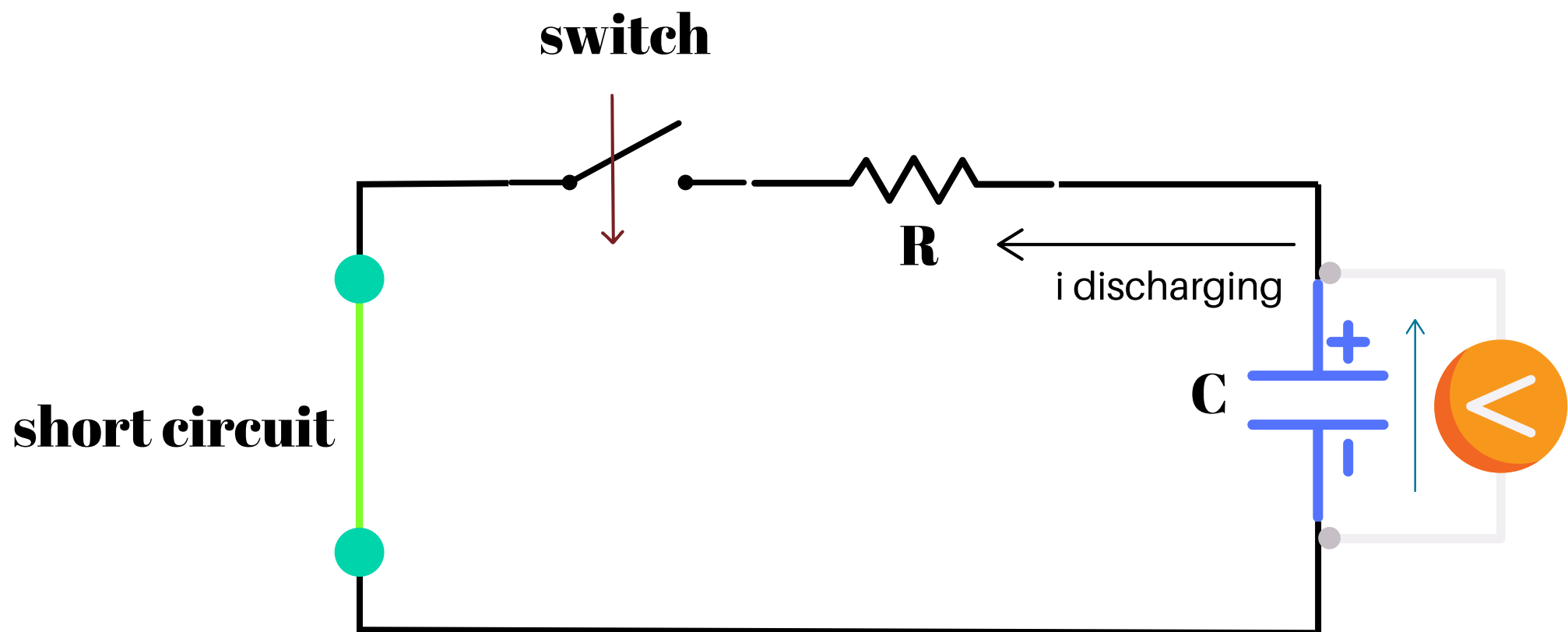WHAT HAPPEN WHEN BATTERY IS DISCONNECTED?





When the switch is pressed, the battery is disconnected (short circuit), and no current flows through the circuit from the battery. The capacitor begins to release its stored energy by discharging through the resistor. The voltage across the capacitor gradually decreases over time. When the capacitor is fully discharged, the voltage across it becomes constant at zero volts (steady state). However, if there is no resistor or discharge path, the capacitor retains its charge for a while.

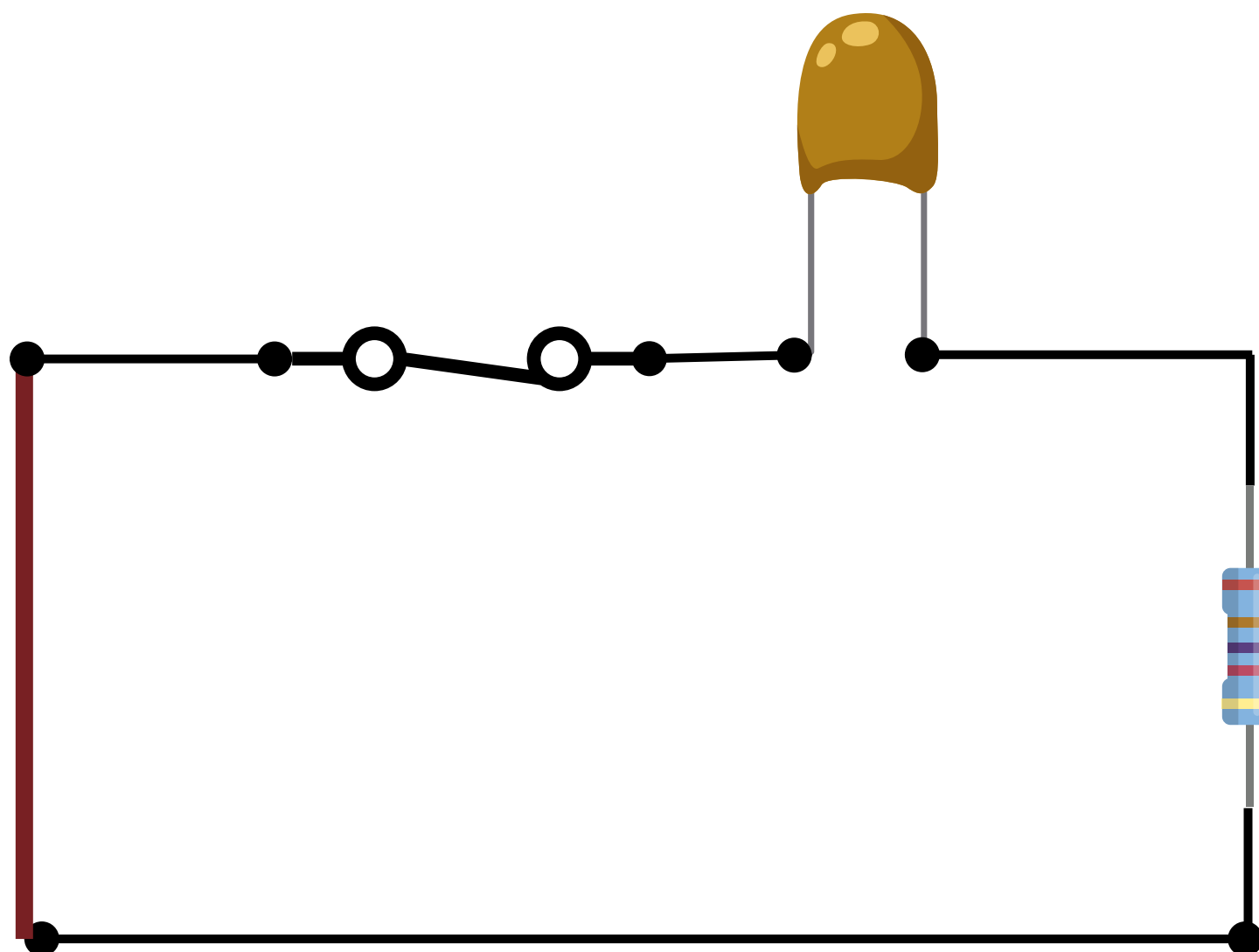When discharging, both the current and voltage of the capacitor drop gradually and follow an exponential curve until they reach zero



DISCHARGING

CAPACITOR VOLTAGE (V_C) VERSUS TIME

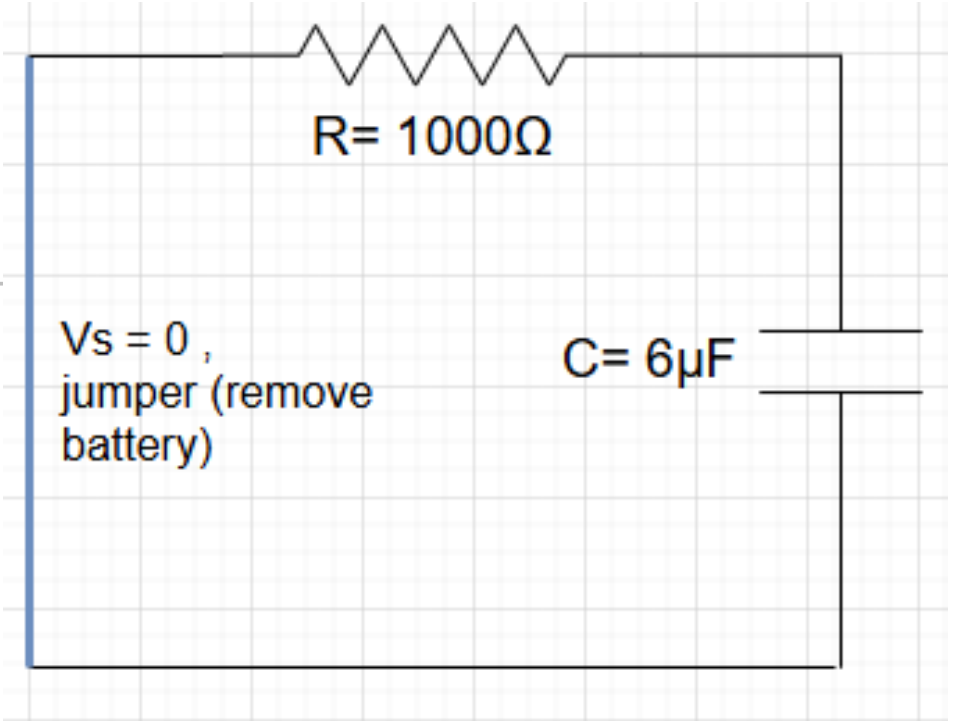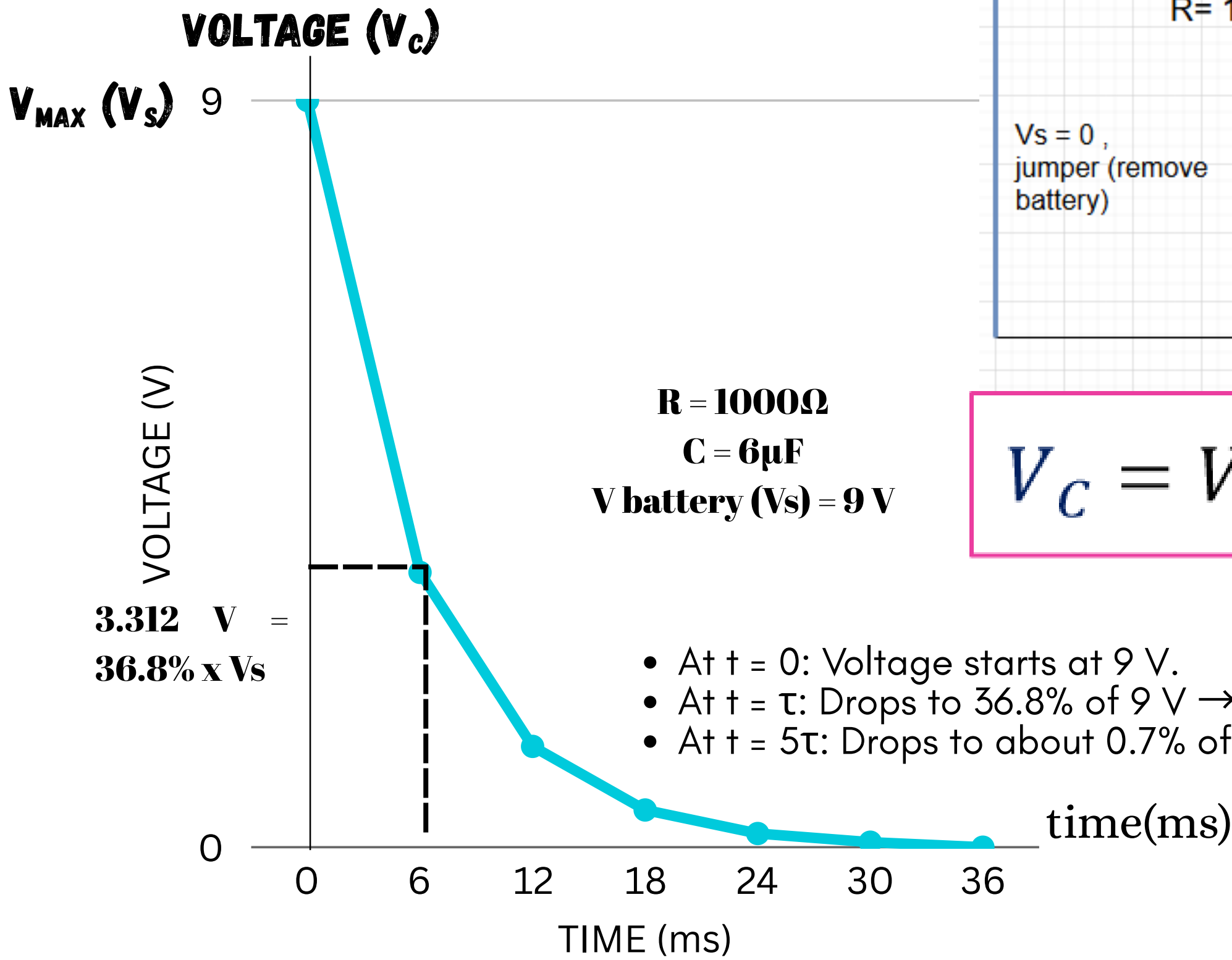

$$V_C = V_S (e^{-\frac{t}{\tau}})$$

Discharging

V_C versus Time


t	$e^{-\frac{t}{RC}}$	$\frac{V_C}{V_S} = (e^{-\frac{t}{RC}})$	$V_C = V_S (e^{-\frac{t}{RC}})$
0	1	1	9
τ ₁ = 6ms	$e^{-\frac{t}{RC}} = e^{-\frac{6ms}{6ms}} = e^{-1} = 0.368$	$e^{-1} = 0.368$	3.312
τ ₂ = 12ms	$e^{-2} = 0.135$	$e^{-2} = 0.135$	1.215
τ ₃ = 18ms	$e^{-3} = 0.0498$	$e^{-3} = 0.0498$	0.4485
τ ₄ = 24ms	$e^{-4} = 0.0183$	$e^{-4} = 0.0183$	0.1647
τ ₅ = 30ms	$e^{-5} = 0.0067$	$e^{-5} = 0.0067$	0.0603
....100% / t=∞	0	0	0

$V_S = 9v$ Time constant, $\tau = RC$ $RC = 1000ohm \times 6\mu F = 6ms$




Voltage	Component
V _S	Battery
V _C	Capacitor
V _R	Resistor

DISCHARGING

CURRENT VERSUS TIME



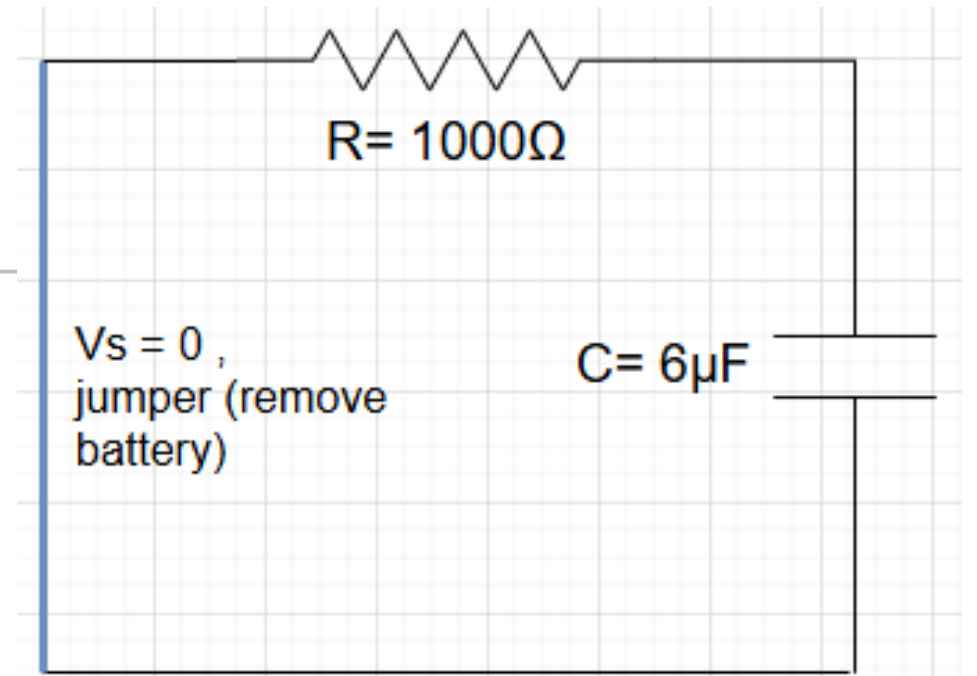


$$i = -i_{max} e^{-\frac{t}{RC}}$$

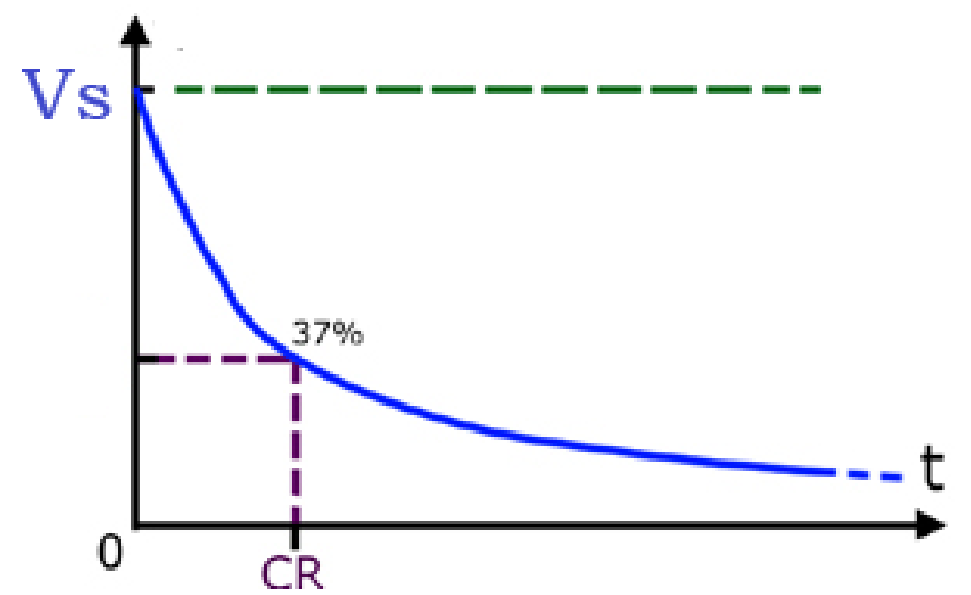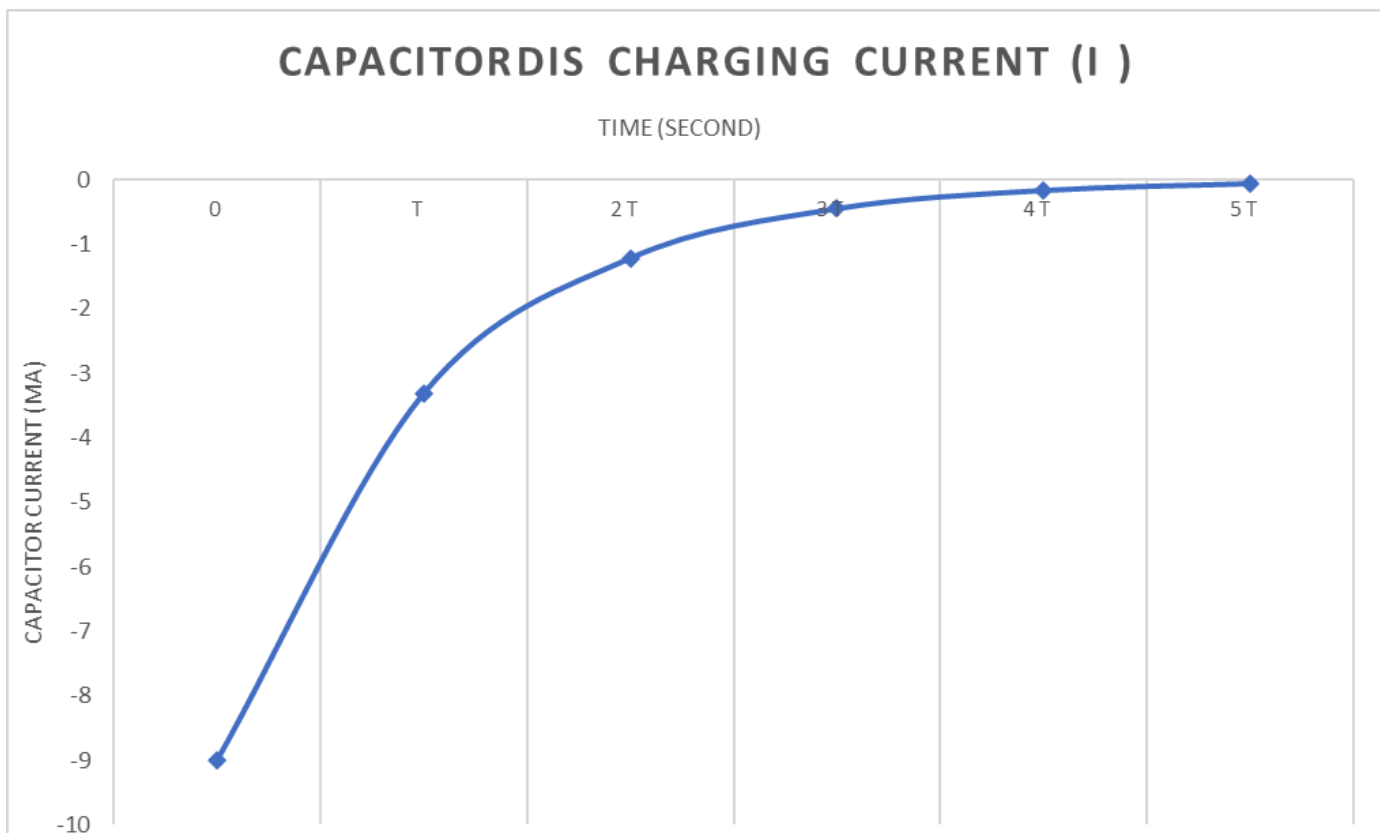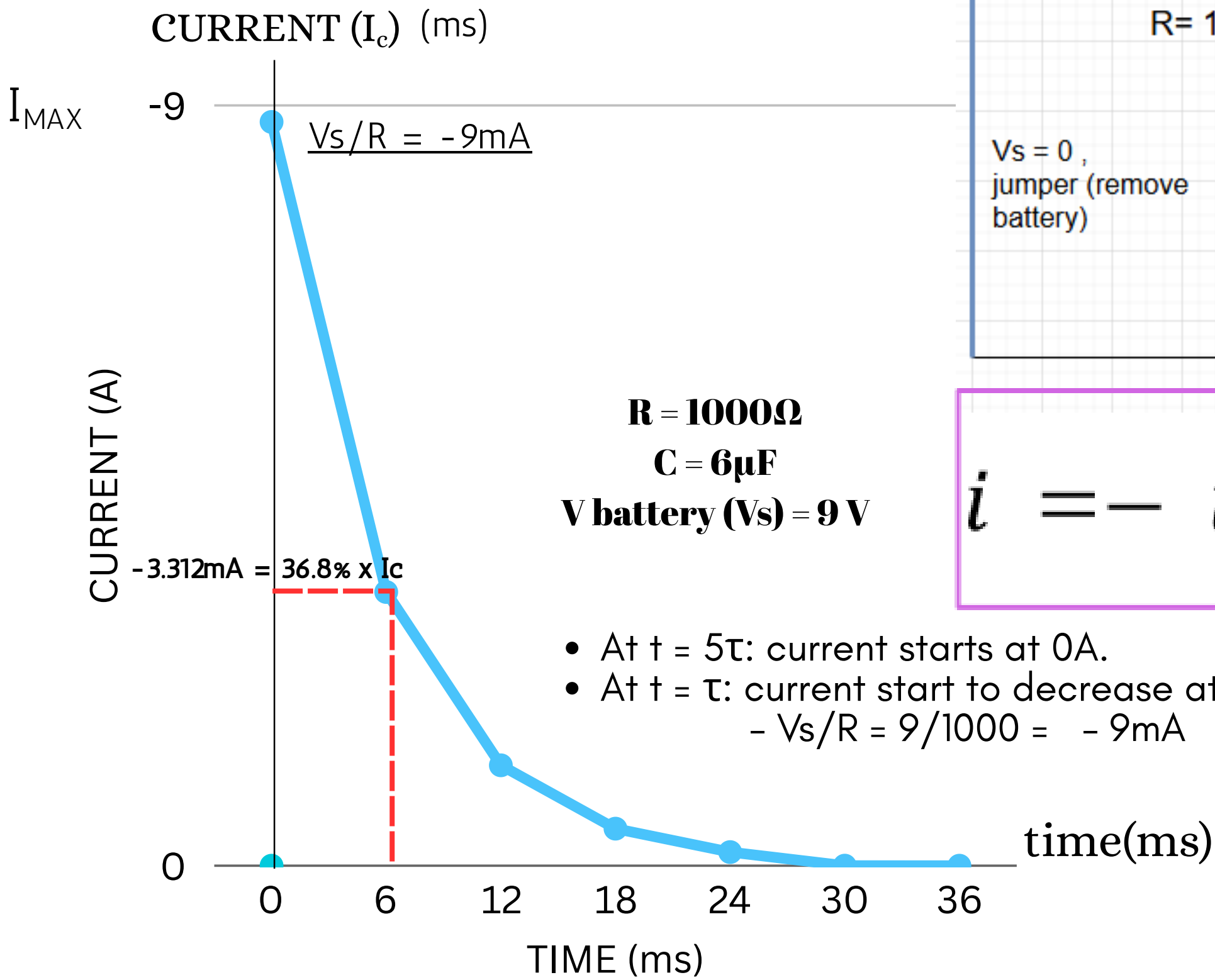

		$\tau = RC = 1000 \times 6\mu = 6ms$					
		0	τ	2τ	3τ	4τ	5τ
		0	6ms	12ms	18ms	24ms	30ms
		e-0	e-1	e-2	e-3	e-4	e-5
$e^{-\frac{t}{RC}}$		1	0.368	0.135	0.0498	0.0183	0.0067
$I_{max} = -\frac{V_S}{R}$	A	0.009	0.009	0.009	0.009	0.009	0.009
$I_c = -\frac{V_S}{R} \times e^{-\frac{t}{RC}}$	mA	-9	-3.312	-1.215	-0.448	-0.165	-0.0603

DISCHARGING GRAPH

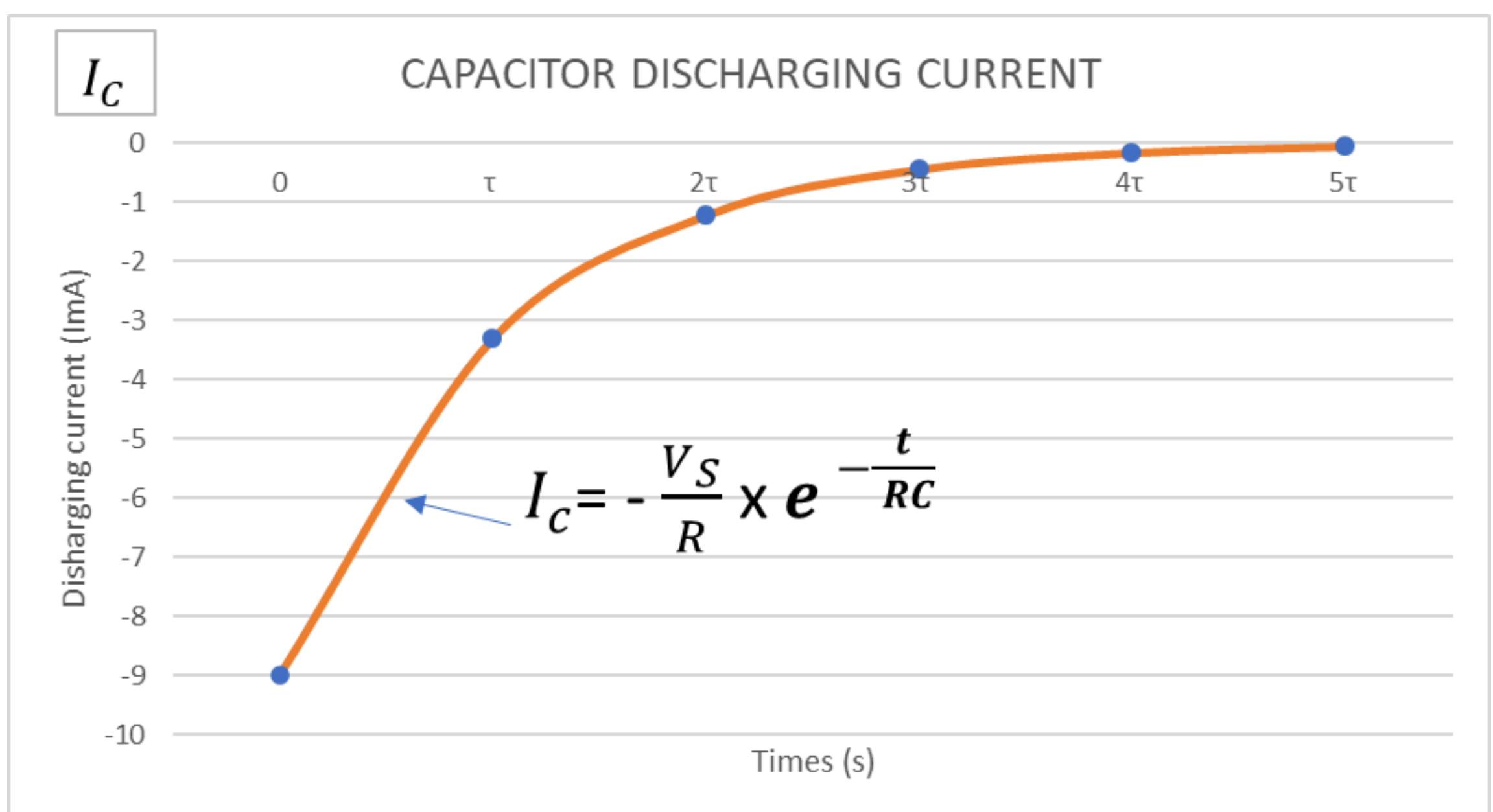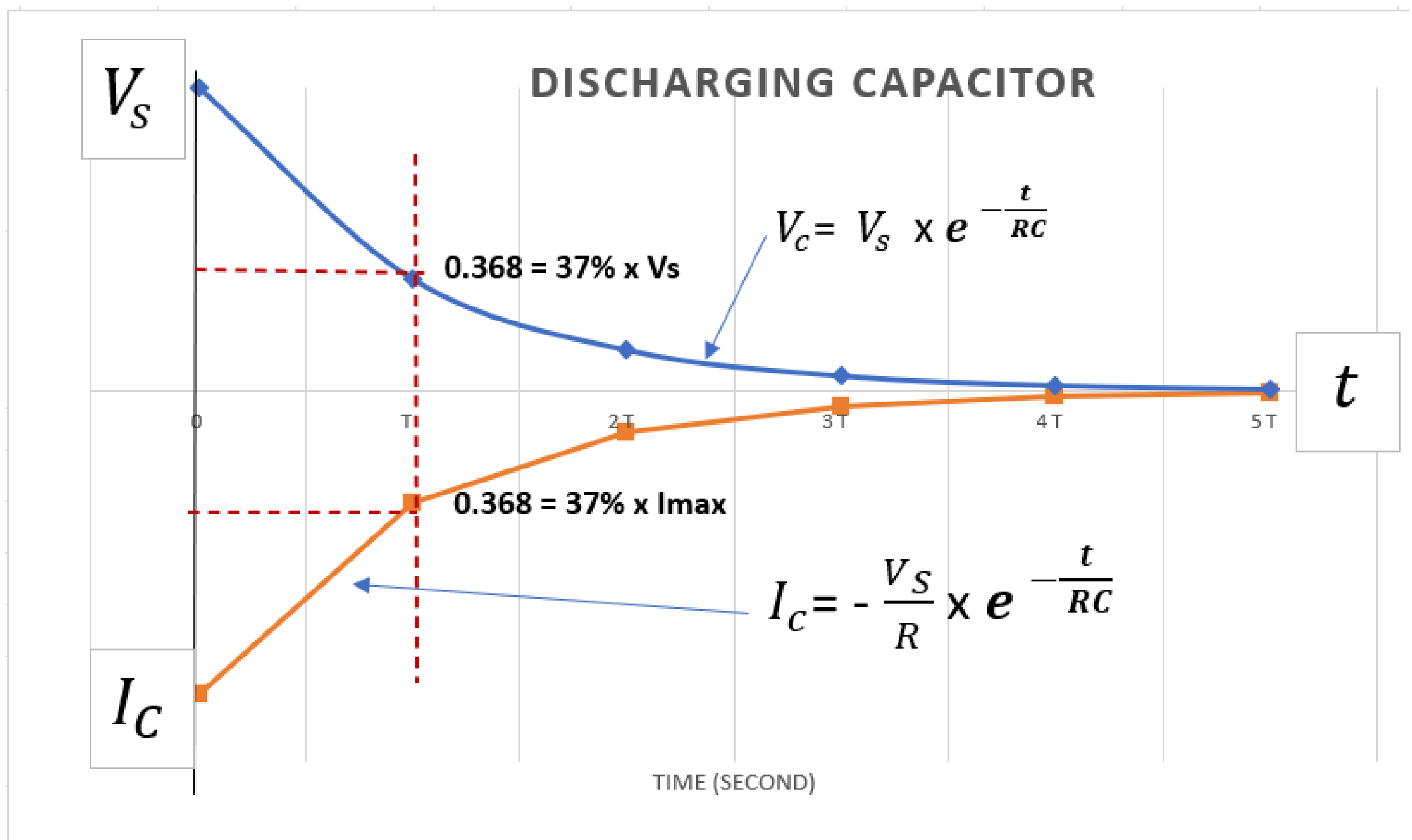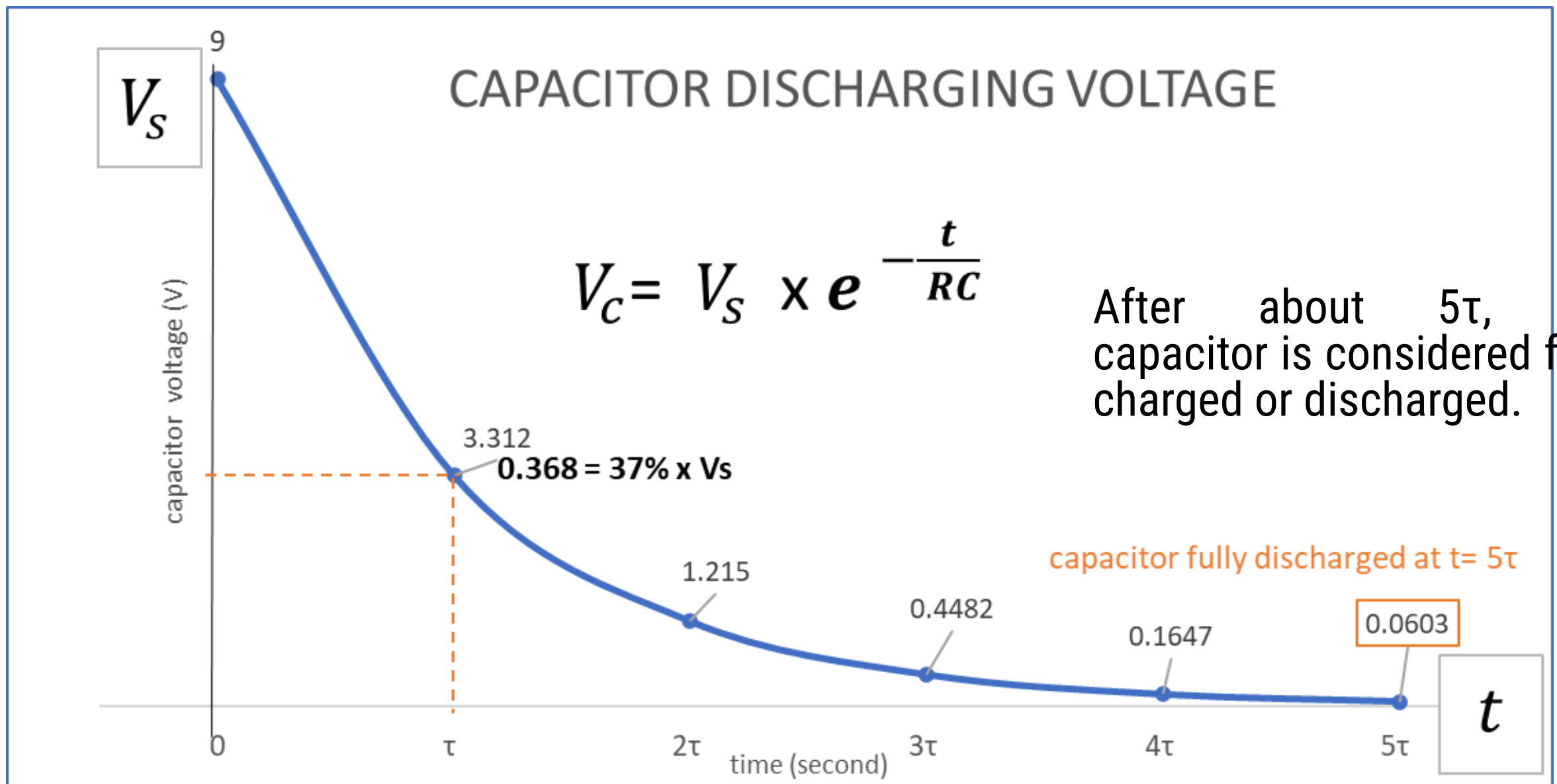



DISCHARGING

- After about 5τ , the capacitor is considered fully charged or discharged.
- After one time constant (τ), the voltage across the capacitor drops to about 36.8% of its initial value.
- After five time constants, the capacitor is considered fully discharged (less than 1% of initial voltage).

$$\text{Time constant, } \tau = RC$$

capacitor discharging voltage

$$V_C = V_S \left(e^{-\frac{t}{\tau}} \right)$$

capacitor discharging current

$$i = - i_{max} e^{-\frac{t}{RC}}$$

When discharging, both the current and voltage of the capacitor drop gradually and follow an exponential curve until they reach zero

SUMMARY

CHARGING AND DISCHARGING

Charging

$$V_C = V_S (1 - e^{-\frac{t}{\tau}})$$

$$i = i_{max} e^{-\frac{t}{RC}}$$

Discharging

$$V_C = V_S (e^{-\frac{t}{\tau}})$$

$$i = -i_{max} e^{-\frac{t}{RC}}$$

Time constant, $\tau = RC$

Time of fully charged, $5\tau = 5RC$

Initial current, $i_0 = i_{max} = \frac{V_S}{R}$

Energy stored, $E = \frac{1}{2} CV^2$ joule

t=0 (initial time)	t=∞
$V_C = 0;$	$V_C = V_S = V_{max}$
$Q=0$	$Q = C \times V_S$
$V_R = V_S$	$V_R = 0$
$i = \frac{V_S}{R}$	$i = 0;$

V_S = Source Voltage/Battery Voltage

V_C = voltage across capacitor

$i_{max} = i_0$ = initial current at $t = 0$



SOALAN-SOALAN PEPERIKSAAN - UNIT
PEPERIKSAAN POLIPD

EXAMPLE 1

A capacitor with a capacitance of $20 \mu\text{F}$ which is connected in series to a $200 \text{ k}\Omega$ resistor is being placed a 250 VDC voltage supply. Calculate the initial current, initial potential different across capacitor, the time constant during charging, the time taken to be fully charge and the energy stored in the capacitor.

SOLUTION

- a) Intial current ($t=0$) ; $I = V/R = 250/200\text{k} = 1.25\text{mA}$
- b) intial potential different; $V_c=0$
- c) Time constant , $t = RC = 200\text{k} \times 20\mu = 4\text{s}$
- d) time taken to be fully carge, $t= 5RC = 5 \times 4\text{s} = 20\text{s}$
- e) Energy (E)= $\frac{1}{2} \times C \ v^2 = \frac{1}{2} \times 20\mu \ 250^2 = 0.625\text{J}$

JUN 15

EXAMPLE 2

Figure C2 shows a $4700\mu\text{F}$ capacitor is connected in series with a $5.6\text{ k}\Omega$ resistor and a 6Vdc supply. When the switch is ON, calculate the time constant, initial charge current, time taken for capacitor voltage to increase to 3V , the voltage across the capacitor at 20s and energy stored in the capacitor.

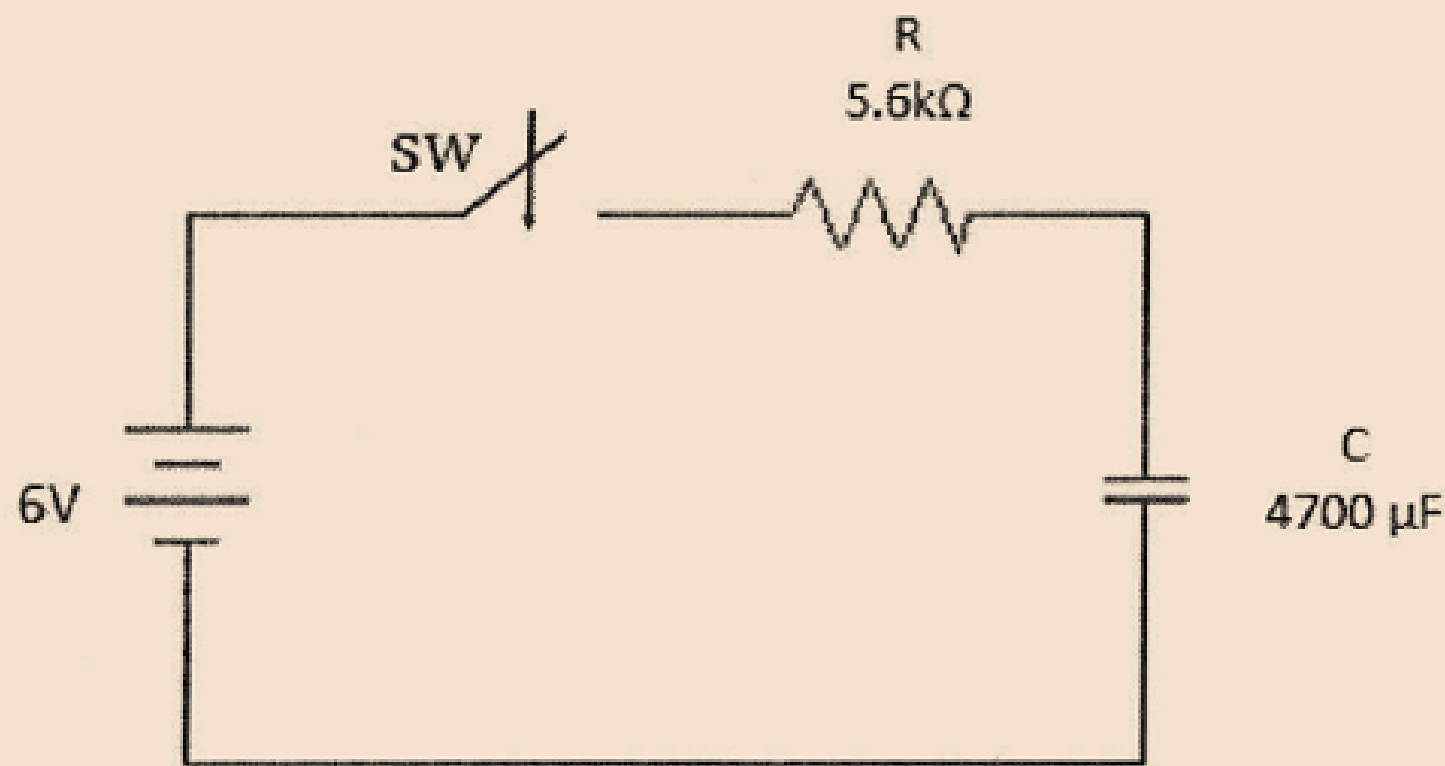


Figure C2

1 time constant, $t = RC = 5600 \times 4700\mu = 26.32\text{s}$

2 Initial charge current, $i = \frac{v}{R} = \frac{6}{5600} = 1.0714\text{ms}$

3 the voltage across the capacitor at 20s

$$V_C = V_s (1 - e^{-\frac{t}{\tau}})$$

$$V_C = 6(1 - e^{-\frac{20}{26.32}})$$

$$V_C = 6(1 - 0.4677) = 6 \times 0.532277 = 3.194\text{ v}$$

4 time taken for capacitor voltage to increase to 3V

$$V_C = V_s (1 - e^{-\frac{t}{\tau}})$$

$$3 = 6(1 - e^{-\frac{t}{26.32}})$$

$$\frac{3}{6} = (1 - e^{-\frac{t}{26.32}})$$

$$0.5 = 1 - e^{-\frac{t}{26.32}}$$

$$-0.5 = -e^{-\frac{t}{26.32}}$$

$$0.5 = e^{-\frac{t}{26.32}}$$

$$\ln 0.5 = \ln e^{-\frac{t}{26.32}}; \ln e = 1$$

$$-0.6931 = -\frac{t}{26.32}$$

$$t = 26.32 \times 0.6931 = 18.242\text{s}$$

5 Energy (E) = $\frac{1}{2} \times C \times v^2 = \frac{1}{2} \times 4700\mu \times 6^2 = 0.0846\text{J}$

EXAMPLE 3

A capacitor consists of two circular metal plates, each with a radius of 5 cm. The plates are parallel to each other and separated by a distance of 1 mm. The capacitor also connected to 9V battery across the plates in vacuum. Calculate the capacitance of the capacitor and the charge on each plate.

SOLUTION

Given:

Radius of each plate, $r = 5 \text{ cm} = 0.05 \text{ m}$

Separation, $d = 1 \text{ mm} = 0.001 \text{ m}$

Vacuum between plates $\rightarrow \epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$

Voltage across plates, $V = 9 \text{ V}$

$$C = \frac{\epsilon \times A}{d} ; \epsilon = \epsilon_0 \times \epsilon_r$$

$$C = \frac{\epsilon \times A}{d} = \frac{\epsilon_0 \epsilon_r \times A}{d} ; \epsilon = \epsilon_0 \times \epsilon_r$$


$$A = \pi r^2 = \pi(0.05)^2 = (7.854 \times 10^{-3}) \text{ m}^2$$

$$C = \frac{(8.85 \times 10^{-12})(1)(7.854 \times 10^{-3})}{0.001} = 6.95 \times 10^{-11} \text{ F} = \mathbf{69.5 \text{ pF}}$$

$$Q = C \times V = 69.5 \text{ pF} \times 9 = \mathbf{625.5 \text{ pF}}$$

SELF-EXERCISE

Figure below shows a schematic diagram that consists of resistive and capacitive load. If the switch SW is switched to node a at $t = 0\text{ s}$.

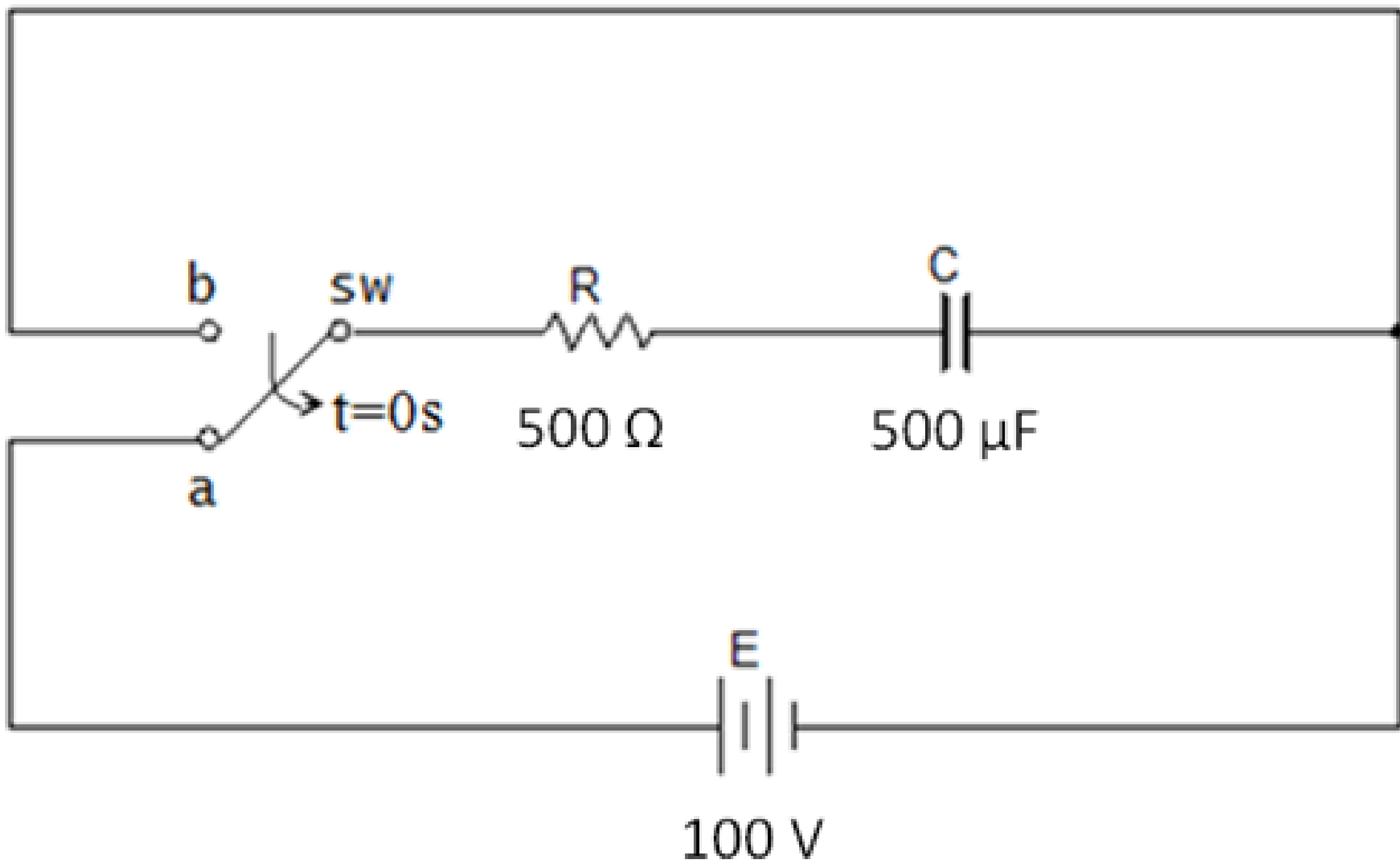

- COMPUTE the time constant, τ
- PREDICT the maximum voltage of the capacitor.
- CALCULATE the instantaneous value of current when $t = 0.25\text{ms}$.
- CALCULATE the time taken to make the instantaneous value of charging voltage equals to 15V.
- CALCULATE the maximum energy stored by the capacitor


Answer :

- $\tau = 250\text{ms}$, b) $v_c = 100\text{V}$, c) $t = 155.76\text{ mA}$, d) $t = 0.1625\text{ ms}$
- $E_c = 2.5\text{ J}$

REFERENCES

1. Malvino, A., & Bates, D. (2016). *Electronic principles* (8th ed.). McGraw-Hill Education.
2. Floyd, T. L. (2012). *Electronic devices: Conventional current version* (9th ed.). Pearson.
3. Schuler, C. A., & Tokheim, R. L. (2003). *Electronics: Principles and applications* (7th ed.). Glencoe/McGraw-Hill.
4. Paynter, R. T. (2006). *Introductory electronic devices and circuits: Conventional flow version* (7th ed.). Pearson Prentice Hall.
5. Alexander, C. K., & Sadiku, M. N. O. (2017). *Fundamentals of electric circuits* (6th ed.). McGraw-Hill Education.
6. Dorf, R. C., & Svoboda, J. A. (2010). *Introduction to electric circuits* (8th ed.). Wiley.
7. Alexander, C. K., & Sadiku, M. N. O. (2013). *Fundamentals of electric circuits* (5th ed.). McGraw-Hill

e ISBN 978-629-7643-70-0

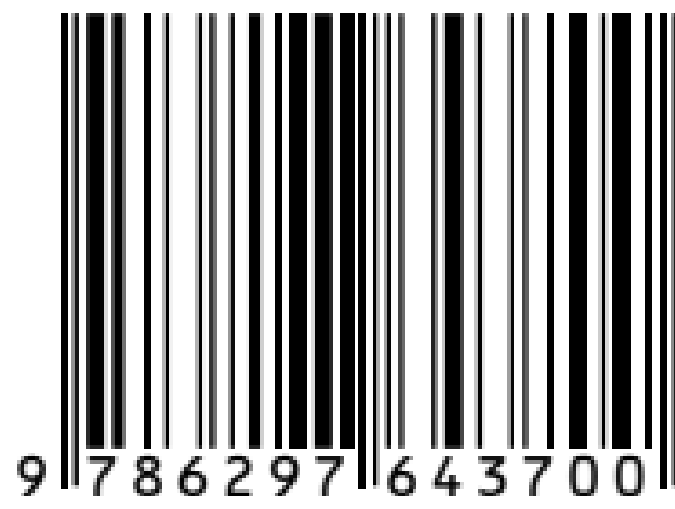

POLITEKNIK PORT DICKSON
(online)